

Rapid prototyping

- ATMega Controller Board
- Electric Fence Energiser
- UV LED Light Box
- Design Tips





NEW 2005 CATATIONS OUT NOW

> Our 2006 catalogue is jam-packed with over 780 new and exciting products! We sell a huge range of innovative products through our FREE 410+ page catalogue. Phone or hop on line to www.jaycarelectronics.co.uk and purchase from us 24/7/365 through our secure encrypted system. Post and Packing charges are modest so you can have any of 8000+ unique products delivered to your door within 7 - 10 days of your order!

"The Champ" Audio Amplifier Kit

KC-5152 €1.95 ÷ post & packing This tiny module uses the LM386 audio IC, and will deliver 0.5W into 8 ohms from a 9 volt supply making it ideal for all those basic audio projects. It features variable gain, will happily run from 4-12VDC and is smaller than a 9 volt battery. allowing it to fit into the tightest of spaces,

PCB and all electronic



"Pre-Champ" Versatile Preamplifier Kit

KC-5166 £2.60 + post & packing Specifically designed in conjunction with our champ amplifier (KC-5152 shown left). Unless your signal has sufficient amplitude the 'Champ' will not produce its maximum power output. The Pre-Champ is the answer with a gain in excess of 40dB. By changing the resister you can vary the gain and there is provision on the PCB for an electret microphone (Use AM-4010 £0.81).

· Power required 6 - 12VDC and can be battery powered.

 PCB and all electronic components included.

deal for school or

Lead-Acid Battery Zapper Kit

KC-5414 £11.75 + post & packing

This simple circuit is designed to produce bursts of high-energy pulses to help reverse the damaging effects of sulphation in wet lead acid cells. This is particularly useful when a battery has been sitting for a period of time without use. The effects are dependant of the battery's condition and type, but the results can be quite good indeed.

Kit supplied with case, silkscreened lid, leads, inductors,



Theremin Synthesiser Kit

KC-5295 £14.75 + post & packing

The Theremin is a weird musical instrument that was invented early last century but is still used today. The Beach Boys' classic hit "Good Vibrations" featured a Theremin. By moving. your hand between the antenna and the metal plate, you can create strange sound effects. Kit. includes a machined, silkscreened, and predrilled case, circuit board, all electronic components, and clear English instructions.

 This product is also available built and fully tested Cat. AM-4025 £29.95.

Automotive Headlight Reminder Kit KC-5317 £8.75 + post & packing

Features include a modulated alarm, ignition and lights monitoring optional door switch detection, time-out alarm and a short delay before the alarm

sounds. Build and install this hassle saving kit and enjoy a feature in your car that many luxury vehicle owners have long taken for granted, Kit supplied with case, silkscreened lid and all electronic components.



Tempmaster Kit

KC-5413 £11.75 + post & packing

Need accurate temperature for a wine cooler or been brewing heater?

This project turns a regular fridge or freezer into a wine cooler by accurately controlling the temperature to make

it suitable for wine storage: A much cheaper option than commercial units. Kit supplied with PCB, case, and all electronic components.

· Australian to UK mains adaptor required > use PP-4020 £2.95.



Requires 9VDC wall adaptor (Maplin #GS74R £9.99).





KC-5404 (red) £41.75 + post & packing

"Clock Watcher's" LED Clock Kits

These clocks are hypnoticl They consist of an AVR driven clock circuit, that also produces a dazzling display with the 60 LEDs around the perimeter. It looks amazing, but can't be properly explained here. We have filmed it in action so you can see for yourself on our website www.jaycarelectonics.com! Kit supplied with double sided silkscreened plated through hole PCB and all board components as well-

as the special clock housing! Available in Blue: (KC-5416) and Red (KC-5404). Requires 12VAC wall adaptor (Maplin #GU10L £9.99)



KC-5416 (blue) £55.25 post & padding

780+ new

Log on to www.jaycarelectronics.co.uk/elektor for your FREE catalogue!

0800 032 7241

(Monday - Friday 09.00 to 17.30 GMT + 10 hours only). For those who want to write: 100 Silverwater Rd Silverwater NSW 2128 Sydney AUSTRALIA

Post and Packing Charges: Cost

Order Value - £49.99 £5 £50 - £99.99 £10 £20 £100 - £199.99 £200 - £499.99 £30

£40 £500+ Max weight 12lb (5kg) Heavier parcels POA. Minimum order £20.



Helping You Succeed



Does your business need more support and resources?

Successful organizations recognize the value of a strategic supplier relationship to help them deliver innovative products to their markets in a timely and cost-effective manner. Microchip Technology supports more than 45,000 customers worldwide, and we're

committed to helping you succeed. In addition to our high-performance silicon solutions, Microchip provides a long list of support functions that reduce time to market and lower your total system cost. And we have significantly expanded our local technical resources.

Use microchipDIRECT to:



- Order directly from Microchip, 24 hours a day, 7 days a week with a credit card or credit line
- Receive competitive, direct volume pricing on all devices
- Check our product inventory
- Order broken reels at steep discounts
- Use fast and inexpensive production programming (now available)
- Place and maintain your order securely from any network connection
- Assign a PO number to your order
- Create a unique part number for any item ordered
- Receive e-mail notification of orders, deliveries, quote status and more







The final product

As announced by our Publishing Plan printed on the Sneak Preview page every month, the focus in this issue is very much on PCB production techniques. Elektor Electronics PCBs are famous the world over for their quality and consistent appearance. Sure, they're also a tad expensive compared to what the competition are supplying but then the quality and finish are

vasily superior. Here at Elektor, the change from manual artwork design using masking tape and photographic reproduction techniques to an 100% PC-driven process was gradual, and took place in the early 1990s. The use of a PC to draw a schematic and then run a PCB design program was not forced or even 'suggested' by our governors at the time. In fact, some of the younger lab designers at the time started to discover the advantages of the PC route for themselves, eventually supplying files instead of drawings to their colleagues in the PCB design department. Others stuck to pencil, paper and rubber with equally good results particularly in RF and space critical designs. No matter how the final artwork was produced, we never actually mass-produced those famous Elektor circuit boards — this was always farmed out to PCB manufacturers. We did, however, handle the storage and packaging of what must have amounted to hundreds of thousands of those blue and green boards. Also, to this day we have our own PCB eiching and drilling facilities. These are used to make prototypes and one-offs of any board we're proud and happy to have kept single-sided (not too many these days, thanks to the micros). I do recall the excitement in the lab and editorial offices about 15 years ago when a parcel arrived containing 500 or so boards for a recently published project. At last, the proud designer was able to see the fruit of all his design efforts. More importantly however, readers all over the world were more than satisfied with superbly produced circuit boards with a component overlay and silk screen finish! Today, there is still the satisfaction not only of publishing these wonderful designs and hearing from you but also of holding a perfectly machined printed circuit board with an Elektor

Jan Buiting, Editor


production number printed in a corner.



International R8C Design Competition great prizes - easy participation page 14

24 PCB Production in the Fast Lane

 Once the design of a circuit has reached the point where the PCB CAD data file has been produced, a physical board is usually wanted as soon as possible so that a one-off unit or laboratory prototype can be assembled and tested. In this article we look how to choose between the various alternative routes to manufacture and survey their advantages and disadvantages.



CONTENTS




The stand-alone analyser described here can be used as a hand-held unit or fitted in your car. Diagnostic data is evaluated using an ATmega 16 and shown on an LCD with four rows of 20 characters. Up to eight parameters can be constantly shown on the display while you're driving. Having this information at your fingertips can be especially handy if you have car trouble.

68 Electric Fence Energizer

Are you bothered by stray cats and dogs prowling and digging in your garden? Or does your own pet require strong persuasion to stay within a restricted area? This electric fence generator may well be the answer to your problems. A simple generator built around a 555 timer and an old ignition coil are sufficient to build a suitable circuit at a small outlay.

30 Mini ATMega Board

 Even if the ATmega microcontroller isn't necessarily mega, it's still quite popular and we feel it hasn't really received the attention it deserves. The Mini ATmega Board described here puts a change to that, and a nice application for it — our Onboard OBD2 Analyser— is featured in an accompanying article.



Volume 32 May 2006 no. 354

know-how

18 Lead-free? No problem

hands-on

- 30 Mini ATMega Board
- 36 Onboard OBD-2 Analyser
- 46 FPGA Course (2)
- 52 An R8C-based oscilloscope
- 64 UV LED Light Box
- 68 Electric Fence Energizer
- 72 Design Tips
 Reforming old capacitors
 Current surge limiter for toroidal
 transformers
 PCB pin insertion tool
 Accurate timebase

technology

- 24 PCB Production in the Fast Lane
- 60 E-blocks for Prototyping

info & market

- 6 Colophon
- 8 Mailbox
- 10 News & New Products
- 14 International R8C Design Competition
- 42 OBD-2 in Elektor Electronics
- 81 Elektor SHOP
- 84 Sneak Preview

infotainment

- 75 Retronics: 1-to-3 Phase Converter (1994/1995)
- 77 Hexadoku (5)



Volume 32, Number 354, May 2005

ISSN 0268/4519

Elektor Electronics aims at inspiring people to master electronics at any personal level by presenting construction projects and spotting developments in electronics and information technology.

Publishers: Elektor Electronics (Publishing), Regas Brentford, 1000 Great West Road, Brendord TWB 9HH, England, Tel. (± 44) (0) 208-261-4509, fax: (± 44) (0) 208-261-4447 www.elektor-electronics.co.uk.

The magazine is available from newsagents, bookshops and electronics retail outlets, or on subscription. Elektor Electronics is published 11 times a year with a double issue for July & August.

Under the name Eleton and Eletons, the magazine is also published in French, German and Dutch. Together with franchised editions the magazine is on origination in more than 50 countries.

International Editor: Iriat Heffels (m.heffels@segment.n)

Editor: Jan Busing (editor@kitkion-electronics.co.uk)

International editorial staff; Harry Baggen, Thijs Beckers, Ernst Krempelsauer, Jens Nickel, Guy Raedersdorf

Design staff: Fon Gresberts, Paul Goossens, Luc Lenvmens, Karel Wairaven

Editorial secretariat: Hedwig Hennekens (secretariat@segment.ru)

Graphic design / DTP: Ton Gulkers, Gel Dols

Managing Director / Publisher: Paul Snakkers

Marketing: Margnet Debei (m.debei @segmentini)

Subscriptions: Elektor Becaronics (Publishing).

Regus Brandord, 1000 Great West Road, Brandord TW8 9HH, England.

Tel (+44)(0) 208 261 4509, fac (+44)(0) 208 261 4447

Internet; www.elekton-electronics.co.uk

Emilia subscriptions@lefelope-pleason-account

Rates and terms are given on the Subscription Order Form

Head Office: Segment b.v. RO. Box 75 NL-6190-AB Beek The Netherlands Telephone: (+31) 46 4389444, Fax: (+31) 46 4370161

Distribution: Seymour, 86: Newman Street, London WIP 3LD, England

UK Advertising: Huson International Media, Cambridge House, Gogmore Lane,

Chertsey, Surrey KT16/9AP, England, Telephone: +44 (0)1932 564999, Fax: +44 (0)1932 564998

Email: reigar@husonmede.com Internet: www.husonmede.com

Advertising rates and terms available on request.

International Advertising: Klass Caldenhoven, address as Head Office

Email: athementes@eleterov/

Advertising rates and terms available on request.

Copyright Notice

The circuits described in this magazine are for domestic use only. All drawings, photographs, printed circuit board (sybuts, programmed integrated circuits, disks, CD-ROMs, software carriers and district texts published in our books and magazines (other than third-party adventisements) are copyright Segment by and may not be reproduced or paramitted in any form or by any means, including photocopying, standing an recording; in whole or in part without prior written permassion from the Publishers. Such written permassion must also be obtained before any part of this publication is stored in a retrieval system of any nature. Fatent protection may exist in respect of circuits, devices, components etc. described in this magazine. The Publisher does not except reports bility for failing to identify such patential or other protection.

The pubmission of designs or soldes implies permission to the Publishers to affect the cast and design, and to use the contents in other Segment publicators and assistes. The Publishers cannot guarantee to return any material submitted to them.

Disclaimer

Prices and descriptions of publication-related items subject to thange. Emors and omissions evaluded

© Segment b.v. 2005

Printed in the Netherlands









Online price calculation Online ordering Online order tracking Online 24/24H and 7/7D

Interested? Contact us: +32 15 28 16 30 E-mail: euro@eurocircuits.com

www.eurocircuits.com

Verified

- pooling for standard boards
- up to 6 layers
- from 1 to 1000 pieces
- from 4 working days onwards



- technology at the right price
- up to 8 layers
- from 1 to 1000 pieces
- from 3 working days onwards



- your board, our challenge
- up to 20 layers
- from 1 piece onwards
- from 2 working days onwards

6

BitScope Analog + Digital

100MHz Digital Oscilloscope

4 Channel Digital Scope using industry standard BNC probes or analog inputs on the POD connector.

40MS/s Logic Analyzer

8 logic, External Trigger and special purpose inputs to capture digital signals down to 25nS.

Mixed Signal Oscilloscope

True MSO to capture 4 analog waveforms time-aligned with 8 logic using sophisticated cross-triggering on any input.

Real-Time Spectrum Analyzer

See spectra and waveforms of all analog channels in real-time displayed simultaneously.

Advanced Networking Operation

Flexible network connectivity supporting multi-scope operation, remote monitoring and data acquistion.

Integrates with third-party software

Use supplied drivers and interfaces to build custom test and measurement and data acquisition solutions.

PC Oscilloscopes & Analyzers

See the big picture with BitScope Multichannel Mixed Signal Oscilloscopes



Turn your PC into an expandable multichannel scope solution.

Never run out of channels again. Whether debugging an embedded 3 phase motor controller or monitoring a full scale synchrotron, BitScope is the right solution.

With 4 independent analog and 8 synchronized logic channels, BitScope is ideal in situations where a dual channel scope is simply not enough. Consider many modern embedded systems, component video, 3D robotics, DSP process control and automotive systems. All frequently require more than 2 analog channels and several synchronized timing channels to really see the big picture.

Perhaps 4 + 8 channels is not enough? No problem, build a scope array accessible from the PC via your network and synchronized via BitScope's trigger bus or logic inputs. "Smart POD" connected active probes and multiple software options complete the picture for the perfect low cost high performance multichannel test and debug solution!



BitScope

Standard 1M/20pF BNC Inputs

200µV-200V/div vertical scale Software select AC/DC coupling Switchable 50 ohm termination x1 to x100 or differential probes:

BitScope Smart POD probe connector

8 logic channels, cross-triggering 4 additional analog inputs on POD Async:serial I/O for external control Trigger bus for multi-scope sync


Ethernet Connectivity

High speed binary data transmission Standard network protocols (UDP/IP) Internet addressable device

Expandable and Programmable

Simple ASCII Protocol BitScope Scripting Language Add active probes and devices

 BitScope and your PC provide an array of Virtual Instruments














 


BitScope's integrated design uses standard oscilloscope probes and a growing range of custom probes to provide functionality equal to instruments many times the price.

BitScope plugs into third party software tools and has an open API for user programming and custom data acquisition.

BitScope DSO software for Windows and Linux

www.bitscope.com

 

Direct toner method

Hi Jan - I've been a subscriber for many years (I think since 1985) and I keep finding your magazine interesting and useful. However, I do have one suggestion regarding PCBs. Not living in a country in which have offices, I've always had problems with getting PCBs, since ordering from abroad is kind of complicated in my country (okay, I understand we're in the EU, but still...). Recently, I discovered a technology for making my own PCBs, which is very useful and quick: the toner transfer technique. Maybe you've heard of it basically it's just printing PCB to photo paper using a laser printer, transfer toner to the board using an ironer or laminator, etch and voila! Okay, choosing the right paper is difficult, but once you've figured it out, you have a finished PCB in less than 10 minutes!

This must be useful info for all home hobbyists, so maybe you should consider publishing a detailed article about it. Here is one link about the method:

www.fullnet.com/u/tomg/ gooleepc.htm

There is also a dedicated group on Yahoo:

http://groups.yahoo.com/gr oup/Homebrew PCBs/

For your information!

Pavel Veider (Slovenia)

Thanks Pavel for the interesting email which are happy to reproduce here for the benefit of other readers. It's no coincidence as this issue is on 'All Things PCB'.

Horn loudspeaker turns 16

Dear Editor - we have constructed a matching pair of horn loudspeakers as published in Elektor Electronics magazine in May 1990 (pages 20-23). We have recently tested the speakers with a frequency analyser and found the low frequencies roll off at around 315 Hz, somewhat higher than expected and higher than the response indicated in Figure 2 of the article. Are you able to provide clarification of the following:

1. In Fig. 2 of the article there are two response curves. Which one is the measured response of this unit? What is the other curve for? This figure isn't referred to in the article.


2. Have there been any modifications or amendments to this design submitted or published that might answer our problem with lack of low frequency response? Any suggestions or information would be very much appreciated.

Julian Weir (New Zealand)

We do not know how you did the measurement, but this design of a horn loudspeaker must give a low frequency roll off at about 50 Hz. The measurement in Figure 2 shows: (a) the frequency response of the complete unit at a distance of 1 m, with superimposed a secand curve showing the pressure right in front of the horn. You should add these two to get an impression of the total frequency response. Drawing (b) shows the impedance curve of the complete loudspeaker system.

With a low frequency roll off at about 300 Hz you should hear no bass response at all when playing music and we cannot imagine that's the case. Something else must be wrong, for instance a wrong value for a filter component (the coil in series with the woofer). Also, the choice of the right woofer is important. I assume you have not used the original McFarlow speakers, since they are not available anymore. You have to use a speaker with the same Thiele-Small parameters, otherwise the coupling of the speaker to the horn will not be correct and you do not get enough bass output.

(Mr Weir replies) The horn response was measured at 1 m from the front (on-axis) and at differing heights (in front of the mouth, and in front of the drivers etc.) with a receiving level of about 80-90 dB. I have definitely heard a distinct lack of low frequencies: while there are some low frequencies, they are rather quiet. They can be heard when I place my head inside the opening. The horns were built by my dad about 9 years ago. We will have a look at the filter electronics first to eliminate if that is the problem, then look into the drivers themselves. You are right, dad did not put the same McFarlow drivers in. He put in a 60 W (rms) 10" driver from Altronics Australia, as per the following web site: www.altronics.com.au/index. asp?area=item&id=C3065 He would have researched the specs of the McFarlow and found one that he thought would have matched at the time, but we will have a re-look into that too. Do you have any thoughts off-hand that you can give regarding the suitability of this driver compared to the McFarlows originally specified? I take it there have been no revisions of the design or discussions/commentaries on the final speaker? Many thank for you help. It is very much appreciated.

 

Corrections & Updates

Simple Rechargeable AA Cell Characteriser April 2006, p. 28-31, 050394-1

Resistor R3 is not shown in the circuit diagram. R3 is a 10-k pull-up resistor between the gate of T1 and the +5 V supply rail. It is present on the printed circuit board. R4 is a leaded component, not an SMD as suggested by the parts list.

Just after printing this article a problem occurred with the software supplied by the author. For this software to run, the user's PC must have Microsoft Java installed. For various reasons Microsoft is no longer allowed to use the name 'Java' and the relevant program is no longer found on the Internet (but Google for MSJAVx86.exe and you will still be able to find it).

No problems are usually encountered on PCs running Windows 95 or 98 as MS-Java will be resident and the program AA-CELL msjava. ZIP may be run without problems. The author has adapted his software to avoid the use of MS-Java. This requires changes to the installation. The following steps are recommended.

1. Install the 1-Wire divers including .NET support (note when to actually connect the circuit, this is indicated during the installation; start without the circuit connected to the USB).

http://files.dalsemi.com/auto_id/licensed/install_1_wire_drivers_v400.msi

2. Download Microsoft .NET Framework 2.0 redistributible package and install it (heft file at 23 Mbytes) http://www.microsoft.com/downloads/details.aspx?familyid=0856EACB-4362-4B0D-8EDD-AAB15C5E04F5&displaylang=en

3. Download Microsoft Visual J# 2.0 Redistributable Package and install it.

http://www.microsoft.com/downloads/details.aspx?familyid=F72C74B3-ED0E-4AF8-AE63-2F0E42501BE1&displaylang=en

4. Download the project software (AA-CELL dotnet.zip) from the Elektor website and install it.

Start → Programs → 1-Wire Drivers → start Default 1-Wire Net and select the DS9490 (USB) adapter.

6. Start → Programs → Maxim Integrated Products → AAcellchar

That completes the modified installation procedure.

In respect of electrical parameters the loudspeaker your dad used differs considerably from the one we specified for the project. Many readers asked us for a replacement type when McFarlow stopped the production, but it is pretty hard to find a similar type. The least we can do is give the main specs:

 $Q_{15} = 0.35$

 $Q_{MS} = 2.6$

 $Q_{ES} = 0.4$ $V_{AS} = 661$

 $F_S = 40 \text{ Hz}$

The main things that must come close to the original specs, are QTS and VAS.

By the way, no corrections were published for this project. It was a successful design, not really high fidelity; but very good given its relatively low building and components costs.

Veroboard and just connected the Avit data lines direct to the microcontroller pins. I used the Avit 5V and ground lines to power the R8C from the PC, again just a direct connection. The system worked first time, the only problem I had was when I tried to download a second program and found that I needed to check the box marked "erase before programming" (or words to that effect) in the FDT software. I also have a 4x20 character LCD display connected

Thanks John and also Adrian Verity of Avit Research; there's another fine example of how quickly solutions can be found via our online Forum.

Energy recovery

Dear Editor — I was interested to read in 'Design Tips',

Elektor Electronics, March
2006, the piece submitted by

Peter Lay, describing how to
recover energy from a relay
coil during switch off.

Many years I ago performed (very amateurish) experiments

using this technique in a motor circuit. The idea was to get an idea of how much energy could be

recovered from a battery driven motor during its normal operation under pulse width speed control.

Obviously the energy recovered would be on-going as the motor was running. My circuit was almost identical to that described by Mr. Lay, with the exception that the motor was in place of the relay shown. The transistor was of course driven by a variable frequency square wave.

I was able to demonstrate an amount of energy recovered by the voltage appearing on the capacitor, although this did not indicate a very large amount. However my limited knowledge and practical skills prevented me pursuing the experiments. Would there be any advantage in this sort of idea in attempts to extend the life between charges of batteries driving motors? (my thoughts at the time were of electric vehicles). Perhaps some of your readers could pass some comments?

David Clenton (UK)

Suggestions and comments invited, please send them to the Editor.

R8C Tom Thumb connects to Avit Easy USB

Dear Jan — regarding your query about connecting the Avit USB cable to the R8C/Renesas board. I had already purchased two Avit cables at the special offer price and decided to use one with my R8C board when it arrived. I mounted the small R8C board on a piece of

which
seems to work
ok, though I didn't try
using the backlight as I don't
know how many mA I have
left!

I may install a switch in the power line so I don't have to switch off the PC or unplug the cable when I need to power down the R8C. So far so good!

Keep these excellent projects coming!

John Bishop (UK).

MailBox Terms

 Publication of reader's correspondence is at the discretion of the Editor.

Viewpoints expressed by correspondents are not necessarily
those of the Editor or Publisher.

 Correspondence may be

translated or edited for length, clarity and style.

When replying to Mallbox.
 correspondence,

please quote Issue number.

- Please send your MailBox

correspondence to:

editor@elektor-electronics.co.uk or Elektor Electronics, The Editor, 1000 Great West Road.

Brentford TW8 9HH, England.

New dimension to solid state lighting applications!


OPTEK Technology has introduced one of the industry's brightest single-source packaged visible LED assemblies. Designated the OPTEK Lednium Series, the 10-W package offers a full 1200 viewing angle for its array of amber, blue, green, red, or white LEDs.

OPTEK's Lednium Series devices are claimed to achieve an output

of up to 330 lumens with nine 1-wait LEDs mounted in an anodized aluminum package just 1.3 inches square, with a board mounted profile of less than 0.5 inch.

Conventionally-packaged LED arrays with comparable light output often require as many as 12 1-W LEDs in configurations up to 8 inches in diameter, which typically consume more power.

 The wide viewing angle and increased brightness are crit-



ical features for lighting design engineers as they begin to incorporate solid state light sources (LEDs) into applications such as automotive interior and exterior lighting, indoor and outdoor electronic signage and displays, as well as architectural lighting and general lighting applications.

The OPTEK Lednium Series LED assemblies also provide different parallel-serial connections that enable the operation of 3, 6 or

all 9 of the mounted LEDs, enabling design engineers to vary the light output and power consumption.

OPTEK's Lednium Series devices are available in amber (595 nm, 330 lm); blue (467 nm, 60 lm); green (524 nm, 290 lm); red (624 nm, 247 lm); and white (250 lm). All colours feature a full 120° viewing angle in water clear lenses. In development are other visible, as well as UV and IR wavelengths and package configurations.

DC forward current is 1.05 A, with peak pulsed forward current of 3 A. Typical forward voltage characteristics range from 6.3 V to 9.25 V (colourdependent), and reverse voltage for all devices is 15 V.

Maximum allowable junction temperature is 130°C (average thermal resistance junction to-board is 5°C/W), and the

operating temperature range for the device is -50°C to +80°C.

OPTEK Lednium Series products are stocked by OPTEK's distributors in the Americas, Europe and Asia.

OPTEK Technology, 1645 Wallace Dr., Carrollton, TX, 75006, USA. Tel. (+1) 972-323-2200. www.optekinc.com/led_prl.asp.


(057) [1-4]

Lascar for design and manufacture

Lascar Electronics Ltd. Now offers a custom design and manufacturing service that provides its customers with an effective route to take projects from conception to market in a timely and cost-effective manner.

Lascar's experienced engineering design and development team have expertise in many aspects of electronics, mechanical and software design — providing the flexibility to engage all elements of the design process. This includes the design and development of custom LCD and LED displays, circuit design, PCB layout, 3D modelling and writing PIC and Windows based software.

 While full control of design and manufacture is retained in the



UK, Lascar's service offers a straightforward route to Far-Eastern manufacture and the cost benefits associated with them. Many types of manufacturing techniques are employed including COB, COG, SM, Plastic Injection Moulding, Metal Casting and Sheet Metal fabrication processes. All manufacturing processes undertaken by Lascar are carried out to BS ISO 9001:2000.

(657111-5)

Lascar Electronics Limited,
Module Hose, Whiteparish,
Salisbury, Wiltshire SP5 2SJ.
Tel. (+44) (0)1794 884567,
Fax (+44) (0)1794 884616.
Internet:
www.lascarelectronics.com

Learn to program AVR microcontrollers in C



If you have always wanted to learn C programming for a microcontroller but have struggled with books and manuals on the subject, then this kit could be what you have been waiting for. The kit is based on our popular E-blocksTM system for rapid prototyping and learning. The concept of E-blocks is simple: each E-block consists of a block of electronics you would find in an electronic system: a processor board, a switch board, keypad, USB interface etc. To make an electronic system you simply snap the appropriate E-blocks boards together and develop the software to make the system run to the specification. Whilst developing the hardware system is relatively easy, the software can be the difficult part - and that's where the C for AVR microcontrollers CD ROM comes in.

The C for AVR Microcontrollers CD ROM fulfils several needs of those wanting to learn C programming for the AVR and for those who want to develop projects.


Firstly the CD ROM includes a full course in C programming. The course is screen-based and makes full use of the computer as a medium for learning: it contains a series of computer simucode. This is a great way of learning C, because the simula-

their status as an input or an output, and their logic level - where logic 1 is

program or step through it lineby-line and see the logic levels of the I/O lines change.

Secondly the CD contains a copy of the AVR Studio development environment which has a fully working licence-free C compiler embedded into it. You can access AVR studio - pre-loaded with the relevant program directly from the CD by clicking on hyperlinks in the tutorials. The learning methodology is really complete: you read the text onscreen, view the program working on the Virtual C machine, load AVR studio, and then compile the program and send it to your hardware.

Lastly the hardware contains an Atmel AVR programming board with In System Programming module a board containing eight LEDs, a board containing 8 switches, and a 2-line 16-character LCD board. This is most of what you need to get started and the AVR programming board is compatible with the whole range of additional Eblocks boards should you want a keypad, prototype board, IrDA board or other peripheral.

 

tions allow you to see the effects on the AVR device as each line of C code is executed, and you can easily understand what is going on. The screen image shows the Virtual C machine. Referring to the diagram: the top part shows you the C program under discussion, underneath that in cyan you can see the variables, which change as the program runs, below that you can see the port A and B I/O lines with arrows that show

And Greene Aredieres This down and trombie:

indicated by a red 'LED'. Below the I/O lines are the critical reaisters: the data direction registers and their hex input and output values. Controls on the right hand side allow you to run the

The first part of the prigramity fertier dawn the impression

> The Elektor Electronics Easy AVR Kit is available now from the Elektor SHOP, check out details and price of

that are as as are are the mark? the age of the first and

I - dayley a majerne and their Wise

process progress to with the process to me was all the parties of many terrains the progress.

The little was bath if the warm

Commercial Contraction

www.elektor-electronics.co.uk

(047111-4)

Network Cable Analyser gets an intelligence boost!

Peak Electronic Design Limited have launched an enhanced version of their Network Cable Analyser the Atlas IT (model UTP05), designed and made in the UK.

The Atlas IT has always had the unique ability to analyse many types of RJ45 based network cabling, including Ethernet, Token Ring, Patch cables and Crossover Cables. The connection pattern of the cables is automatically recognised and displayed on the unit's display as well as confirmation of the full connection pattern.

Now the Atlas IT has been enhanced with cable defintions of 8 more cable types, including Cisco terminal cables, Linn Audio network cables, Ethernet Economisers, 4 line crossovers, voice/data cables and many more. Additionally, for the first time ever, the Atlas IT can now recognise the cable type even if there are connection faults (such as missing connections, swapped lines or other errors). It



will display the cable type and highlight any lines that have errors.

The Atlas IT hardware has had a boost too, now it can cope with connection to live comms systems and even withstand the high telephone ring voltages (upto 80 V) associated with mixed voice and data cabling. Using the Atlas IT could not be easier, connect the main unit at one end of your cable run and the miniature (18 mm cube) ter-

minator at the other end. For socket testing you can use the supplied mini patch leads too. Press the test button and after a few seconds the results of the analysis are displayed on the clear alphanumeric display. If you use the unique Identified Terminators, the Atlas IT will identify the cable run for you too, allowing the easy testing and identification of many cable runs (upto 24) without having to make lots of trips to swap termi-

nators

The Atlas IT will automatically power down after a period of inactivity, so you'll never forget to switch it off. Measuring just 103mm x 70mm x 20mm, the Atlas IT fits in the palm of your hand or could even happily dangle from a network socket! When it's not in use, it can be stored safe and sound in the supplied custom machined carry case along with your accessories, terminators, cables and a spare battery.

The Atlas IT is available from many distributors including Farnell and Maplin as well as directly from the manufacturer for £89.00 fully inclusive of UK delivery and VAT.


Peak Electronic Design Ltd.
Atlas House,
Harpur Hill Business Park,
Buxton, Derbyshire SK17 9JL.
Tel. 01298 70012,
Fax. 01298 70046.
www.peakelec.co.uk

(057111-2)

Coldfire suite embraces Freescale MCF5207 and MCF5208

Crossware has enhanced its ColdFire® Development Suite by adding support for Freescale Semiconductor's MCF5207 and MCF5208 ColdFire microprocessors. This support includes a utility that allows programmers to integrate Freescale's dBug ROM monitor software instantly into the Crossware development environment allowing developers to be debugging this firmware within minutes.

 In addition, Crossware has added support for 64-bit integer arithmetic to its ColdFire C compiler as this is becoming an essential requirement for modern embedded systems. 64-bit integer arithmetic is used extensively, for instance, for check-sum calculations in Freescale's compressed audio reference software.



The MCF5208 is a high speed microprocessor based on the V2 ColdFire Core. It includes a wide range of connectivity peripherals, an integrated DDR SDRAM memory controller and an enhanced multiply and accumulate unit (eMAC). Distributed clocking allows the on-chip modules to be separately enabled and disabled which, in conjunc-

tion with a low power clock divider, makes a low power implementation particularly practical.

Many developers wish to use Freescale's dBug ROM monitor software as a starting point for their own application. This is particularly easy with the lastest Crossware release because a new utility allows the complete

dBug source tree and build settings to be imported, in a matter of seconds, into the Crossware graphical development environment. Developers can complete a build and download cycle within minutes of unzipping the Freescale files. Additionally Crossware's FireFly USB BDM (background debug mode) interface allows rapid download of the firmware into flash.

Crossware's ColdFire Development Suite allows developers to create, build and debug their ColdFire programs both with and without hardware. The totally integrated, user-friendly environment accelerates the development process and significantly reduces new product time-to-market.

(067111-7)

www.crossware.com

Dual-tuner DVB-T PCI Express solution for the living room

Micronas offers PC OEMs and system integrators production-ready DVB-T design for home theaters.

At CeBlt 2006 Micronas launched the MicPythonTM2H-X, a dual-tuner DVB-T PCI Express® card for home theater solutions. A universal antenna connection lets the user watch and record analogue, digital, and future HDTV signals without worrying about complicated cable connections or even switching antennas. MicPython 2H-X works with Windows XP Media Center and other third-party applications, guaranteeing easeof-use. Micronas will showcase MicPython 2HX for the first time at CeBIT in Hanover, Germany from March 9 to 15, 2006.

Home theatre systems must be small and unobtrusive, while delivering picture quality good enough for ever larger screens. MicPython 2H-X's small size and



low power requirements mean the system enclosure is small and quiet. The company's extensive television expertise went into the design to ensure best picture quality. MicPython 2H-X uses the DRX 3975D demodulator, the nGene® APB 7202A PCI Express controller, both from

Micronas, and a MicroTuner™ MT2060 digital TV tuner from Microtune.

Micronas' nGene dual-channel multimedia PCI Express controller delivers the bandwidth needed for two TV channels up to HD, all in a single slot – eliminating potential bottlenecks that may occur with two slats required by conventional PCI. nGene is certified by the PCI-SIG, the industry standard body for PCI Express technology, to be PCI Express 1.0a compliant. This certification guarantees that MicPython 2H-X is compatible with a wide variety of PC motherboards offering PCI Express x1 slots.

MicPython 2H-X and the ATSC-based MicViperTM2H-X are the first members of a family of nGene-based reference designs supported by a common software model. The common software support across the family makes it easy to design world-standard products. MicPython 2H-X and MicViper 2H-X are complete, production-ready solutions. Both reference design kits are available now.

(047111-8)

www.micornas.com; www.dvb.org

TMD Technologies' guided transition to lead-free

Specialist UK electronics manufacturing company TMD Technologies Ltd (TMD) has appointed Dr Shubo Gao to implement the transition from the company's traditional to latest environmentally-friendly lead free soldering processes.

The new project is being undertaken as a Knowledge Transfer Partnership (KTP) between TMD and CRDM Research (Centre for Rapid Design & Manufacture), a Department of the Faculty of Technology, Buckinghamshire Chiltern University College (BCUC). The programme is funded by the Department of Trade and Industry.

Dr Shubo Gao, who has a degree in Electronics Engineering and 10 years of industrial experience in electronics assembly, will be responsible for the detailed planning and execution of the project, and will be based mainly at TMD's manufacturing facility in Hayes, West London, near Heathrow Airport.

She will be working under the



guidance of both TMD and David Jacobson, Professor of Materials at CRDM Research, BCUC, who is responsible for overall supervision of the programme.

This important development is aimed at meeting the require-


ments of new 'green' EU legislation that bans the use of lead in soldered products, and which comes into force in July of this year. It will ensure that TMD's future manufacturing methods will be compatible with all components from the European Market tailored for lead free use - as well as those from other world markets that are currently not suited to lead free processes. The in-house programme will include the re-training of relevant TMD personnel in all aspects of lead free soldering technology. TMD Ltd. designs and manufactures specialised transmitters for radar and electronic warfare applications, power supplies and microwave tubes. It also produces a range of commercial amplifiers for EMC testing, medical and scientific applications.

(667111-3)

TMD Technologies Ltd., Unit 3, Swallowfield Way, Hayes, Middlesex, UB3 1DQ, UK. Tel: (+44) (0)20 8573 5555. www.tmd.co.uk

International R8C 1st Prize: your design goes in

The R8C Service Page and the R8C Forum topic on our website clearly show that the 16-bit Tom Thumb Starter Kit from the February 2006 issue is a great source of inspiration for readers' own experiments and applications. The free C Booklet supplied with the March 2006 issue was a further stimulus by presenting C programming for the little board. A great time, we thought, to launch a design competition and give the R8C project a further boost.

 

Microcontrollers are no longer the exclusive domain of professional designers and programmers. We estimate that about half the readership of Elektor Electronics are conversant with microcontrollers, and the percentage is sure to rise with the availability of our Tom Thumb R8C Starter Kit (costing just £ 8.30 plus P&P).

A 16-bit controller with great connectivity for peripherals, the R8C/13 from Renesas offers lots of possibilities for interesting applications that are easily thought of as going into mass produced commercial products. After all, millions of R8C micros are in daily use all over the world, mostly in consumer electronic equipment and automobile electronics. This circumstance really triggered us to organise a design competition around our successful R8C micro and offer full commercialisation of the winning entry as the first prize. The lucky winner will receive royalties over the turnover realised by the product. However there are lots of other great prizes to be won!

The assignment

Develop a killer application for the R8C/13 microcontroller introduced in the January and February 2006 issues of Elektor Electronics. Both the Tom Thumb module (February 2006) and the R8C Prototyping Board (March 2006) may be used, but really any hardware configuration around the R8C is fine. The only condition is that a microcontroller from the R8C series is used. There are no limitations or conditions for software tools, although we should add that for a publication of your

design it would be advantageous that freely available tools have been used, i.e., any of the programs on the Starter Kit CD-ROM, or an Elektor free download. This recommendation is made to make sure that ideally the whole R8C community can reproduce your application through the magazine pages or the Elektor website.

What to supply

To participate in the competition, please do not send us hardware or prototypes. Instead, supply the following:

1. A short description of the functionality in Word, RTF or ASCII format.

2. Circuit diagram (excluding the R8C board) on paper by post or by email as a .jpg, .tiff, .eps or Acrobat file.

3. Source code or hex code file(s) of the R8C target software (on diskette or CD if sent by post).

4. Additional documentation you deem essential for an initial appreciation of your project (for example, images).


Where to send it to

Please send your competition entry by email to

editor@elektor-electronics.co.uk

and use R8C competition as the Subject. Automatic sorting will be applied to incoming emails so please copy the subject exactly.

 Design Competition to production! Special Prize As is generally known, genius and lunacy go hand in hand.



Alternatively, send the project by post to

Elektor Electronics R8C Competition Regus Brentford 1000, Great West Road Brentford TW8 9HH United Kingdom

The Jury

The Jury consists of Elektor designers and editors, Mr Burkhard Kainka and Mr Günther Ewald (the authors of the January 2006 article) as well as several other R8C specialists and project contributors active in our R8C Forum and on our R8C Service pages. Mat Heffels, our International Editor in Chief, has been appointed Head of the Jury.

Winners

The winners of the competition will be announced in the **November 2006** issue. The decision of the Jury in respect of prize-winning entries is not open to discussion. The competition is not open to employees of Glyn, Renesas, Elektor Electronics, or publishing houses with a business relation to Segment b.v.

Publications

By participating in this competition, you agree to publication, in original or edited form, of all material you have As is generally known, genius and lunacy go hand in hand. Consequently, not all competition entries can be measured with the same yardstick regarding real-life value, efficacy and the extent to which the project is 'finished'. That's why a special prize is offered for the most creative project we receive for this competition. The prize is also as creative as it gets: An E-Blocks Easy AVR Starter Kit from Matrix Multimedia with a value of £ 250 and a

Valve Experimenters
Kit from
AK-Modul-Bus with a
value of £ 65!



supplied in relation to the entry. The Jury decides which projects are published in *Elektor Electronics* magazine, and which on our website(s). In addition to a prize, a remuneration of 75 pounds or 100 euros is paid per published page (assuming an article size of five pages, that's £ 375 or € 500).

1st Prize

The First Prize is awarded to the R8C application that's best suited to production, marketing and sale through the Elektor SHOP (magazine and web) and/or

Elektor's business partners, within the Publishers' abilities. The prize consists of royalty payments to the amount of 10% (ten percent) of the turnover realised by the winning project.




2nd Prize

TASKING M16C & R8C/Tiny Software Development Tools v3.1

Value: £ 2239 (3242 €)

 A complete software development toolset from Tasking, including Altium's Viper Compiler technology. The ultimate for M16C and R8C software builders. Info: www.tasking.com/products/8_16_bit/M16C/Altium Europe GmbH www.altium.com



3rd Prize

EAGLE Professional Value: £ 975 (1392 €)

Complete design suite for circuit board design (up to 1.6 m x 1.6 m, 16 signal layers, 99 schematics pages). Product: 1 User, Layout Editor, Schematics Module, Autorouter Module.

CadSoft Computer GmbH www.cadsoft.com



4th Prize

EAGLE Standard

Value: £ 480 (696 €)
Complete package for PCB design (1 Eurocard, 4 signal

layers, 99 schematics pages).

Product: 1 User, Layout-Editor, Schematics Module,

Autorouter Module.

CadSoft Computer GmbH www.cadsoft.com

5th Prize

Money prize: £ 350 (500 €)


The fifth prize is 350 pounds (or 500 euros) sponsored by IPS-Pressevertrieb GmbH www.ips-pressevertrieb.de

6th Prize

Elektor Versatile FPGA Module &

Prototyping Board Value: £ 324 (469 €)

 Versatile FPGA
Module with programming interface, cable and
connectors, and
the FPGA
Prototyping
Board.
Info:



Elektor Electronics March 2006.

Elektor Electronics (Publishing) www.elektor-electronics.co.uk

7th Prize

ME 2-channel PocketScope DS1M12 with TESTEC double MF 312-2 probe kit. Value: £ 259 (374 €)



A mobile USB Mini Scope / Waveform Generator including 2 x TT-MF 312 test probe for 20 / 250MHz.

Reichelt Elektronik www.reichelt.de

8th Prize

DK51 – Complete Starter Kit for SC11 and SC13 IPC@CHIP Value: £ 219 (312 €)

Comprehensive
Starter Kit for
your IPC@CHIPapplication with
DK50 Development Board,
SC13 IEC,
CoDeSys CD,
Borland CD,
serial cable and
power supply.
Beck-IPC
www.beck-

ipc.com



9th Prize

USB Logic Analyser ME ANT 6 Value: £ 199 (279 €)



Mobile, compact 8-channel USB Logic Analyser, ideal for mobile use in combination with a Notebook PC.

Meilhaus Electronic GmbH www.meilhaus.de



10th Prize

MicroPLC Hardware Value: £ 179 (257 €)

Kanis and Cadsoft's EAGLE-programmable PLC. Ready-to-use board with detailed documentation, power supply and accessories.

Design Bureau W. Kanis GmbH www.kanis.de


11th Prize

PCB manufacturing Value: £ 140 (200 €)

Voucher to above value for a PCB manufacturing order placed with PCB

placed with PCB-POOL.

Beta LAYOUT www.pcb-pool.com

 

12th Prize

PCB manufacturing Value: £ 140 (200 €)

One off discount of the above amount (incl. VAT) on an online 'Plot&Go' or 'Verified' order.

Eurocircuits Byba www.eurocircuits.com

13th and 14th Prize

Wireless audio modules WA-TX-01 and WA-RX-01A Value: £ 99



(140 €) each

These modules (transmitter and receiver) from Circuit Design enable a high quality wireless link to be created (e.g. for a cordless microphone).

Circuit Design www.circuitdesign.de

15th through 24th Prize

Renesas E8 Emulator Value: £89 (128 €) each

The E8 enables serial synchronous debugging independent of quartz frequency and monitor.

Glyn www.glyn.com

25th Prize

Alitum Live Design Evaluation Kit Value: £ 79 (115 €)

The Altium Designer LiveDesign Evaluation Kit contains the LiveDesign Evaluation Board with FPGA (Altera Cyclone or Xilinx Spartan-3) and the Altium Designer Software (unrestricted 30-day licence).

Altium Europe www.altium.com

26th and 27th Prize

I/O Warrior
Starter Kit
Value: £ 39
(57 €) each
Kit for IO Warrior
Evaluation Board
including software

Kit for IO Warrior Evaluation Board including software for Win, Mac, and Linux.

Code Mercenaries Hardware and Software www.codemercs.com



28th, 29th and 30th Prize

Elektor Electronics Voucher Value: £ 35 (50 €)

Valid for all SHOP products supplied by the Publishers like books, CDs, ready-made modules, kits, software items and circuit boards.

Elektor Electronics (Publishing)
www.elektor-electronics.co.uk

(350000-1)

Lead-free? No

Felix Meckmann and Jens Nickel

The use of lead-containing solders will be severely restricted from the beginning of July 2006. This has far-reaching consequences, especially with regard to automated soldering.

We take a closer look.

Electronics is playing an ever-increasing role in all areas of daily life. As a consequence the number of discarded and redundant electronic appliances and components is continuously on the rise. The EU member states together generate over six million tonnes of electronic waste per year. Furthermore, many electronic and electrical appliances contain toxic substances such as lead, mercury and cadmium.

In 2002 the European Parliament and the Council of the European Union, representing the national governments, enacted two directives, 2002/95/EC and 2002/96/EC, which became known as 'RoHS' and 'WEEE' [1][2]. The directive on 'Waste Electrical and Electronic Equipment' puts liability on manufacturers to mark their appliances, to take old appliances back, recy-



cle them as far as possible and prepare the residual waste for disposal [3].

The ban on the use of certain specified hazardous substances in the manufacture of new appliances will avoid damage to the environment and human health, and questions of disposal methods will arise. To this end the RoHS ('restriction on the use of certain hazardous substances in electrical and electronic equipment') regulations have been adopted, which restrict the use of specified hazardous substances. The regulations cover not only lead, which is an important constituent of solder and which is responsible to a large extent for its properties, but also mercury, cadmium and other substances used in such things as cables and enclosures. The various EU member states are transposing the directives into national law.

18

roblem

Soldering in the RoHS era



The one part in one thousand limit

July 1st 2006 is a key date for developers and manufacturers of electronic equipment: this is when the ban on hazardous substances comes into effect. From this point it will no longer be permitted to bring 'onto the market' any electrical or electronic appliance which is not RoHS compliant, that is, which contains any of the proscribed substances. In order to make the purification and analysis of materials technically and economically feasible, thresholds have been set below which a material will be considered 'free' from a particular substance: for example, a solder containing less than 0.1 % lead by weight will be deemed 'lead-free' for the purposes of RoHS. These thresholds apply for all 'homogeneous' materials from which an appliance might be constructed. ('Homo-

geneous' means that the material can only be further decomposed by chemical, rather than mechanical means.) Examples are the metal used for an enclosure, copper printed circuit board tracks, solder and so on. It is therefore necessary that not only the equipment, but also the boards and components used in it, are RoHS compliant. If, for example, the solder used contains more than the maximum permissible level of lead, the whole appliance may no longer legally be sold. Non-compliant components and printed circuit boards may, however, be used after 1 July 2006 as spare parts for, or for repairing appliances which were sold before the critical date. Lead-containing solders may also be used in servers and storage systems until 2010, as well as in various types of telecommunication equipment. There is also a comprehensive exemption for military equipment.

The regulations are principally aimed at the manufacturers of electrical and electronic devices, but inevitably all parties in the chain of production and sale are affected to some extent. New lead-free components and manufacturing processes must be made available. Those responsible for development and manufacture will have new challenges in coping with the regulations. End users, on the other hand, will see little change. Building a circuit or device purely for your own use does not constitute bringing it 'onto the market' and so in this case old components and lead-containing solders can still be used.

Purchase and design

The RoHS directive has a double effect on the choice of components, since assembly houses and manufacturers may no longer use lead-containing solders, which have a particularly low melting point (183 °C). This means that, in general, higher soldering temperatures are necessary. Unfortunately it is not possible to deduce from the fact that a component is declared as 'RoHS compliant' that it can withstand higher soldering temperatures! RoHS compliance means only that, for example, the coating on the leads of a component is lead-free tin. Critical components include, for example, electrolytic capacitors, devices in BGA (ball grid array) packages, and SMD connectors. Caution should be exercised when purchasing new versions of components. More on this problem can be found on distributors' websites [4][5][6] (see Figure 1).

In a mass production environment a complete changeover for all component types in a single step is thought to be the best way to proceed. This of course demands considerable research into new components, redesigns and experimentation with soldering processes. In this regard it is possible to learn from the experiences of others through the formation of industrial associations and groups. The ZVEI (Central Association of the German Electrical and Electronic Engineering Industry) has published a guide to lead-free soldering, available on the Internet as a free download [7].



Figure 1. Many component distributors have set up special RoHS pages.

 


Figure 2. The formation of solder bridges can be avoided by the use of an inert atmosphere.

 


Figure 3. The porous appearance of the surface of a lead-free soldered joint may seem odd at first.

In general significant changes to printed circuit board layout, such as increasing the size of solder pads and increasing the distances between copper areas, are not required. Larger components and larger tracks must however be provided with thermal pads for optimal soldering.

Wave soldering

In industry through-hole (TH) components are most frequently soldered using a wave soldering process. Here the printed circuit board is passed over a solder bath in which a wave is created using nozzles.

If it is not desired to completely replace soldering equipment in the switchover to a lead-free process, modifications will be required to existing equipment. The reservoir and pump systems in new equipment are already supplied with surfaces coated so that they are capable of withstanding the more aggressive lead-free alloys; older equipment must be likewise modified.

When lead is substituted by other metals with a higher melting point, the soldering temperature must increase. Whereas until now temperatures of around 230 °C have been adequate, solder baths must now run at temperatures of up to 260 °C. In general the preheat temperature now plays a more important role: large components, with their higher heat capacity, must be checked and adequately heated in order to avoid failure or damage.

There is a plethora of solder alloys available on the market. In general a SnAgCu (tin-silver-copper) alloy, with a melfing point of 217 °C, is the most popular and there is already plenty of experience with it. It avoids problems such as whisker formation which can occur with pure tin alloys. These whiskers are threads of solder forming from the soldered points which can unfortunately cause unwanted short circuits.

When using lead-free alloys the contents of the solder bath must be continuously monitored by taking samples, since there is a tendency for the proportion of copper to increase. When this reaches a critical level the solder can flow too readily, leading to unsatisfactory results. Depending to the results of the tests, it is possible to add tin-silver alloy, pure tin, or tin-silver-copper alloy to the solder in the both.


Reflow soldering

As in the case of wave soldering, reflow ovens (see box) also require modification or replacement by new equipment. The modifications generally include a powerful heater system and improved thermal insulation, in accordance with the higher temperatures involved in the process. Solder bridges must be watched out for: these arise from increased oxidation of the solder and can be prevented by the use of an inert atmosphere (see Figure 2). In mass production the use of an inert atmosphere is essential.

The established manufacturers offer a selection of leadfree solder pastes. When experimenting it is possible to use a standard lead-free solder temperature profile, which will, as a rule, give good results for 90 % of components. The number of available temperature profiles can be rather large, depending to a significant extent on the product range.

Reflow soldering

Although most 'normal' SMD components can still be soldered manually using a fine soldering iron bit and fine solder, components in BGA, CSP (chip scale package) and similar packages can still only be soldered by machine. The so-called reflow process is a reliable method. In this process a solder paste is spread onto the pads on the printed circuit board where the component will sit: the paste can of course be lead-free. The components are then placed on the printed circuit board so that their connections are embedded into

 

the paste. The connections can now be soldered in a reflow oven. This process takes place in five precisely-controlled steps, called 'phases' (phase 1 to phase 5 in the figure above).

Phase 1 is called the 'preheat phase'. The temperature in the reflow oven is gradually increased to approximately 125 °C. The temperature must rise slowly, as otherwise bubbles can form in the solder paste. Phase 2 is the 'soak phase', or 'activation phase'. Here the temperature is very slowly increased to approximately 175 °C. During this phase the solder paste is activated; the flux changes into its liquid state and flows over the pads.

Once the circuit board and components are 'soaked', phase 3, the 'reflow phase', is entered. The temperature rises relatively quickly to above the melting point of the tin in the paste so that it melts, and the actual soldering takes place. With lead-containing solders the target temperature is about 220 °C to 240 °C; with lead-free solders it must be increased to between 250 °C and 260 °C. In phase 4, the so-called 'dwell phase', the soldering temperature is held constant for a few seconds. The tin particles held within the solder paste melt into one another and displace the other components of the paste. Between the component connections and the pads on the printed circuit board there is now only molten tin, which binds them together. After 15 s to 20 s of dwell, phase 5, the 'cooling phase', is entered and the populated board is gradually cooled to room temperature.

Hand soldering

For repairs and hand soldering the switchover will be straightforward: simply turn up the temperature on the soldering station. Lead-free solders corrode the bit more rapidly, although service companies have reported no significant increase in their use of soldering iron bits. Nevertheless, some manufacturers have brought out new products, such as soldering iron bits made of silver to improve heat conduction. In some cases, such as when a circuit board conducts heat away too rapidly, it is possible to obtain better results by providing additional heating using hot air.

Lead-free soldering takes a little getting used to. The joints are not as bright as those made using lead-containing solder and have a porous surface appearance (Figure 3). Lacking lead, the joints are thicker and harder and have a different shape (Figure 4). A joint that has what would have been an unsatisfactory appearance is thus likely to be perfectly good. This calls for new guidelines for the quality control of soldered joints, as laid down in the paper 'IPC A-610D' by the IPC (formerly the Institute of Interconnecting and Packaging Electronic Circuits) [8].

Outlook


In the medium term the need for two sets of component stores and two sets of soldering stations will disappear.

Niche companies will be set up alongside existing inhouse manufacturers and electronics servicing companies, offering repair facilities as well as materials and manufacturing capacity for appliances falling outside the regulations.

For hobbyists the switchover to a lead-free regime means access to a wide range of new solders, fluxes and components. At the same time a wide range of lead-containing materials will disappear from the market. It is



Figure 4.
Because of the lack of lead, the shape of the joint is different.

 

The Electronics SMD Reflow Soldering Oven

Here at the Elektor Electronics laboratories theory and practice go hand in hand. When we had to solder an FPGA in a BGA package [9], we realised that we needed a reflow oven. Rather than ordering an expensive device, the Elektor Electronics designers had a clever idea: convert their beloved pizza oven into a reflow oven. The team developed a temperature controller circuit based around an AT89C52 microcontroller. Of course, we did not keep the idea a secret

I from our readers [10]: the 'SMD Reflow Soldering Oven' project by Paul Goossens, published in the January 2006 issue, generated enormous interest, as evinced by the dozens of reader letters and e-mails we received. There were many questions about reflow soldering and about our oven design in particular, and many interesting modifications were proposed. One UK reader has even converted his toaster into an SMD soldering oven [11]!

It is easy to alter the temperature profile in the controller to suit lead-free soldering using the 'EDIT' function in the microcontroller program; a good starting point is the set of values given in the box 'Reflow soldering', but this is no substitute for a careful study of device datasheets.

expected, however, that in the short to medium term availability of lead-containing components will remain good, since residual stock will come on to the market.

About the author: Felix Meckmann is marketing manager at Schlafhorst Electronics GmbH. The focus of operations for this firm, based in Germany, is the contract development and manufacture of electronic modules, products

and systems. With 130 staff, the company has been making a positive commitment to lead-free technologies since the beginning of 2004. As well as an SMT production line, wave soldering and selective lead-free soldering are available. The company has to date delivered 200,000 RoHS-compliant modules.

(050045)

Felix Meckmassi Heltomeckmann (Sechlaffaxet-alectran -- da)

Links

- [1] www.europa.eu.int/scadplus/leg/en/lvb/l21210.htm
- [2] http://europa.eu.int/comm/environment/waste/pdf/ fag_weee.pdf
- [3] Elektor Electronics, January 2006, p. 22 and www.elektor-electronics.co.uk/Default.aspx?iabid=27 &year=2006&month=1



- [4] http://uk.fornell.com/static/en/rohs/
- [5] http://rswww.com/
- [6] www.arrow.com/green/
- [7] www.zvei.org/fileadmin/user_upload/Technik_Umwelt/ Elektro_Elektronikaltgeraete/Bleifrei/Leitfaden/ LFBlei-EN.pdf
- [8] www.leadfree.org
- [9] Elektor Electronics, March 2006, p. 16 and www.elektor-electronics.co.uk/Default.aspx?tabid=27 &year=2006&month=3
- [10] Elektor Electronics, January 2006, p. 28 and www.elektor-electronics.co.uk/Default.aspx?tabid=27 &year=2006&month=1
- [11] Elektor Electronics online Forum,
 www.elektorelectronics.co.uk/default.aspx?tabid=29&forumid=16
 &postid=697&view=topic

SERIAL COMMUNICATIONS SPECIALISTS Test and Measurement Solutions



featured products



Affordable CAN Bus Solutions from £61 (CAN-232)

CANUSB and CAN-232 are small adapters that plug into any PC USB / RS232 Port respectively to give instant CAN connectivity. These can be treated by software as a standard Windows COM Port Sending and receiving can be done in standard ASCII format. These are high performance products for much less than competitive solutions.



USB Instruments - PC Oscilloscopes & Logic Analyzers

Our PC Instruments may be budget priced but have a wealth of features normally only found in more expensive instrumentation. Our oscilloscopes have sophisticated digital triggering including delayed timebase and come with application software and DLL interface to 3rd Party apps. Our ANT8 and ANT16 Logic Analyzers feature 8/16 capture channels of data at a blazing SOOMS/S sample rate in a compact enclosure.



UPCI Serial Cards from £15 (uPCI-100L)

Discover our great value for money range of multi-port uPCI serial cards. Supporting from one to eight ports, the range includes R5232, R5422, R5485 and opto-isolated versions. Our 4 port and 8 port models can connect through external cables or the innovative wall mounting COMBOX.



USB-2COM-M

2 Port Industrial USB RS232 Serial with wall mount bracket and 5V DC auxiliary output

Quality USB to RS232 converter cable with detachable 10cm extender cable. FTDI Chipset and Drivers for superior compatibility and O.S. support.

1 to 16 port USB to Serial Adapters from £12.50

£36.00

With over 20 different models available, we probably stock the widest range of USB Serial Adapters available anywhere. We offer converter cables, multi-port enclosure style models in metal and plastic, also rack mount units with Integral PSU such as the USB-16COM-RM. Serial interfaces supported include RS232, RS422 and RS485. We also supply opto-isolated RS422 and RS485 versions for reliable long distance communications. All our USB Serial products are based on the premium chipsets and drivers from FTDI Chip for superior compatibility, performance and technical support across Windows, MAC-OS, CE and Linux platforms.



8 Port Industrial Ethernet RS232 / RS422 / RS485 Serial Server with wall mount bracket and PSU.

Single Port high performance Industrial Wireless Ethernet RS232 / RS422 / RS485 Serial Server with PSU and wall mount bracket. Connects wired also.

EtherNet and Wi-Fi 802-11b/g RS232/422/485 Serial Servers

One to eight port industrial strength Ethernet and Wireless ethernet serial RS232/RS422/RS485 Servers. Connect to your serial device remotely over your Wireless network, Ethernet or via the Internet. Based on the 32-bit ARM CPU these systems offer powerful serial connectivity and a wealth of features. WLAN models comply with IEEE 802.11b/g, max. 54 Mb/s and also offer a 10/100Mbps secondary ethernet connection. All models come complete with PSU. Prices start at only £85.00 (NetCOM 111).

EasySync Ltd

373 Scotland Street Glasgow G5 8QB U.K. Tel: +44 (141) 418-0181 Fax: +44 (141) 418-0110

Web: http://www.easysync.co.uk E-Mail: sales@easysync.co.uk


Prices shown exclude carriage and VAT where applicable

PCB Production in th

Prototype boards: quick turn-around manufacture,

Ernst Krempelsauer

 Once the design of a circuit has reached the point where the PCB CAD data file has been produced, a physical board is usually wanted as soon as possible so that a one-off unit or laboratory prototype can be assembled and tested. In this article we look how to choose between the various alternative routes to manufacture and survey their advantages and disadvantages.



Anyone who has manufactured prototype PCBs themselves, whether using chemical or mechanical processes, will know from experience what the advantages and disadvantages of this route are. It is therefore perhaps worth taking another look at the various options available. In preparing this article we have drawn on our own experiences in the *Elektor Electronics* laboratory and consulted service providers and their customers.

The basics

The basic question to answer is whether one wants to have one's own independent means of producing prototype boards. The simplest route today is surely to outsource the job of manufacturing the circuit board to one of the many service providers.

Tried and tested technologies and free competition in the market ensure that there are in general very few problems with quality or reliability of delivery, and that prices are at an acceptable level. In view of this we would need a good reason to want to make small quantities of printed circuit boards in house. One clear reason would

be confidentiality, which would be a consideration in both the military and civilian sectors. But the most important reason would probably be speed. If a design is still showing problems at the second or third version of the prototype, time will inevitably be short. Of course, the shorter the turn-around time requested, the more expen-

"Isolation milling is expensive, slow and technically antiquated."


Dietmar Bungard

(Bungard Elektronik GmbH & Co. KG)

sive contract board manufacture gets.
Further reasons for 'doing-it-yourself' include the benefits of learning the processes involved or even the simple pleasure that can be derived from producing as good a result as possible from the equipment available. This is of less relevance in the professional world: many companies

e Fast Lane

milling, or etch-it-yourself?

 

have gone out of business in the unending quest for such perfection!

If the choice is made to take the do-it-yourself route for one of the above reasons, the next decision is to select between etching and milling. Milling of printed circuit boards is the less widely used procedure (and not just among readers of Elektor Electronics), but the impression one receives from the stream of news about the subject is that there is a great deal of interest at least in finding out more about the method. The impression is reinforced by the presence of PCB milling machines at exhibitions. We will therefore start with a look at this method.

Run of the mill

Let's start with a couple of facts. One definite advantage of milling is the speed with which results can be obtained and the fact that the machines are also capable of drilling. A combined drilling and milling machine may also find other applications. And of course, the production of the circuit board in its final physical form takes place without the use of chemistry.

Against these advantages there weigh several points that account for the relatively low take-up of the milling method. First is the set-up cost: the cheapest machine, suitable for hobby use, costs around £ 500; the entrylevel industrial model from the market leader (LPKF, see p. 34 in the March 2006 issue) starts at around £ 7000. The cost of milling tools, at between £ 5 and £ 10 each, is not to be overlooked. Bungard, for example, specify a life of around 25 m path length for their isolation routing tool. This corresponds to perhaps one densely laid-out Eurocard. Such a complex board might take 20 minutes to mill per side. To this you may have to add the time it takes to convert the layout data into a suitable form for the machine, although most suppliers claim that for their machines this process is not particularly difficult using modern layout programs. Layout programs such as 'Target 3001!' can already work with machine-specific milling tools, and both Target and Eagle support the output of contours and drilling data in the standard HPGL plotter format.

A controversial question, affecting isolation milling as well as other processes, is the production of fine dust particles. Stricter controls on these particles could potentially present a problem.

"For the rapid production of prototypes or small quantities the chemical-free approach, using a milling machine as a plotter, is ideal."

Kian Kazemzadeh

(LPKF Laser & Electronics AG)

There are essential differences between a prototype

board made using a milling process and one mass-produced using an etching process. This can in particular result in different high-frequency characteristics arising from the differing shape of the track edges. Another difference which it is also essential to be aware of is the poorer solderability of milled boards. Milling a double-sided board obviously requires two separate operations, doubling the milling time. Stable mounting and careful alignment when turning the board over are essential. Through-hole contacts must be made in a separate process when milling is complete. The mechanical approach of inserting small plugs followed by chemical processing is popular. LPKF also offers a 'semi-chemical' method where a conductive paste is applied through a stencil. The board is then placed on a vacuum table and the paste is sucked into the holes. The paste is heated in an oven and the paste forms a conductive layer on the walls of the holes, making the through-hole contacts. LPKF also offers complete systems for manufacturing multi-layer boards using milling tech-

Small and large

pared to etching methods.

The most economical starting point is the Proxxon MF70 CNC XXL milling machine (**Figure 1**) from Usovo. This is a modified Proxxon MF70; if you already have such a machine, the kit of extra parts is also available separately. In contrast to the more usual 'gantry-style' milling

niques, which is a rather complex process when com-

 


Figure 1. A modified Proxxon MF70 is, at around £ 500, the cheapest CNC machine available for milling printed circuit boards. (Source: Usovo)


 


Figure 2. Prices for the entrylevel model from LPKF start at around £ 7000. (Source: LPKF)

 

A PCB milling machine

(Source: Charlyrobot)

Figure 3.

in oction.

"To me it seems that these days do-ityourself etching is just something to help explain to non-specialists how printed circuit boards are manufactured." Dirk Stans (Eurocircuits)

machines used for PCB work, this unit has a fixed milling

under the mill. The travel of the table is 162 mm (in the X

£ 100 or so). Z-axis travel is 88 mm, which explains why

the machine is so popular with model builders, for whom

using the machine for milling the occasional circuit board.

ble-sided boards is rather 'ambitious', but emphasises the

machine's high stability when compared to simple gantry-

style machines, which results in a high level of accuracy.

The machine takes around an hour to mill a complicated

The most economical gantry-style machines are available

from StepWalk (Dr Gert Müller) and from Haase. Prices

start at around £ 1400, rising rapidly depending on the

model and choice of accessories (such as drive motors).

50000 rpm) allow a considerably higher milling speed

than the slower 230 V or DC motors. These machines are

also capable of a wide range of additional tasks in addi-

The more expensive high speed spindles (up to

might be considered something of a bonus. Peter Urban

of USOVO says that using the machine for milling dou-

head and a two-axis table which moves the workpiece

axis) by 84 mm (in the Y axis), allowing only half-Eurocard size boards to be milled. For full Eurocard format

the MF70 CNC Euro version is needed (for an extra

the manufacturer suggests is suitable for engraving front panels and for manufacturing circuit boards with feature sizes down to 100 µm. The spindle rotates at 50000 rpm, allowing a milling speed of 50 mm/s.

Traditional methods

single-sided Eurocard.

For mass production of printed circuit boards the only reasonable approach is etching. It is also the first choice in many cases for prototype development in the laboratory. Start-up costs are relatively low and, because of the size of the market, there are products from various manufacturers to help with all stages of the process, including solder masks, component overlay printing, and multilayer board production. The differences between the one-off prototype and the mass-produced version are, depending on the system, less than when milling is used, and the disposal of the used chemicals is clearly regulated and relatively straightforward. As in the case of milling, setting up the equipment is only worthwhile if regular use is anticipated, or if contracting out is for some reason not feasible. The laboratory space required and logistical problems are somewhat greater than in the case of milling. and, to do the job properly, up-to-date equipment and a certain amount of discipline are required.

When it comes to speed, the question is debatable. With good equipment and efficient practices etching should be faster than milling, at least for double-sided Eurocards.

For special situations such as schools and private users there are low-cost solutions which allow good results to be achieved with reasonable effort. As is so often the case, good tools pay for themselves and cheap equipment is frequently false economy.

Quick service

Turn-around time, the range of services available, and price are the main differentiating factors between prototype PCB manufacturers. If you want a full range of services and the quickest turn-around, the price will be correspondingly high, and perhaps relatively few of the manufacturers will be able to meet your requirements. On the other hand, if you are happy to wait a little longer, and to deal entirely via a website, lower prices are available without necessarily compromising quality. Delivery times can range from a minimum of four hours (for example the 'Superblitz' service available from Cantag) to as long as three weeks (for example the 'Plot&Go' service for private individuals offered by ThePCBShop).

By using the 'pool' model to reduce set-up costs (by col-

By using the 'pool' model to reduce set-up costs (by collecting together individual orders to make for more efficient processing), and the 'on-line' mode to reduce order processing costs, the price for one-off boards can be considerably reduced. As a result ordering prototype boards through well-known suppliers such as Beta Layout/PCB Pool or Elektor's business partner 'The PCBShop' (Eurocircuits) has become the norm, while do-it-yourself produc-

"Do-it-yourself printed circuit board manufacture is particularly suitable for the smaller laboratory if a quick development cycle is needed." Jochen Lutz (Radix GmbH)

tion has become less popular. There are of course differences in price and levels of service, which can become particularly relevant if you have special technical requirements or strict deadlines. On the customer side considerations include not just the reliability and quality of the supplier but also the time involved in placing the order. The board manufacturers and the layout program suppliers have cooperated to solve this problem so that it is possible, for example, to order the circuit board online directly from the layout program. The websites of layout programs such as Eagle, Target and Abacom/Sprint Layout describe the procedure and have links to circuit board manufacturers.

Conclusion

The quick turn-around printed circuit board manufacturers now offer good quality and value for money, and are in many cases the first choice. Nevertheless, in many cases one will not wish to dispense entirely with the facility to make one's own boards. That is the current situation in the Elektor Electronics laboratories: whereas right up the 1990s we made practically all our prototypes for printed circuit boards ourselves, including double-sided boards and those with a component overlay, we now generally order prototypes from one of the online PCB manufacturers. Contrary to what some older readers believe we never undertook mass-production of our boards our-



Figure 4.
Typical single-sided printed circuit board made by milling.
(Source: Charlyrobot)

 


Figure 5.
This milled printed circuit board is somewhat more complicated.
(Source: LPKF)

 


Figure 6.
Four-layer printed
circuit board with
100 µm features made
by milling.
(Source: LPKF)

 


Figure 7.
A component overlay can easily be added to prototype printed circuit boards.

selves. As befits an international magazine with several editions covering Europe, we use several suppliers, which between them have a presence throughout Europe and beyond.

Our in-house PCB etching and drilling facilities serve as a backup for difficult and urgent cases only, and (much appreciated by the electronics enthusiast whose day job is at Elektor Electronics) as an economical and quick solution for single-sided boards.

"Single-sided SMD is ideal for do-ityourself etching. Quick turn-around contract service is the only realistic method for double-sided prototypes." Kurt Harders (Elektor Electronics reader)


Milling printed circuit boards is reserved for special situations. For example, a model builder who already owns a suitable milling machine might also use it for making

printed circuit boards. Regarding another scenario, Markus Friedrich of Friedrich Design Bureau (a supplier of Target) says: "in our experience we see mainly schools

> and universities that want simultaneously to teach layout techniques using CAD systems and how to use CNC milling machines". For industrial users LPKF seems to be is the only supplier of a complete system for manufacturing printed circuit boards with special requirements using milling

technology, but the capital costs involved are comparatively high.

(96005i-i)

 

The following have contributed comments and information to this article:

Dielmar and Jürgen Bungard (Bungard Elektronik GmbH & Co. KG)

Markus Friedrich (Ing. Büro Friedrich)

René Drescher (Contag GmbH)

Kurt Harders

Claudio Hediger

Kian Kazemzadeh (LPKF Laser & Electronics AG)

Burkhard Lewetz

Jochen Lutz (Radix GmbH)

Dirk Stans (Eurocircuits BVBA)

Peter Urban (Usovo)

Further reading

Making your own PCBs, Elektor Electronics, September 2002, p. 40 (downloadable).

Printed Circuit Board Production,

Elektor Electronics, November 1994.

Links

www.ibfriedrich.com/english/index.htm (Target) www.usovo.de (Proxxon MF70 CNC XXL, in German only) www.lpkf.com/home.htm (LPKF ProtoMat S42) www.bungard.com/home.htm (Bungard Elektronik) www.cadsoff.de (Eagle) www.stepwalk.de (StepWalk Automation, in German only) www.team-haase.de (Haase, in German only) www.charlyrobot.com/2-Web_site_English/index-GB.asp (Charlyrobot SA) www.radixgmbh.de/english/index.html?main.htm (Radix GmbH) www.contag.de (Contag, in German only) www.pcbpool.com/ppuk/info.html (Beta Layout/PCB Pool) www.eurocircuits.com (Eurocircuits/ThePCBShop) www.abacom-online.de/uk/ (Abacom/Sprint Layout)

MikroElektronika

MICROCONTROLLER DEVELOPMENT TOOLS


PICmicro

EasyPIC3 PICmicro Starter Pack £99.00



- · High quality development board
- · Built-in USB 2.0 programmer
- Windows 98/ME/2000/XP compatible
- Supports 8, 14, 18, 28 and 40-pin DIP microcontrollers from the 10F, 12F, 16F and 18F PICmicro families
- On-board LEDs, switches, 7-segment displays, potentiometers, RS-232 interface, USB and PS/2 connectors
- All I/O lines available for expansion
- · EasyPIC3 Starter Pack includes:
- √ PIC18F452 microcontroller
- √ 16x2 character LCD
- 128x64 pixel graphic LCD
- ✓ DS18S20 temperature sensor
- ✓ USB programming/power lead
- Programming software and examples

 BIGPIC3 80-pin PICmicro Starter Pack £119.00



- · High quality development board
- Built-in USB 2.0 programmer
- Windows 98/ME/2000/XP compatible
- Supports the latest 80-pin microcontrollers from the 18F PICmicro family
- On-board LEDs, switches, potentiometers, two RS-232 interfaces, PS/2 connector, and MMC/SD and Compact Flash card slots
- All I/O lines available for expansion
- BIGPIC3 Starter Pack includes:
- ✓ PIC18F8520 MCU module
- √ 16x2 character LCD
- √ 128x64 pixel graphic LCD
- √ DS18S20 temperature sensor
- ✓ USB programming/power lead
- Programming software and examples


dsPIC

EasydsPIC2 dsPIC Starter Pack £99.00



- · High quality development board
- Built-in USB 2.0 programmer
- Windows 98/ME/2000/XP compatible
- Supports 18, 28 and 40-pin DIP digital signal controllers from dsPIC30 family
- On-board LEDs, switches, potentiometers, RS-232 interface, PS/2 and ICD2 connectors, and MMC/SD card slot
- · All I/O lines available for expansion
- · EasydsPIC2 Starter Pack includes:
- √ dsPIC30F4013 digital signal controller
- ✓ 16x2 character LCD
- √ 128x64 pixel graphic LCD
- ✓ USB programming/power lead
- Programming software and examples

 dsPICPRO 64/80-pin dsPIC Starter Pack £149.00



- · High quality development board
- . Built-in USB 2.0 programmer
- Windows 98/ME/2000/XP compatible
- Supports 64 and 80-pin digital signal controllers from the dsPIC30 family
- On-board LEDs, switches, two RS-232 interfaces, RS-485 interface, two CAN interfaces, real-time clock, 12-bit A/D and D/A, and CF card slot
- · All I/O lines available for expansion
- dsPICPRO Starter Pack includes:
- √ dsPIC30F6014 DSC module
- √ 16x2 character LCD
- √ 128x64 pixel graphic LCD
- ✓ DS18S20 temperature sensor
- ✓ USB programming/power lead
- ✓ Programming software and examples

AVR

EasyAVR3 AVR Starter Pack £99.00



- · High quality development board
- Built-in USB 2.0 programmer
- Windows 98/ME/2000/XP compatible
- Supports 8, 20, 28 and 40 pin DIP AVR microcontrollers
- On-board LEDs, switches, potentiometer, RS-232 interface, 12-bit A/D and D/A, and MMC/SD card slot
- All I/O lines available for expansion
- EasyAVR3 Starter Pack includes:
- ATmega8535 microcontroller
 16x2 character LCD
- ✓ 128x64 pixel graphic LCD
- DS18S20 temperature sensor
- USB programming/power lead
- Programming software and examples

BIGAVR 64-pin AVR Starter Pack £119.00



- High quality development board
- Built-in USB 2.0 programmer
- Windows 98/ME/2000/XP compatible
- · Supports 64-pin AVR microcontrollers
- On-board LEDs, switches, potentiometers, two RS-232 interfaces, PS/2 connector, and MMC/SD and Compact Flash card slots
- · All I/O lines available for expansion
- BIGAVR Starter Pack includes:
- ✓ ATmega128 MCU module
- ✓ 16x2 character LCD
 ✓ 128x64 pixet graphic LCD
- 128x64 pixel graphic LCD
- DS18S20 temperature sensor
- USB programming/power lead
 Programming software and examples

8051

Easy8051 8051 Starter Pack £99.00



- · High quality development board
- Built-in USB 2.0 programmer
- Windows 98/ME/2000/XP compatible
- Supports 20 and 40-pin DIP Atmel
 8051 Flash microcontrollers
- On-board LEDs, switches, potentiometer, RS-232 interface, 12-bit A/D and D/A, and two additional 8-bit I/O ports
- All I/O lines available for expansion
- Easy8051 Starter Pack includes:
- √ 40-pin 8051 microcontroller
 √ 16x2 character LCD
- √ 128x64 pixel graphic LCD
- ✓ DS18S20 temperature sensor
- ✓ USB programming/power lead
 ✓ Programming software and examples

PSoC

EasyPSoC3 PSoC Starter Pack £119.00



- High quality development board
- Built-in USB 2.0 programmer
- Windows 98/ME/2000/XP compatible
- Supports 8, 20, 28 and 48-pin DIP PSoC mixed-signal controllers
- On-board LEDs, switches, potentiometers, RS-232 interface, RS-485 interface, CAN interface, real-time clock, and MMC/SD and CF card slots
- · All I/O lines available for expansion
- EasyPSoC3 Starter Pack includes:
- √ 48-pin PSoC microcontroller
- √ 16x2 character LCD
- ✓ 128x64 pixel graphic LCD
- DS18S20 temperature sensor
- USB programming/power lead
 Programming software and examples




Breadboarding Systems can supply all MikroElektronika products from stock. Credit and debit cards accepted. Prices shown exclude delivery and VAT.

Breadboarding Systems
Software and hardware development tools

Tel: 0845 226 9451

Web: www.breadboarding.co.uk

Mini ATMega Board

 

Florian Schäffer

It's about time, you might say! After all, even if the ATmega microcontroller isn't necessarily mega, it's still quite popular and we feel it hasn't really received the attention it deserves in *Elektor Electronics*. The Mini ATmega Board described here puts a change to that, and a nice application for it — our Standalone OBD2 Analyser— is featured in an accompanying article.

The Mini ATmega Board is a complete application board for the ATmega16 and ATmega32 members of the Atmel AVR family. It includes an LCD port, a serial interface, and abundant I/O lines. For programming, the board also has a mini-interface for communicating with a PC serial port.

There are numerous potential applications for small single-board computers in the domestic and hobby realm, such as central heating controllers, roller-shutter controllers and alarm systems. Another popular application is controlling autonomous robotic systems. In any case, developing your own application programs requires a certain amount of programming expertise, and this board with its programming interface is naturally quite

suitable for acquiring that expertise. It's easy to convert user inputs into actions and responses, even with only a small program.

Simple but versatile

In its standard configuration, the board is intended to be fitted with an ATmega16. This relatively inexpensive

For Almegal 6 and Almega32

 


Figure 1. Schematic diagram of the Mini ATmega Board, which forms a good basis for compact applications.

microcontroller from the 8-bit AVR RISC family is quite suitable for beginners due to its DIL package, which is easier to handle than the SMD packages of the smaller AVR microcontrollers. The ATmega8, which comes in a skinny 28-pin package but still has a large number of I/O pins, is also very popular. However, its 8 KB of internal flash program memory is a bit on the

Almega 16 with twice as much memory. If you need even more memory, the pin-compatible Almega 32 can also be fitted to the board. As the latter device is also largely software-compatible, it's generally only necessary to recompile the software in question without having to make any other modifications.

Another reason for the popularity of the ATmega processors is the fact that many major elements are already integrated. In addition, the 32 I/O lines of the two larger versions provide adequate connectivity for supplementary hardware, including eight pins that can be routed to an internal analogue-to-digital converter. The processor can run at a

 


Figure 2. Track and component layouts of the circuit board.

maximum clock rate of 16 MHz, which yields respectable computing power. Processing complex, time-critical tasks is usually not a problem, because most of the machine instructions require only two system clocks for execution. Additional useful features include internal software UARTs for serial communication and the ability to respond to interrupts and handle system crashes using a watchdog timer.

Everything on board

As you can see from the schematic diagram (Figure 1), only a few components are fitted to the board. Of course, operating power and a clock source are essential. The first is provided by a 5-V voltage regulator (IC3), and an 8-MHz crystal sets the rate of the microcontroller's internal oscillator.

Nearly all of the other components are used to support the various interfaces. K1 is the connector for the programming adapter. The circuit arrangement is compatible with conventional 10-lead adapters, such as those used with the Atmel STK boards.

The RS232 port (K4) can be programmed via the internal software USART, and it can achieve high data transmission rates thanks to interrupt control and buffering. The two jumpers JP3 and JP4 allow + 10 V and -10 V to be connected to the D-Sub connector in order to power 'vampire circuits'. A null modem cable must be used to connect the port to a PC, and jumpers JP3 and JP4 should be left open in that case.

A few switches and LEDs are naturally quite welcome for simple experiments using the board. Consequently, a set of LEDs (LED array D1) and DIP switches (S1) are connected to the I/O lines. The ATmega can supply up to 40 mA per pin to drive LEDs or other components directly without additional circuitry. If you want to use the port lines for some other purpose, the pull-down resistors (array R2) and LEDs can be disabled by jumper JP2 or JP1, respectively. If port A is used as an output, the DIP switches must be switched off (open) to avoid damage to the IC.

Components L1, C2 and C14 are provided to improve the accuracy of the A/D converter. If an accurate A/D converter is not needed, these components can be omitted and L1 can be replaced by a wire bridge.

A LCD module with four rows of 20 characters (4 x 20) is the preferred choice for the display and a perfectly suitable type is offered through the Elektor SHOP. The board is laid out to exactly fit such a display module. The display can be connected using a pair of flat cables. However, a more elegant solution is solder half a wire-wrap IC socket to the circuit board. If a pin header is fitted to the LCD board, it can be plugged directly into the socket. As there are many similar versions of this standard type of display. you should check carefully to make sure the pinout matches the board layout. The modern blue versions are of course easier on the eye than the usual green versions, but as so often happens, it costs a bit more to have a special taste.

 


Figure 3. The fully assembled prototype board.



Don't forget to adjust the contrast setting with P1 when you first power up the board – otherwise you might think the display is defective, because you won't see anything if the setting is wrong.

A LED array with ten LEDs is recommended for D1. In that case, D3 is automatically the tenth (uppermost) LED in the array, and the ninth LED is not used. If you can only obtain an array with eight LEDs, fit it in the lower eight positions. The ninth position will then remain open, and a normal LED can be fitted in the tenth position for D3.

K3 and K3A can be used to fit pins on the bottom of the board. That will allow the entire board to be plugged into another board as a replacement for an ATmega for experimental purposes. K2 and K2A are left open for connecting I/O lines.

The only thing left to mention is the decoupling capacitors under the micro-

controller. If you use a socket for the microcontroller, there will probably be enough room on top of the board to fit small capacitors. If that isn't possible, solder three capacitors in SMD-0805 packages to the pads provided for that purpose on the bottom of the board.

Programming

The microcontroller can be programmed directly from a PC via a simple programming adapter (see inset). A variety of small programs are available for this purpose. Although some of them are not especially user-friendly, they all do the job. For instance, you can use PonyProg to download fully compiled programs to the ATmega and set the most important (and crucial) fuse bits.

The fuse bits are used to configure the microcontroller, and this can lead to unfortunate situations in which you lock yourself out, for instance if you

 


Figure 4. The correct settings must be configured very carefully in PonyProg before the microcontroller is programmed.

configure the clock source incorrectly or reconfigure the Reset pin as an I/O pin. On top of that, the AVR data sheets use a somewhat puzzling logic that is then partially inverted by the program. The first time you use the program, you must use Setup / Interface Setup to configure the right settings and then select the proper microcontroller type in the Devices menu. It's certainly a good idea to use the programmer to read the actual settings of the fuse bits (via Security and Configuration Bits in the Command menu if you're using PonyProg) before you start programming. Not every program does this automatically. You can then compare the bit settings to the descriptions provided in the data sheet. Figure 4 shows the required. settings for using an external 8-MHz crystal and enabling brownout detection, which resets the processor when the supply voltage is applied or removed. Data loss could occur if brownout detection is not used. because no external circuitry is provided for that purpose.

Free development environment

Numerous development environments are available for the AVR family, and it's easy to develop programs in Basic using BASCOM-AVR (free for code sizes up to 4 KB), in assembly language using the free AVR Studio environment, or in GCC using the free WinAVR environment.

The example applications for this board were generated using WinAVR, compiled for the ATmega16, and converted to machine language, so all you have to do is use the programmer to download the resulting hex files to the flash memory of the microcontroller. If

 


Figure 5. These fuse bits must be set to use an external 8-MHz crystal and enable brownout protection.

you want to recompile the code to use a different crystal or a different type of ATmega microcontroller, you only have to modify the 'make' file accordingly. The AVR GCC Tutorial referenced the link list provides a very extensive introduction to C programming, aithough you must always bear in mind that many of the examples were developed for somewhat older types of microcontrollers (now discontinued) and require some changes. The routines for the LCD may also need slight modifications, because even though very good general-purpose templates are already available, they have not been included in the examples in order to keep the code as simple as possible.

All the examples can be downloaded from the Elektor Electronics website (www.elektor-electronics.co.uk) in a Zip file. You can use these programs to become familiar with all the essential components and test your board. To get started, you could use the simple 'blinking LEDs' program. The next step would be to display a message on the LED or try out data communications via the serial interface.

As already mentioned in the introduction, an interesting application for this board is described in a companion article in this issue. It is a stand-alone OBD display unit for car diagnostics, which you can also use to display vehicle-specific data 'on board' via the LCD module while you are driving.

Extensions

If you are interested in extending the board after successfully completing your initial programming and application projects, there are many possibilities – far too many to mention them

all in this article. For instance, you could implement an I²C bus with only a few additional components, add a USB port, or even connect an SC memory card to store measurement data for subsequent analysis using a PC. Naturally, you can also make contact with other ATmega fans in the various microcontroller forums, including (of course) the one at www.elektor-electronics.co.uk, and various newsgroups.

[350175-1]

Items available for this project

050176-1 PCB, supplied including programming adapter board (050176-2).

050176-42 Programmed ATMEGA16

O50176-72 Kit of parts, includes ATMega board 050176-1, programming adapter board 050176-2, preprogrammed ATmega microcontroller (with OBD2 program), all components for both boards but excluding LC display.

050176-73 LCD, module, 4 x 20 characters, 60 x 98 mm, with background lighting.

050176-74 Case, Bopla Unimas 160 with perspex cover and mounting plate

Available from www.elektor-electronics.co.uk
Hyperlinks for the project.

050176-11.zip Development software including program examples (free download).

In-system programming

The minimum circuit configuration for an ATmega actually amounts to nothing more than a supply voltage. The external crystal can be omitted if you use the internal oscillator. However, the processor clock rate is not defined especially accurately in that case, so operation using the internal oscillator is only suitable for applications that are not time-critical.

Aside from the supply voltage and the crystal (if used), you also need a programming interface port to load a program into the ATmega. As the ATmega has an in-system programming (ISP) interface, it can be programmed in the application circuit – or reprogrammed as often as desired. The flash memory can handle up to 10,000 write operations, and the EEPROM can handle up to 100,000.

The programming adapter described here can be connected directly to a PC using a one-to-one cable. Connect the other end of the adapter to the ISP connector (K1) of the Mini Mega Board, and you're all set to program the microcontroller directly from your PC.

The circuitry of the programming adapter (**Figure 1**) can be built into the housing of a 9-way D-Sub cable connector to produce a handy programming adapter cable.

Assembling the circuit on the small circuit board (Figure 2) is not particularly difficult, but it does require a steady hand and a bit of care. Before fitting the components, check to make sure the board fits in the housing of the D-Sub connector. Then fit the SMD components first, followed by K2 on the other side of the board. Before soldering the D-Sub connector (K1), check again to make sure the board fits. In our prototype, we removed the rear wall of the connector housing. That allowed K2 to just fit, and the flat cable could be fed out without any problem. Do not solder K1 in place until you are sure that the board fits in the connector housing. It will probably be necessary to shorten the pins of K1 slightly and fit the board at a bit of an angle. As the connector housing is made from metal or conductive plastic, you should cover the inside with insulating tape to prevent unwanted contact with the circuit board

 


Figure 1. Circuit diagram of the programming adapter.

 


Figure 2. Track side and component side layouts of the programming adapter circuit board.

COMPONENTS LIST

(programming adaptor)

Resistors (SMD 0805)

 $R1,R5 = 10k\Omega$ $R2,R3 = 4k\Omega 7$ $R4 = 33k\Omega$

Capacitors (SMD 0805)

C1 = 220pF

Semiconductors

D1,D2,D3 = zener diode 5V1, 250 mW, SOT23 case (e.g. BZX84 5V1 SOT23)
T1 = BC847 (SOT23)

Miscellaneous

K1 = 9-way sub-D socket (female) with case
K2 = 10-way pinheader
10-way flatcable (0.5 - 1 m)
10-way UIDC connector for flatcable
PCB, order code **050176-2** (see SHOP pages or website)


 


Figure 3. The circuit board with the SMD components fitted.

 

You can use the OBD-2 / EOBD diagnostic connector required in all recent cars to read out a lot of interesting data if you have a suitable interface adapter and a notebook computer. An even more practical solution is to use the stand-alone analyser described here, which can be used as a hand-held unit or fitted in your car. Diagnostic data is evaluated using an ATmega 16 and shown on an LCD with four rows of 20 characters. Up to eight parameters can be constantly shown on the display while you're driving. Having this information at your fingertips can be especially handy if you have car trouble.

It seemed like an obvious idea: why not use the OBD-2 analyser described in the 2005 Summer Circuits issue more than just twice a year? After all, the car's OBD-2 interface provides interesting data all the time while the vehicle is underway, although using a notebook computer as a display while travelling is rather impractical. Just as with navigation systems, the only suitable approach is to use a portable display or a built-in display with convenient dimensions.

No sooner said than done. Fortunately, the OBD data is not so complex that the processing power of a PC is actually necessary to handle it. A microcontroller with a serial port is perfectly adequate, and an easy-to-read alphanumeric LCD is a lot more suitable than a cumbersome notebook screen for displaying the data in a car.

The microcontroller hardware consists of the Mini Mega Board described in another article in this issue. It is fitted with an Atmel ATmega16 microcontroller, which fetches the data from the OBD-2 analyser via a serial interface, analyses the data, and presents it on the LC display. The board already has all the components necessary for this application, except a pushbutton switch on PAO for configuring the display parameters.

As the available readings vary from one vehicle to the next, the display should be freely configurable so the digital cockpit can be adapted to every vehicle that can supply data to the OBD-2 Analyser. To find out which vehicles fall in that category, you can consult the *Elektor Electronics* forum or the database referenced in the link list at the end of this article. Thanks to this

configurability, each user can personally decide which of the available readings should be displayed and whether to display the readings in short form or long form.

Combo

As the OBD-2 Analyser and the Mini ATMega Board (Figure 1) both have a full-fledged serial interface, it's easy to establish a communication link between the two boards. With regard to mechanical mating of the two boards to form a stand-alone analyser, refer to the capsule instructions listed in the 'Step by Step' inset.

The boards can be powered from the OBD-II connector. However, the supply voltage on that connector is unswitched, so it's worth having a look at the fuse box to see whether a

 


Figure 1. OBD-2 Analyser board and ATmega board after assembly.

'switched ignition plus' terminal is available so the boards will only be powered when the ignition switch is on. That's more practical than pulling the OBD plug or using an additional switch.

One problem that cannot be ignored for in-car used is the large temperature range. Many inexpensive LCD modules are not designed for the freezing temperatures that can occur in cars in the winter. Freezing of the liquid crystal medium can cause permanent damage. Most modules are more tolerant with regard to the upper end of the temperature range. The module shown in components list for the Mini Mega Board has an operating temperature range of -20 °C to +70 °C, and it can withstand temperatures as low as -30 °C without damage when not operating. However, the maximum allowable current for the

LED backlight is reduced at temperatures above +25 °C.

What do you want to see?

Information about the ignition timing advance or exact intake air volume is probably not as interesting in normal driving situations as the engine speed (rpm) or vehicle speed, to mention two examples. It's commonly known that standard speedometers read slightly high despite using electronic drive, with the deviation being as much as 10 km/h depending on the speed. Interestingly enough, a significantly more accurate value is output by the OBD system. Comparative measurements using a stopwatch and a GPS receiver showed that the OBD-II system provides a very accurate indication of the true speed, and the OBD-

controlled digital cockpit display provides an accurate reading over the entire speed range. Of course, if you rely on that reading you will lose the 'margin of safety' that has probably saved you from being caught in a radar trap several times already. If you don't already have a tachometer, or if you mistrust the one fitted in your car, you can also obtain reliable rpm data from the OBD-II system.


The exact coolant temperature is another thing that is doubtless interesting. Unfortunately, there's no uniform specification for the OBD-II interface with regard to outputting the water temperature or the oil temperature. The oil temperature is more commonly output with diesel vehicles than with petrol vehicles, which usually output the water temperature. You can figure out where the sensor is fitted by



Figure 2. Prototype of the stand-alone OBD analyser.

Byte	Meaning
06	Reply ID
02	Mode 2 response (report readings)
0A	Number of following bytes (10)
48	Protocol information
6B	Protocol information
10	ECU address
41	40 + requested service (1)
00	Requested PID (0)
9.8	First data byte (MSB)
3F	Second data byte
80	Third data byte
11	Fourth data byte (LSB)
6Ç	Checksum

Figure 3. Assembly of the boards shown in our prototype.

 

observing the time behaviour of the temperature reading provided by the OBD system. If the temperature increases linearly after a cold start, it represents the coolant temperature. If instead the indicated value does not increase until the engine has been running for a while, and then increases rapidly to around 90 °C, it comes from an oil-temperature sensor. The oil temperature is important with regard to the load capacity of the engine, and it takes a lot longer to return to the 'green' zone than the water temperature. That means an oil temperature display can certainly help extend the service life of your engine.

Software

The software for the microcontroller on the Mini Mega Board is available on the Elektor Electronics website in the downloads for this article in the form of a ready-to-use hex file, which you only have to download into flash memory. The program has been compiled for an ATmega16 with an external 8-MHz crystal. The software was tested with chip version 2600 of the mOByDiC microcontroller in the OBD analyser. However, future versions shouldn't cause any changes in communications between the OBD analyser and the Mini Mega Board, so we don't anticipate any problems. If necessary, information about any relevant changes will be provided in the Elektor Electronics website forum and the Mailbox or Corrections & Updates section of the magazine.

For readers who not only want to build and use the stand-alone analyser, but also want to know how the software works, here's a brief explanation. Simple commands can be used to request the microcontroller of the OBD-2 Analyser to establish a connection to the vehicle and supply data blocks. These commands are described in the data sheet for the mOByDiC microcontroller. The communication process essentially consists of exchanging request and response bytes. The commands are very similar to those for the well-known ELM OBD ICs, so a glance at the (significantly more informative) data sheets for those devices can be helpful.

If you want to find out which data is supported by a particular vehicle, you should request the parameter identifiers (PIDs) by sending the byte string 02 01 00 (hexadecimal values). That particular series of bytes means that you want to read data (02), you are working in Mode 1 (request readings), and you want to read out PIDO. In response, you will receive (among other things) four data bytes for the first 32 supported PIDs. Many vehicles can also supply additional parameters, but they are not supported by the display unit in its present form.

After this, you can send the byte sequence 02 01 followed by a PID number to request the data block for the corresponding PID. The response will be something resembling what is shown in Table 1. The checksum calculation is quite simple: the byte values starting with the third byte onward are added, and the sum is then ANDed with FF to eliminate everything except the two least-significant hex digits.

The meanings of the individual bytes and the calculations necessary to generate the displayed readings are described for all the supported protocols in the ISO 15031-5 standard and its US counterpart SAE J1979. However, if you're not willing to spend £ 100 or so for your own copy, you can obtain more information from the well-known www.obd-2.de website, which is run by the author of the first OBD article in *Elektor Electronics* (October 2002).

Display configuration

The readings shown on the display depend on two factors. The first factor is which PIDs are available from vehicle in question, and the second factor is which of the available readings the user selects for the display configuration.

When the stand-alone analyser is switched on, it automatically determines which PIDs are supported by the vehicle and stores them in the EEPROM of the ATMega. If the analyser is connected to a different vehicle, it will automatically recognise any change in the available PIDs. In both cases, the unit will ask you to configure the display for the readings you want to have displayed (Figure 4). You can also enter the configuration mode whenever you wish by pressing and holding the PAO button.

The display can show up to eight readings in short form (Figure 5) or four readings in long form (Figure 6). For each line, you can select either one reading in long form or two readings in short form. A blinking cursor indicates the position that is currently being

Step by Step

1. Before you start, you have to consider where and how you want to fit the two boards. One option is to fit them into an enclosure, as we did for the prototype shown in the photos. However, you might be able to find a suitable place for them in the car (measure carefully!), so all you need is a frame or front panel to cover the boards. In that regard, you should bear in mind that the OBD cable is relatively thick, and for cosmetic reasons it should probably be concealed from sight.



Figure 2 shows the construction of our prototype unit. The enclosure has a transparent acrylic sheet as a front panel. We painted it on the inside using spray paint. The opening for the display was masked off before painting. That's an easy way to produce a perfect display window without drilling, sawing or routing.

2. The two boards are joined together using a mounting plate (aluminium sheet or piece of circuit board). The mounting plate is located between the two boards. The Mini ATMega Board is placed at the front, and the OBD analyser board is placed at the rear. The mounting plate fits into the guide slots in the enclosure. With the enclosure we used for the prototype, 15-mm and 10-mm standoffs produced exactly the right spacing for the board assembly.

As an alternative, the OBD-2 Analyser board could be fitted horizontally in the enclosure. However, the vertical arrangement we used for the prototype has the advantage that it is easier to connect the OBD cable. If you use a straight D-sub connector for K2 instead of an angle connector, the cable can be plugged in directly. Of course, you can also omit K2 and solder the OBD-II cable directly to the board. In that case, you will have to cut off the D-sub connector at the end of the OBD-II cable, but you may have to do that anyhow if the OBD cable is not long enough. If the OBD vehicle connector is located somewhere other than near the steering wheel, such as under the seat, the cable will usually be too short. Then it's a good idea to use a different cable of sufficient length and fit the OBD-II plug at one end. The other end can be fitted with a 9-way D-sub connector or soldered directly to the OBD analyser board.

3. Only four connections are necessary between the two boards. Pins 2, 3 and 5 (ground) of K1 on the OBD-2 Analyser board must be connected to the same pins of K4 on the ATmega board. You should use stranded wire for this instead of solid wire to avoid a risk of breakage. The fourth connection is required to route the +12-V supply voltage to the ATmega board. If you omit K4 (power supply connector) on the ATmega board, you will have a connection point for +12 V that is connected to the anode of D2 via a circuit board track. On the OBD-2 board, +12 V is present at the anode of D3. You can thus connect the anode of D3 on the OBD board to the anode of D2 on the ATmega board.

Connect the display configuration pushbutton switch between PAO (microcontroller pin 40) and +5 V.

 


Figure 4. Display contents after switch-on in the car.

 


Figure 5. Display screen showing four readings.

 


Figure 6. Up to eight readings can be displayed simultaneously.

Important Tips

- If the existing OBD-2 cable is too short and you cannot find nine-conductor screened cable to make a replacement cable, 8-conductor network cable (CAT5, preferably screened) is a readily available alternative. The missing ninth conductor (with respect to the OBD cable) is actually unnecessary, because you can use a single ground connection instead of two connections. Refer to the construction instructions for the OBD-2 Analyser in the July/August 2005 issue of Elektor Electronics for cable wiring details.
- If you already fitted the 9-way D-sub connector (K1) on the OBD analyser board, that doesn't have to present a problem for joining it to the ATmega board. Simply leave the connector in place and solder the three leads to the bottom of the ATmega board.
- If you already fitted the 9-way D-sub socket (K2) on the OBD analyser board, you shouldn't try to unsolder it intact, because the through-hole plating will usually not survive such an exercise. A better solution is to cut off the pins and then unsolder the pin remnants individually (hold the pin with pliers, heat the solder joint until the solder melts, and them pull the pin out).
- There is a new version of the OBD-2 software. Information about possible upgrades will be published on www.elektor-electronics.co.uk as soon as the details are known.

configured. If the cursor is at the start of a line, you can select the long form or the short form for displaying a reading. Pressing the button causes the next available reading or next display option to be shown. The display position is blanked after you have cycled through all the available PIDs, and pressing the button again causes the first reading option (protocol and available PIDs in hexadecimal notation) to be displayed. If you leave the button

What's in a car?

The question about which parameters you can read out from your car is best answered by your car. You can be sure of the answer after reading out the supported PIDs via the OBD-2 connector. After that, you can read out measured values for the PIDs supported by the ECU. Consult the author's website

www.blafusel.de/misc/ obd2_pid.php

for specific information about he PIDs.

That website also provides another brilliantly simple feature: type the PID code read out by the standalone analyser into the search field to view full list of the supported functions. For example, the meaning of PID 983F8011 is shown in the following table.

PID	Sensor
1	System tests status
4	Calculated load value
5	Engine coolant temp
11	Intake manifold pressure
12	Engine RPM
13	Vehicle speed
14	Ignition timing advance
15	Air intake temperature
16	Air flow rate from MAF
17	Absolute throttle position
28	OBD standard
32	More PIDs

unpressed for a couple of seconds, the cursor will jump to the next display position. If you previously selected a long-form display, it will jump directly to the next line.


The configuration session is ended when the last available position has been configured. Only short-form outputs can be configured in the second half of each line.

Functions

As the stand-alone analyser is designed to be used as a digital add-on instrument for cars, its trouble diagnosis capabilities are limited. Storing text descriptions of trouble codes would vastly exceed the memory capacity of the ATmega16. Consequently, you will still have to use a laptop computer with diagnostic software to read and clear trouble codes.

PID 2 is also not supported. That PID indicates which trouble codes caused trouble data to be stored in the engine control unit. However, the ATmega software does recognise any trouble indications that may occur if they can be read out in Mode 7. That actually includes all continually monitored systems. However, the fact that no trouble is indicated does not necessarily mean that no trouble codes have been stored. The actual trouble codes must be read using other OBD service modes, depending on the manufacturer.

The blinking spanner symbol

 

alternating with an inverted exclamation mark and 'Diagnosis' on the display indicates that a trouble code has been detected. You can then use the diagnostic software on your laptop to read out the trouble code and clear the trouble memory.

Of course, it's also possible to configure the unit to display PID1. If PID1 is supported by the engine control unit, it contains the number of pending exhaust-related trouble codes that caused the engine-trouble warning symbol (MIL, or 'malfunction indicator lamp') to be illuminated in the vehicle cockpit.

Construction information for autonomous analyser

Component population changes to ATmega board:

Not required: R1, K4, K6, S1, D1, JP1, JP3 and JP4 (do not fit), JP2 = wire link

Additionally required:

S3 = pushbutton (1 make contact) between PA0 and +5 V
Case, e.g. Bopla Unimas U160, size 160/133/75 mm
Programmed ATmega Controller, order code 050176-42 (HEX file contained in free download 050176-81.zip from www.elektor-electronics.co.uk)
Configuration bits for ATmega: All bits upprogrammed (*17) avecas PCOTS70

Configuration bits for ATmega: All bits unprogrammed ("1") except BOOTSZO, BOOTSZ1, BODEN and SUT1.

Component population changes to OBD-2 Analyser board:

Do not fit K1; use straight pins version for K2, or do not mount it.

For kits and parts for this project,

see Elektor SHOP pages or www.elektorelectronics.co.uk

DIY ideas

A microcontroller system (such as the Mini Mega Board) connected to an OBD-2 Analyser naturally lends itself to a wide variety of further applications, including DIY projects. For instance, you could develop a data logging function using a standard SD

memory card so the data could subsequently be read out and analysed on your home PC. If you add GPS data storage to that, you have a true digital 'black box' in your car, which might be too much of a good thing in terms of monitoring.

(052175-2)

Links

www.elektor-electronics.co.uk (OBD forum)

www.blafusel.de/misc/obd2_scanned.php (vehicle list; the Elektor Electronics OBD-2 Analyser is shown there as 'mOByDic interface')

www.ozenelektronik.com/uplcad/data/oe/moby2600.pdf (mOByDiC 2600 data sheet)

www.blafusel.de/misc/obd2_pid.php (PID calculation)

www.obd-2.de/tech_prog.html (Gerhard Müller's reading calculations for individual PIDs)

www.iso.org (ISO - International Organization for Standardization)

www.sae.org (SAE - Society of Automotive Engineers)

An ATmega by any other name...

As mentioned in the article, the Mini ATMega Board can be fitted with the ATmega 16 (which has 16 KB of program memory) or the ATmega 32 (which has 32 KB). The only difference between the two microcontrollers thus appears to be the size of the flash memory. At least, that's what we thought when we loaded code compiled for an ATmega 16 into an ATmega 32. When nothing at all worked and we were at our wit's end trying to figure out why, an attentive colleague pointed out that we had the wrong type of microcontroller. Now you know, so you don't have to try it for yourself.



Rarely have we received so many (enthusiastic) reactions from readers as those that were prompted by the publication of the OBD-2 analyser. Rarely were we asked so many questions and rarely did we have so few answers...

Karel Walraven

In the Double Summer Issue (the July/August issue) of 2005 we published an article concerning a DIY car analyser device, the OBD-2 Analyser.

With the aid of this circuit. and a (laptop) computer it is possible to read information from your car such as temperature, speed, engine rev speed and instanta-

neous power. In addition, the screen also shows fault codes as soon as something goes wrong with your precious possession, so that you're no longer completely dependent on your mechanic.

Thousands of readers have built this circuit and it was unavoidable that we at the editorial offices were going to

was obviously: I have such and such a car and will the circuit work with my car? To get some clarification we asked you to share your experiences on the forum on our website and

we received a massive response. At the moment we are sorting through all the responses so that it will be easier for you to get a quick overview. The most important issues we discuss here.

be inundated with questions. The most common question

The reports of models that were

successfully read started to stream in.

tor Electronics

"The PC communicates with my Fiat Stilo

from 2003, but the measurement results

make no sense at all."

Hurray!

It appears that our car is our most precious possession, we cherish it and with every small deviation from normal driving behaviour or sound we are concerned. It is then not surprising that you as technically interested people are so happy with a circuit that allows you to diagnose possible defects. The comments on this topic varied from "Hurray, at last!" to "What a good idea".

Without doubt, the most common question was: "For which cars is the OBD-2 tester suitable?" In the original article we naturally mentioned that in principle petrol cars from 2001 and diesels from 2003 are fitted with an EOBD-interface. However, it appears to be a little sneakier than that. A few old hands in the trade butted

into this discussion and the answer is: "New petrol cars from 2001 and new diesel models from 2003. If a model was already in production before that year, then it does NOT need to conform to the OBD-2 standard. And of

course there are always the stubborn manufacturers who will do different if they can get away with it..."

The pinch is therefore the word 'new'. This does not mean new from the factory but a new model or an upgraded model. So it is quite possible that the car with petrol engine that you bought in 2002 is not compatible!

ues that make no sense: "The PC communicates with my Fiat Stilo from 2003, but the measurement results make no sense at all. For example, water temperature 215. I

have read on another site (Özen Elektronik) that Fiats from 2003 and earlier speak their own language and they were going to make a program that would work with this. Does anyone know any more of this? I'm keen to find a good working

program, because I have been struggling with this car from the beginning and really would like to read everything back. Fiat have been dragging the chain and are now saying that the warranty is over."

The company Özen does indeed have special chips for certain makes, including Fiat, Ford and Mazda. It is however best to go directly to the website for Özen Elektronik and to have a look around and, if necessary, to contact them.




It is not all gold that glitters...

We cannot ignore that a number of readers were disappointed with the design and had hoped for more. Your official car dealership has diagnostic equipment from the factory that costs thousands of Euros and provides a practically complete insight in all aspects of your car. We will be very honest here: Our OBD-2 analyser cannot compete with this, its capabilities are considerably more modest. But this is offset by a price tag that is also considerably more modest. Only those parameters (plus a few extras that differ for each car) that the manufacturer is required to make available according to European law, are displayed by our analyser. In particular with cars from earlier than 2000 it is sometimes disappointing how much (read: how little) can be read. "Not completely OBD-2 compliant. I can scan sensor values, but no DTCs are found. Unfortunately I do not know if there are no DTCs or if they cannot be read..."

In addition there were a large number of readers who wanted to use the OBD-2 circuit for engine tuning. Unfortunately it is not suitable for this. This is the domain of specialisis! Consider that it is much easier to ruin your engine than it is to get more power from it!

Cars from the Fiat group often provide measurement val-

 

 


Figure 1. in this way a reset button can be added to the circuit.

A few readers with non-European cars tried to connect to the WDS (Worldwide Diagnostics System) bus, but without positive results: "I was

wondering if the OBD-2 kit will allow me change or write to the ECU using WDS?" But the answer from the forum was unanimous: "WDS requires sep-

arate PC software with its own interface. This will absolutely not work via OBD-2."

Good service!

From chipping come chips. A few circuits did not work and after checking them it appeared that the program was not burned properly in the microprocessor. We promptly replaced those and in general people were quite happy with that, particularly when everything was resolved quickly.

Reset perils

The early-bird buyers were confronted with start-up problems: a few components were missing here and there. This resulted in a drastic review of our internal buying procedures, after which the problem was solved. In addition it appeared that the microprocessor in the circuit required a relatively long reset-pulse in order to start reliably. That is why initially both C7 and the ZSH560

Suitable programs

In the forum the following programs have been mentioned that appear to work well with the OBD-2 hardware:

MCI 1.2b

Digimoto lite

Mobytester plus

OBD25py

Scanmaster

VitalScan

All these programs can be found at http://www.ozenelektronik.com. You have to log in and then select Download/Mobydic.

needed to be fitted. We had to replace the reset generator with a pin-compatible, more readily available type. C7 does not have to be fitted with the new type, a DS18212, because this already provides a long resetpulse by itself.

The reports of models that were successfully read started to stream in. For a brief period there was some doubt over the jumper because it was not mentioned in the article. "We use this jumper when downloading the firmware. Leave it open for normal use. While the flash memory will not be erased if the jumper is in place, the chip will not run either."

In the meantime, owners of cars from the Volkswagen group had a few difficulties. They were plagued by startup problems. But in the shortest possible time the answer was available in the farum: At power on the red LED has to light up. The moment the microprocessor starts to communicate the yellow LED will blink irregularly. All protocols are now tried one after the other. As soon as a valid protocol has been found the green LED lights up and the yellow LED will flash every now and then to indi-

cate that communication is taking place. If no valid protocol has been found, then the yellow LED will light every 3 seconds. The search for the protocol is done only once after each

reset. If the electronics in the car is switched on later via the ignition key so that the protocol is not available early enough, then the OBD-2 analyser will wait indefinitely. There are a few remedies for this: Briefly unplug the OBD cable so that the microprocessor is reset after which the cable can be plugged back in, add a reset switch on the circuit board, or and on/off switch in the +12-V connection between the car and the analyser. In Figure 1 you can see that adding a reset pushbutton is a straightforward job.

Other pitfalls

Who has succeeded in mounting the

assembled PCB in its enclosure?

When working on a car, a laptop is obviously much more practical than a large PC with all its individual parts. However, laptops often have only USB connections. and there was quickly the realisation that some types of USB/RS232 converters were not compatible enough. If the conversion from RS232 to USB is too slow then it is possible that the OBD-2 analyser does not find a valid protocol. In any case, the converters from the company Ozen Elektronik work well and all converters with FTDI chips work without problems.

About the construction

"Who has succeeded in fitting the assembled PCB in its enclosure without removing the front?" a reader asked. The answer came from both the Elektor Electronics lab as well as from a reader: "I have done it differently. Place the PCB on the upside-down lid and place the enclosure on top, so that the holes line up. Then mark the width of the connectors. After that, place the enclosure with the edge on the lid and mark the height of the connectors. Cut out or file away the marked parts. When you place the PCB on the lid and the enclosure over the top and screw them together, the PCB is then held in place by the connectors. Sliding or rattling is then not a problem."

(USB176-II)



B² Spice Professional V5.2



Low cost - high performance.

Features only normally found in packages costing more than £1,000.

Virtual Instruments & unlimited simulation options. See what's really going on with powerful new Dynamic Schematics, animated graphs and charts. Real-time simulation means that parameters can now be altered as a simulation is running. New circuit wizard, new graphing module, over 30,000 models as standard, 'easy view', 'live circuit' functions and PCB Export. No limit on circuit size. Free technical support.

'We're confident the new B2 Spice will impress you. We offer an unconditional 45 day evaluation of the full boxed version, complete with printed user manual. If you don't like it, just return it.'

Call for details 01603 872331 www.spice-software.com




PicoScope 3000 Series PC Oscilloscopes

The PicoScope 3000 series oscilloscopes are the latest offerings from the market leader in PC oscilloscopes combining high bandwidths with large buffer memories. Using the latest advances in electronics, the oscilloscopes connect to the USB port of any modern PC, making full use of the PCs' processing capabilities, large screens and familiar graphical user interfaces.

- High performance: 10GS/s sampling rate
 & 200MHz bandwidth
- 1MB buffer memory
- High speed USB 2.0 interface
- Advanced display & trigger modes
- · Compact & portable
- Supplied with PicoScope & PicoLog software

Tel: 01480 396395

www.picotech.com/scope340

 

PiceStreps
Candendth
Sampling rate (reputation)
Sampling rate (single shot)
Chamiels
Challescripe timeleses
Templese accuracy
Spectrum ranges

Buffer memory size
Receiption / according
Ranges
PC Connection

3204 SOMHI 2.5655 SOMS5 2+Ext tripper Section to 50cdin

50epm 0 to 25Mg/s 256KB 100MHz 5GS:5 100MS:s 2+Est trigger Sig pas 2=5 Viv to 505 Viv 50epes 3706

200MH

10G5 a

200M5a

50mm

2 tEst Linear Street

les div to bila div

O se TOUMBLE

2205


50₇₂m 0 to 50MHz 512XB

8 kits / 8% 1100mV to 120V USB2.0 (USB1.1 compatiMal

Piconology Limited

FPGA Course (2)

Paul Goossens

 

In the first article of this series, we described the basic components of digital electronics and put them to use. In this second instalment, we introduce some components that are a bit more complicated and perform a few simple calculations using digital logic.

After reading the first part of this series, you should know enough about the basic components of digital electronics. In this instalment, we use them to do things that are a bit more useful.

Memory

Let's start off by looking at the most commonly used type of memory element: the flip-flop.

The simplest type of flip-flop is the 'set-reset' (SR) flip-flop. It has two inputs (Set and Reset) and one or two outputs (O and O). When the Set input goes to '1', the Q output also goes to '1'. That state remains unchanged even if the Set input returns to '0'. When the Reset input goes to '1', the

O output will go to '0'. That state also remains stable after the Reset input returns to '0'. The response of the flipflop is undefined if the Set and Reset inputs are both '1'. That is regarded as a forbidden state that must never OCCUI.

Figure 1 shows a schematic diagram for this type of flip-flop. It is constructed from standard components. IC1 and IC2 are NAND gates (a NAND gate is an AND gate with an inverter at its output, and an inverted output is marked by a small circle or diagonal line at the output).

Truth table

How can this be translated into a truth table? The answer is shown in Figure 2. The SR flip-flop is shown at the far left. The associated truth table shows output QN+1 instead of output Q. That indicates that this column shows the state of the output after the input signals have been processed. In some cases, the output state also depends on the previous state of the output. That is indicated here by Q_M .

Advanced forms

A slightly more advanced form of flipflop is the type known as a 'latch'. Its truth table is shown in Figure 2. This type of flip-flop has two inputs - D ('data') and Gate - and one output (Q). The Q output is the same as the D input as long as the Gate input is '1'. When the Gate input goes to '0', the Q

Part 2: Memories and calculations

output retains its value regardless of the state of the D input. It effectively stores the state of the D input at the time when the Gate signal became '0'. The next step brings us to the D-type flip-flop. The output of this type of flipflop assumes the state of the input when the signal on the CLK input changes from '0' to '1'. That is indicated in the truth table by an arrow. The output remains unchanged as long as the CLK input stays at '1' or '0'.

The D-type flip-flop can be expanded with a variety of additional inputs. Figure 2 shows such an expanded D-type flip-flop. It has three inputs in addition to the D and CLK inputs: SET, RESET and CE. The SET and RESET inputs perform the same functions as with an SR flip-flop. The clock enable (CE) input of this flip-flop controls the response to the clock signal: a rising edge on the CLK input has no effect if the CE input is not in the High state.

Trying it out

Like

The ex5 folder (included in the downloads for the second instalment on the Elektor Electronics website under Magazine/May) contains an example with various types of flip-flops. The RS flip-flop and the latch are implemented in the example in the form of logic gates. You can use the example to convince yourself that these functions can be constructed using ordinary gates. The other types of flip-flops are taken from the Quartus library.

You can use the pushbuttons to experimentally test the operation of the various types of flip-flops.

VHDL

Things really start to get interesting when you use VHDL for flip-flops. The nice thing about VHDL is that you can describe a design instead of building it with small logic elements. The program uses the description to design logic that does exactly what your description says.

Before we get into the details of the design, you need to know how the

VHDL compiler reads your description. A VHDL file describes how the outputs (and the internal signals, if any) have to respond to the inputs. For this purpose, the VHDL compiler applies every conceivable combination of input signals (in virtual form) to the inputs of your design. For each change to the input signals, the compiler attempts to determine how the outputs must respond.

That all sounds a bit abstract, but the following example should help clarify what it means.

Structure

The structure of a simple VHDL file is shown in Figure 3. The first thing you have to do is make the standard library 'visible' to the compiler. Several basic functions for digital logic are defined in the standard library.

After that, you must declare at least one entity. You can think of an entity as something like a particular type of IC. In the entity declaration, you give the entity a name (a 'type number') and define the inputs and outputs of your 'virtual IC'.

After that comes the architecture section, which describes how the entity functions.

An example

We can use an example to show exactly how all this works. The project for this example is located in the ex6 folder. Double-click on the block named Latch_VHDL. That will open the VHDL, file that describes how this particular bit of logic operates.

The declaration of an entity named Latch_VHDL starts on line 29. The inputs CLK and DATA and an output named O are declared here. These signals are all of type std_logic. That data type indicates that they are digital signals. We'll describe some other types later on.

The description of how the Latch_VHDL entity has to respond to its input signals starts on line 44.

 


Figure 1. Basic configuration of a Hip-flop using four NAND gates.

Processes

You have already seen that Boolean equations can be used to describe functions. An even more powerful approach is to use processes. In a process, you can specify the value(s) that one or more signals must assume under various circumstances.

The process keyword is followed by a sensitivity list. Each time the compiler changes the (virtual) value of any of the signal in this list, it must evaluate the code segment of the process. We'll explain this a bit later on.

If then else

The keyword if appears on line 51. It will doubtless be familiar to the programmers among our readers. This line says that if the signal on the CLK input is '1', the compiler must evaluate the code until it encounters an end if statement.

In this case there is only line in between, and it contains the statement Q < = DATA;. The whole process is terminated by an end process statement, and the end of the description is declared in line 56.

Evaluation

When the compiler evaluates the code segment, it discovers that the Q output must be the same as the DATA input as long as CLK is '1'. Nothing must happen when CLK is not '1', which

 


Figure 2. Various types of flip-flops and their truth tables.

means Q must not change. That shows how you can design a latch in VHDL.

D-type flip-flop

Now open the file D_ff_VHDL in the same way as before. Here you will see a similar file with a few crucial differences.

A new construction for the if statement appears on line 51. The construction clk'event is only true when the CLK signal changes. The construction clk'event and clk='1' is thus only true when a positive edge (low-to-high transition) is present at the CLK input. The Ω output will only assume the value of the DATA input in that situation. In all other situations, Ω will

remains the same. This is thus a description of a D-type flip-flop.

Another D-type flip-flop

The second example of a D-type flipflop has two additional inputs: SET and RESET. In the accompanying VHDL code, you can see that a test is first made to see whether reset is '1'. If it is, the output is set to '0'. Otherwise the state of the set input is examined. If it is '1', the output will go high.

If the set and reset inputs are both not '1', a test is made to see whether the clk signal exhibits a rising edge (just as in the previous example for a D-type flip-flop).

If you refer back at the start of the

process, you will see that the signals clk, set and reset appear in the sensitivity list. Output O can change if any one of these signals changes state. The set and reset inputs act asynchronously to the clk input. In other words, the device does not require a rising edge on the clk input to respond to a set or reset command.

You should also note that reset has a higher priority than set for this flip-flop. If set and reset are both '1' at the same time, reset will win the contest and the output will go to '0'.

Arithmetic

The examples up to now have used signals of type std_logic. An extension

 


figure 3. The various states of a flip-flop.

of that type is std_logic_vector, which we abbreviate as S_L_V for the remainder of this article. That type consists of a set of signals of type std_logic. You can use such a set of signals to represent a number (see inset).

There is also a type known as natural. It encompasses all positive whole numbers (integers). Doing arithmetic with signals of type natural is quite easy. You can use them for addition, subtraction, multiplication and division in VHDL.

That capability is used in ex7 to create a pulse waveform with a frequency of 1 kHz, derived from a 50-MHz clock.

Open the example and double-click on the block named pulse_generator. In the associated VHDL code, you can see how a signal of type natural is used for counting. First the ports are defined: a input signal named clk and an output signal named slow_clk. In the associated VHDL code, you can see how a signal of type natural is used for counting. This signal must be able to hold the range of values from 0 to 500,000 inclusive. The VHDL code uses these numbers to determine how many bits are required.

In the associated procedure, a test is made on each rising edge of clk to determine whether the value of the counter signal has reached the maximum value (499,999). If it has, the new value is set to '0' and the slow_clk output is set to '1'. In all other cases, the value of counter is incremented by 1 and the slow_clk output is set to '0'.

The net result is that the output goes to '1' after 500,000 clock pulses. On the next clock pulse, it returns to '0' and the cycle starts again from the beginning. If a 50-MHz clock signal is applied to the clk input, the output will briefly go to '1' a thousand times per second.

The VHDL code for calculate sum demonstrates something else that's new. First, line 25 shows that an additional library is necessary – the numeric std library. A variety of arithmetic operations and conversions are defined in that library.

The input signal a is declared in line 34. The expression $STD_LOGIC_VEC_TOR$ (3 downto 0) says that this signal set consists of four signals: a(3), a(2), a(1) and a(0). You already know that a signal set can be used to represent numbers. Making calculations with S_L_V is a bit more roundabout. The functions of addition, subtraction and so on are not defined for type S_L_V in

Binary arithmetic

Numbers can be represented using one or more digital signals. As binary signals can have only two states (1 or 0), the binary number system must be used in such cases. In normal life, we use the decimal number system (base 10). In the decimal system, a set of three numerals can be used to represent 10³ (1000) different numbers (0–999).

In the binary system, a set of three digits (signals) can represent a total of 2^3 (2 × 2 × 2 = 8) values ranging from '000' to '111', or 0 to 7 in decimal notation.

Sample calculation

1 The number '821' in decimal notation consists of $8 \times 10^2 + 2 \times 10^1 + 1 \times 10^0$. 1 Similarly, the number '101' in binary notation consists of $1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 1 \times 4 + 1 \times 1 = 5$ in decimal notation.

1 You may find the following table useful for converting between binary and deci-

23=8	22=4	21=2	20=1	Decimal	Hexadecimal
0	0	0	0	0	0
0	Ó	0	1	1	1
0	0	1	0	2	2
0	0	1	7	3	3
0	1	Ô	Q	4	4
0	1	0	1	5	5
0	1	Ī	0	6	Ó
0	1	7	Į.	7	7
1	0	0	0	8	8
1	Ö	0	1	9	9
1	0	1	0	10	А
1	Ö	1	1	11	В
1	7	0	0	12	C
1	1	. 0	1	13	D
1	1	1	0.	14	Ε
1	1	1	1	15	F

Hexadecimal notation

Relatively large binary numbers are generally difficult to comprehend due to the large number of ones and zeros. Hexadecimal notation (base-16 number system) can be used to make them easier to understand. That notation uses the numerals 0–9 and the letters A–F, with A representing the decimal value 10, B the decimal value 11, and so on. See also our Hexadoku puzzle! A single character can thus be used to represent 16 different values. That corresponds to four bits in the binary system.

Active High and Active Low

Many components have 'active Low' inputs. That means the input is 'active' when the logic level at the input is Low.

For instance, a flip-flop with an active-low Reset will be reset when a logic Low signal is applied to the Reset input. Active-low inputs can be recognised by the small circle or triangle at the input concerned. An 'inversion bar' can also be placed above the name of the input to indicate that it is active low, such as RESET

It's also possible for outputs to be active Low. Such outputs can similarly be recognised by the inversion bar over the name or a small circle or slanted line at the output.

VHDL. However, they are defined in the numeric_std library for some other types, including unsigned. Several useful conversion routines are also located in that library.

The expression UNSIGNED (a) converts the set of signals a(3)...a(0) to type unsigned.

A set of signals of type unsigned can be converted to type S_LV in the same manner.

You can see all that on line 49. There the two input signals a and b (each of which is a signal set) are converted to type unsigned. The two values are added together, which yields a result of type unsigned. Finally, that result is converted to type S_LV . These signals are also linked to the SUM output. This thus amounts to a simple addition function.

A subtraction function is described in the same manner in calculate_dif.

Busses

The two blocks are interconnected in the Quartus schematic by several signal lines originating from dipswitch S5. The input port, DIPSWITCH[3..0], consists of four independent input lines with the designations DIPSWITCH[3], DIPSWITCH[2], etc. This deviates from the VHDL standard with regard to the notation for a set of signals.

This set of signal lines can also be connected using a bus instead of individual signal lines. You can draw a bus in Quartus by using the Bus Tool instead of the Node Tool. A bus is shown in a schematic diagram with a thicker line than individual signal lines.

The schematic diagram here has several busses, some of which are connected to a port at only one end. Quartus regards all signals with the same name as being linked together, so it isn't necessary to connect all the associated lines together.

Multiplexing

The 7-segment displays must be driven one at a time. Only one segment can be on at any given time. This sequential drive is provided by the sequencer block.

In the count process in sequencer.vhd, you can see that the internal_select signal is incremented by 1 each time each time a rising edge occurs on the clk line when the clk_en input is '1'. In the schematic, clk_en is connected to a signal line that goes to '1' once every 500,000 clock pulses. As a result, the internal_select signal is incremented 100 times per second (50 MHz ÷ 500,000).

Line 66 shows a new feature of VHDL. It says that the sel1 signal must go to '1' if the counter value is '0', and otherwise the sel1 output must be '0'. Signals sel2 to sel4 are generated in the same way. As a result, these outputs

go to '1' sequentially. The counter value is also output via the sel signal (line 72).

Signals self-sel4 drive transistors T1-T4 on the prototyping board to enable the various groups of LED segments.

In step

This example is designed to display four different numbers. The numbers must be output sequentially, synchronised with the drive signals for transistors T1–T4. The sel[1..0] signals from the sequencer can be used for this purpose.

The mux block takes care of all this. The current output is enabled by the four inputs (val1, val2, sum and dif) according to the value of the sel signal. The keyword when appears in line 52 of the associated VHDL code. In that line, the current output is enabled by the val1 input if the value of sel is '00' (0). Similarly, the output is enabled by val2 if sel is equal to '01' (1), and so on. Once again, the final enable is provided here by the else keyword.

Decoding

The current output contains the value to be shown on the display. This value is also nicely synchronised with the drive signals for the individual groups of LED segments.

The value of current is available in binary form, so the individual LED segments must be driven based on this binary code. The value '1' must be shown on a 7-segment display by driving segments b and c. To display the value '0', segments a-f must be driven. That means the binary values must be converted into the proper drive signals for the various segments.

This last bit of processing is handled by the block named to seven segment. In the VHDL code for that block, you will see another new keyword: case. The line CASE val IS says that the value of val determines how the following bit of code is to be processed. You could read line 50 as 'if val has a value of '0000', then the following must happen'. The software will then evaluate the subsequent lines of code until it encounters the next when keyword.

In line 51, you can see that this causes the value '1111110' to be assigned to the segments out output. In other words, segments a—f are driven on and segment g is not driven. The numerals 1—9 and the digits A—F (for hexadeci-

Earlier in this series

Versatile FPGA Module, Elektor Electronics March 2006.

FPGA Prototyping Board, Elektor Electronics March 2006.

FPGA Course (1), Elektor Electronics April 2006 (with free downloads).

mal display) are decoded in a similar manner.

Finally, the end of the case statement is indicated in line 84.

Testing

The best way to understand the previous explanation is to try it out in practice. To do so, program the FPGA unit with the example program in ex7. If everything goes right, you will see several numbers appear on the 7-segment displays. few changes to the code of the example. For instance, you can change the order of the numbers, or instead of calculating the difference of two numbers, you can calculate and display the product of the two values (multiply = ' in VHDL).

The ex8 folder con-



Digital arithmetic in practice

All digital devices calculate using the binary number system, even if their users are not aware of the fact. The arithmetic processes are often considerably more complex than simple addition.

Your personal calculator is a good example of what can be done with digital arithmetic. Besides normal arithmetic operations, it can also be used for relatively complex calculations such as sine, cosine, square root, and so on.

An example of a more practical application of this arithmetic capability is a digital control system for a rocket. A considerable amount of real-time calculation is necessary to accurately send a rocket into space along its intended path.

Yet another example is your DVD player. It takes a lot of mathematical calculations to transform the compressed data on a DVD into a nice picture on your screen. All those calculations are performed by a processor. Naturally, that's a digital processor, and it calculates (lightning fast) using only binary numbers.

You can use switches 0-3 of S5 to assign a value to val1. It will be shown on the display at the far left. You can similarly use switches 4-7 to assign a value to the second number.

The third number on the display shows the result of adding the two input values, and the last number shows the difference between the two values.

Experimenting

To familiarise yourself with this approach to designing, try making a

folders with even more examples. Now that you've read this article, you should be able to figure out how these examples work. Try out each of them in turn, and study the associated code to discover how they work. That's the only way to become fluent in VHDL!

050005-20



An R8C-based Oscilloscope RBC/13 Scope Tom Thumb as a software 'scope Burkhard Kainka and Olaf Kaluza

The previous instalments of our R8C 'Tom Thumb' series concentrated on explaining the basic functions of the R8/13 system. Now it's time to look at some real applications. The objective here is to develop a small oscilloscope in two forms: first on a PC, and second as a stand-alone device with its own graphic display.

Many 'real' PC oscilloscopes can achieve sampling rates of up to 20 MHz, but usually with 8-bit resolution. Simple implementations using a sound card typically have a sampling rate of 48 kHz or so. However, sound cards cannot process DC signais. One way to remedy this situa-

tion is to use a microcontroller with an A/D converter.

A PC storage oscilloscope

The objective is to have the R8C/13 take samples as rapidly as possible, buffer the measured values in RAM,

and then transmit them to the PC at a high baud rate. To keep the conversion time short, the A/D converter will be operated in 8-bit mode. In theory, the maximum memory depth is nearly 1000 bytes. However, only 500 bytes: are used here, because a conflict with the memory demands of the KD30

 


Figure 1. The analogue inputs are protected by $10-k\Omega$ resistors.

```
Data acquisition using the R8C/13 ('Scope1' project)
unsigned char ad buf[500];
unsigned char ad in(unsigned char ch)
    adcon0 = 0x80 + ch;
                                          //Port P0 group
    adcon1 = 0x20;
                                          //8-bit mode
    adst = 1;
                                          //Conversion start
    while(adst == 1)()
                                          //Wait A/D conversion
    return ad;
                                          //AD value
void sample(unsigned int ch)
  unsigned int adr;
  for (adr = 0; adr < 500; adr++)
     ad buf[adr] = ad in(ch);
      for (adr = 0; adr < 500; adr++)
     sendTxd0(ad buf[adr]);
void main(void)
  while (1)
     sample(receiveRxd0());
```

debugger could easily arise with a larger data volume.

The 'Scope1' project (see Listing 1) uses the UART0 serial interface port of the microcontroller. That leaves UART1 free for the debugger. The data transmission rate is set to 38,400 baud. The A/D converter can use the seven available channels (AN0-AN6), which are located in port 0. As the LCD is not used for this application, all seven channels are available.

Data communication is governed by the following protocol. The PC first transmits a single byte containing the desired channel number (0-6). The R8C/13 then takes 500 individual samples and stores the results in its data buffer. At the end of the measurement process, all 500 bytes are transferred directly to the PC. The sampling rate is approximately 100 kHz, which is suitable for general measurement tasks. It is highly recommended to fit $10-k\Omega$ protective resistors in series with the inputs of the individual channels (Figure 1). That will avoid any risk of damage to the microcontroller if an excessive voltage is accidentally applied to an input. The potentiometer connected to analogue channel 6 can be put to good use as a zero-reference control for measuring AC signals. Additional smoothing of the supply voltage may necessary, because the voltage drop across the Polyswitch fuse (F1) creates noise on the V_{CC} line and thus on the reference voltage for the A/D converter. A 100-µF electrolytic capacitor connected to V_{CC} will provide adequate smoothing.

Displaying measurement data in Visual Basic

On the PC side, a small Visual Basic (VB) program looks after displaying the measured values. The VB project was generated using VB5, and it can also

```
Listing 2

Data reception in VB

Private Sub Command1_Click()

TIMEINIT

SENDBYTE 1 :... Ch

DELAY 200

For n = 0 To 500

a = READBYTE()

Chi(n) = Int(a)

Next n

Plot

End Sub
```

 


Figure 2. An oscillogram on the PC monitor.

be compiled using VB6. The accompanying exe file was generated using VB6. The user selects the desired input channel and starts a measurement session by pressing the 'Start' button. Automatic repetitive measurements can enabled instead by pressing 'Auto' (see Figure 2). The 'Spectrum' button selects a Fourier spectrum display as described in the next section.

The procedure for requesting and receiving the data (Listing 2) stores the incoming 500 bytes in a data array designated Ch1(n), from which the data is passed to the output routine ('Plot').


Fourier analysis

When measurement data is available in digital form, the spectral components of the signal can be calculated and displayed using Fourier analysis. In simplified terms, that consists of multiplying the actual waveform by a sine wave with a known frequency.

Sample projects on the Web

The serial interface and A/D converter are highly versatile in use, as can be seen from several projects described on the R8C Info pages (accessible from the Quick Service menu on www.elektor-electronics.co.uk). You can also download the sample projects from the Service page. If you're looking for a new application for your microcontroller, you're bound to find something useful there. Contributions are welcomed!

Figure caption: A PC oscilloscope using the R8C/13

 

 


Figure 3. Frequency spectrum of a 1-kHz square-wave signal.

The result indicates the amplitude of the signal component at that frequency that is present in the original signal. However, this requires a considerable amount of computation. If 500 samples are present, 500 sine-wave values must be calculated for each frequency and multiplied by the measurement data. The whole process must actually be performed twice, because the unknown phase offset of the measured signal makes it necessary to perform two analyses with a phase difference of 90 degrees. After that, the two output values must be processed by vector addition to obtain their joint magnitude. To avoid generating measurement errors due to the abrupt termination of the signal at the edges of the measurement window, it is recommended to first process the measurement data using a rounded window function.

This analysis is normally performed

with a 'fast Fourier transform' (FFT) using the butterfly algorithm. Although the FFT may be fast, it is complicated and requires quite a lot of memory. Nevertheless, our objective later on will be to copy the algorithm used for this purpose as exactly as possible from the VB code into C code compiled for the R8C. Consequently, we use a simple digital Fourier transform (DFT) here. Listing 3 shows the conversion routine that processes the time sequence in Ch1 into a frequency spectrum in Ch2. The edges are rounded using a Hann window before the actual transformation takes place. Figure 3 shows the spectrum of a 1-kHz square-wave signal as displayed in the program window.

Graphic LCD

The graphic LCD really turns the R8C/13 into a powerful system. With it in place, the PC is only needed for programming, and an application such as the simple oscilloscope described here can run fully independently on the microcontroller system. Here we use a type 64128E from Displaytech (distributed by Glyn, and available from AK MODUL-BUS and Geist Electronic as well). The display has a resolution of 128 × 64 pixels and requires a supply voltage in the range of 3 V to 3.6 V (maximum). It can be driven either in parallel or serially via an SPI interface. Parallel operation would occupy too many port lines in this case. The LCD. is thus operated in serial mode here, which also simplifies the connection. The sample project described here ('LCD64128E') specifically requires the indicated display type. Unfortunately,

('LCD64128E') specifically requires the indicated display type. Unfortunately, there is no commonly used type of 'standard' controller for graphic displays, but instead a wide variety of types. In this case, the controller is the KS0713 from Samsung. The specified 3-V operating voltage means that the control lines must also be driven using 3-V signal levels. There are two ways to do that. One way is to use a 3-V supply voltage for the R8C/13 as well, and the other way is to use suitable level converters – which in the simplest case can be voltage dividers formed by pairs of resistors. These two options are illustrated in Figures 4 and 5.

An extra 3.3-V voltage regulator can be used to operate the R8C/13 at a reduced voltage, as shown in Figure 5. However, there's an even simpler option. For initial testing, it's sufficient to connect two 1N4004 diodes in series

```
Listing 3
Fourier analysis in VB
```

```
Private Sub Transform()
  For n = 0 To 500
        Ch2(n) = (Ch1(n) - 127) * (1 - Cos(n * pi / 500)) 'Hanning
Window
  Next n
  For k = 1 To 500
        r = 0
        i = 0
        For j = 1 To 500
        r = r * Ch2(j) * Sin(k * j / 380)
        i = i * Ch2(j) * Cos(k * j / 380)
        Next j
        Ch1(k) = 1 / 100 * Sqr(r * r + i * i)
        Next k
End Sub
```

with the 5-V supply lead. With a voltage drop of approximately 0.7 V per diode, the supply voltage for the R8C/13 and display is reduced to 3.6 V (5 V - 1.4 V), which is within the allowed range for the display. The diodes can be fitted very easily by preparing a 'special' jumper for JP11 on the application board, with the two diodes wired in series between the contacts. Incidentally, we accidentally operated the display for a very short time at 5 V without any adverse effects. It thus appears to be able to survive such mistakes.

To enable the display to be driven in serial mode, you must bridge jumper JP3 on the back of the LCD circuit board with a drop of solder.

The signal lines required for serial data transmission are:

DB7 = SID	to TXD0/P14
DB6 = SCLK	to CLK/P16
/CS1B	to P1.3
RS.	to P1.7
E	to ground
R/W	to ground
RST	to Reset or fitted with its own reset circuit

The Reset line can be connected to the R8C/13 microcontroller Reset line. The display also has a white backlight LED that draws a current of 20 mA.

 


Figure 4. Display connection with reduced VCC.

 


Figure 5. LCD connection with a 3.3-V voltage regulator.



Figure 6. Outputs from the sample project.

 


Figure 7. An oscillogram on the LCD.

The sample project for serial operation (LCD64128) implements two different serial drive methods: using the synchronous UARTO (SPI port) of the R8C/13 or using direct port instructions, which take more time. The project supports both options. The directive '#define SYNCUARTO' selects fast SPI transmission with a clock rate of 1.6 MHz.

Unfortunately, the display RAM cannot be read back in serial mode, so a large 'shadow RAM' (1024 bytes) would normally be required. Here we use a trick in ks0713.c instead. It consists of storing only the most recently used bytes in a relatively small buffer. If a suitable sequence is chosen, characters and lines can be generated in this manner without overwriting previously generated elements.

The instruction '#define LCDSIZE 128' in file ks0713.h configures a buffer with 128 entries, which requires 384 bytes of memory. That value can be reduced if RAM space is tight. When you want to set a pixel, the function 'bitbuffer' first checks whether other pixels have already been set in the corresponding byte of the display before it sets the bit for the new pixel. However, the old bits will be lost if the routine encounters a location that could not be saved previously in memory.

A description of the details of the driver would exceed the scope of this article. However, the project code is carefully commented, so if need be you can figure out for yourself how it works. Here we limit ourselves to brief descriptions of the functions provided by the driver, which you can use to create your own projects.

lcdg_init();

Initialises the display

lcdg_drawpixel(x,y,BLACK);

sets a pixel at position (x, y)

lcdg_line(x1,y1,x2,y2,BLACK); draws a line from (x1, y1) to

(x2, y2)

lcdg_circle(x,y,r,BLACK);

draws a circle with origin (x, y) and radius r

lcdg_box(x1,y1,x2,y2,BLACK);

draws a rectangle with corners (x1, y1) and (x2, y2)

ks0713_invert();

inverts the entire content of the display

ks0713 normal();

switches back to non-inverted display

ks0713 clrscr();

clears the display

```
oprintf("%z%qText",x,y);
    writes a character string at
    location (x, y)
oprintf("%z%q%d",x,y,n);
    writes the integer n at location
    (x, y)
```

The oprintf function is a simplified version of the normal printf function in C. It can output integers as well as character strings. To keep the code size within limits, we omitted support for real numbers. The char8.h character set is supported with an 8×8 pixel matrix.

The sample project illustrates the capabilities of the display and generates the pixel graphic shown in Figure 6. It includes a line, a circle and a rectangle. Finally, a character string is output, including an incrementing number. The entire display is inverted after 20 passes through the routine and then restored to the normal state after another 20 passes. The example also demonstrates the limitations of the memory-saving graphics algorithm: a small portion of the drawn rectangle is erased by the superimposed text.

A mini oscilloscope

Now that all the necessary tools are ready, we can put together a small oscilloscope with an LC display. The data acquisition function is nearly the same as for the PC oscilloscope. However, in this case we only have to acquire 128 bytes. The entire LCD area is used to display the results (Figure 7).

As we need memory space to store the measurement data, the size of the auxiliary RAM for the display must be reduced In this case, good results can

Listing 4

Measurement and display on the LCD ('LCD64128Scope' project)

```
void main(void)
{
   unsigned int adr;
   maxspeed();
   delay(10000);
   lcdg_init();
   while (1)
   {
        ;trigger();
        for (adr = 0; adr < 128; adr++)
        {
            ad_buf[adr] = (ad_in(6));
        }
        ks0713_clrscr();
        for (adr = 0; adr < 127; adr++)
        {
            lcdg_line(adr, 63-ad_buf[adr]/4, adr+1,63-ad_buf[adr+1]/4,
        BLACK);
        }
        delay(10000);
    }
}</pre>
```

Listing 5

Trigger function ('LCD64128Scope' project)

```
void trigger (void)
{
   int start;
      start = 0;
   while (pl_0 & !start)
   {
      while (ad_in(6) > ad_in(5));
      while (ad_in(6) < ad_in(5));
      start = 1;
   }
   while (pl_1 & !start)
   {
      while (ad_in(6) < ad_in(5));
      while (ad_in(6) > ad_in(5));
      while (ad_in(6) > ad_in(5));
      start = 1;
   }
}
```

Serial interface timing

The program generates a 200-ms delay after sending the Start command. A shorter delay was initially configured here, since the actual measurement takes only 5 ms. After that, Readbyte receives the characters as fast as they arrive. A timeout value of 10 ms applies to the reception of individual bytes. Each byte, with its eight data bits, start bit and stop bit, takes 0.26 ms [10 × 1/38,400 s], so there shouldn't be any problem. However, timing problems did occur with some relatively recent PCs and a few USB/RS232 adapters. It turned out that the data stream is temporarily stored in a buffer with a size of 64 bytes or so and then transmitted as a block in a USB frame. No problems occurred with the Prolific IC on the application board, but some recent-model PCs are no longer fitted with a 'normal' RS232 interface using a 16550 IC. Instead, they have a virtual COM interface that presumably also uses USB internally and exhibits exactly this buffer behaviour. That can cause time gaps in the received data stream, which in turn lead to timeouts. The 200-ms delay solves this problem by providing sufficient time for all the data to be received by the serial interface and stored in the receive buffer. After that, the VB program can read out the data at full speed.

 


Figure 8. Controls for the trigger function.

be obtained with '#define LCDSIZE 8'.

The actual measurement process requires only a few lines of code (Listing 4), which makes for rapid display

of the results. The displayed curve consists of a large number of short line segments, each of which joins two sample points.

Triggering

A proper oscilloscope also requires a trigger function. The function 'trigger' provides the necessary capability in the code (Listing 5). An additional potentiometer is connected to AD 5 to set the trigger level. Two pushbutton switches are also needed (Figure 8). Triggering occurs on the negative edge if P1.0 is pulled high and on the positive edge if P1.1 is pulled high. If you use the LEDs on the application board, you get a trigger indication for free in the bargain - something you otherwise can only hope to find at the upper end of the price scale. Incidentally, you can adjust the trigger level of this oscilloscope during operation, just as with its analogue cousins, until a signal is displayed. If you can't manage to trigger on a signal, simply open the trigger switch and operate the 'scope in freerunning mode.

Fourier analysis in the R8C/13

If you want to use mathematical functions such as sine and cosine with the R8C, you have to use a library (refer to our 'C Booklet' supplied with the March 2006 issue). The directive

Listing 6

Fourier analysis using the R8C/13 ('LCD64128Spec' project)

```
while (1)
    for (adr = 0; adr < 256; adr++)
         ad buf[adr] = (ad in(6));
    for (adr = 0; adr < 256; adr++)
         ad_buf[adr] = ((ad_buf[adr]-127)*(1 - cosf((float)adr * PI / 128))/2+ 127);
    ks0713 clrscr();
                                                                    q. many
    c old = 0;
    for (k = 0; k < 129; k++)
      x = 0;
      i = 0;
         for (j = 0; j < 256; j + +)
          r = r + ((ad buf[j]-127) * Sintab[(k * j / 4) & 255]) / 128;
           i = i + ((ad buf[j]-127) * Sintab((k * j / 4 + 64) & 255)) / 128;
         r = (int)sgrtf(((float)r*(float)r*(float)i*(float)i));
         c = r/200;
        //c= ad buf[k]/4;
        lodg line(k, 63-c old, k+1,63-c, BLACK);
        c old = c;
     delay(10000);
```

#include "mathf.h" allows you to use functions such as sinf, cosf and sortf for floating-point ('float') values, which require less memory than the usual functions for the 'double' format. However, they take up considerably more space in ROM. In its default configuration, the compiler is limited to a maximum program size of 8 KB, so the start of ROM must be moved down from 0e000H to 0c800H. That leaves enough room for the firmware of the KD30 debugger. Line 609 of file 'Sect30.inc' must be modified accordingly. Incidentally, the entire LCD64128Spec project generates a code volume of 10,950 bytes.

.section rom_NE,ROMDATA
.org 0c800H

"mathf.h" is important here. Although the source code will compile without an error message if it is missing, the mathematical functions used in the code will not work properly. It's also important to pay attention to uppercase and lower-case characters, because only floating-point values can be passed to the functions. The conversion function 'float(adr)' converts the integer variable 'adr' into a real number in floating-point format (Listing 6).

 


Figure 9. A Fourier analysis without the Hann window.

The sample project shows that working with C for the R8C/13 is just as easy as using Visual Basic for the PC. However, due to time constraints the actual computation loop for the Fourier transform has to manage without the sinf function, because 65,536 sine calculations and multiplications would simply take too long. A pre-calculated sine lookup table is used instead. That

reduces the computational effort to 65,536 multiplications in 16-bit format, which the R8C manages without batting an eye. By contrast, the 256 cosf calls for the Hann window and 128 sqrtf calls for the vector addition do not cause any objectionable delay. The full screen display is generated in a fraction of a second.

(050173-5

See your design in print!


Elektor Electronics (Publishing)

are looking for

Freelance Technical Authors/Designers

If you have

- * an innovative or otherwise original design you would like to see in print in Europe's largest magazine on practical electronics
- * above average skills in designing electronic circuits
- * experience in writing electronics-related software
- * basic skills in complementing your design with an explanatory text
- * a PC, email and Internet access for efficient communication with our in-house design staff;

 


Elektor Electronics

David Daamen, Head of Design Dept.

P.O. Box 75, NL-6190-AB Beek, The Netherlands, Fax: (+31) 46 4370161

Email: d.daamen@segment.nl

 

E-blocks for Protot Design an E-blocks controlled PSU

Many readers have asked how they can make their own E-blocks. This month we take a look at some options on making your own prototype E-blocks and give you some suggestions for E-blocks that we would like to see.

 


Figure 1. Our cigarette packet plan.

The first step to making an E-block is to get some hardware up and running. Before you do that you need some kind of plan for what you want to make. Usually with electronics this means you have to draw up a circuit diagram. To make your initial design you will need to draw on information from datasheets: the datasheets on the development equipment you are using and the datasheets on the electronic components you plan to use. Your schematic can take many forms - from a Computer Aided Design (CAD) schematic, to a sketch on the back of a cigarette packet. For the sake of this article we have gone for the 'cigarette packet' approach that you can see here. On the cigarette packet in Figure 1 you can see my ideas for a simple benchtop instrument containing a basic E-blocks logic analyser and a voltage-variable power supply. As well as being a useful instrument, I am hoping this will help me learn a little more about analogue electronics.

At this stage of a project I like to make sure I have all the information I am likely to need: which pin numbers on the ICs correspond to each signal lines, pinout of the transistors, etc. You can see that even on this simple diagram there is quite a lot of information.

My plan

At the heart of the system is a 16F877 40-pin PICmicro with 20-MHz crystal oscillator and two push-to-make switches on E0 and E1. A two-line 16-character alphanumeric LC display is connected to port B of the PICmicro. Port C of the device is connected – via 330-ohm resistors – to an E-blocks port (not shown) on the left of diagram. I plan to use the first line of the LCD dis-

play to show me the status of the lines on Port C in both binary and hex formats. Later I might also use this for monitoring 12C or SPI bus commands, which is why I chose port C as it is internally connected to the PIC USART serial asynchronous (universal receiver/transmitter). A good old 7805 regulator will create 5 V for the circuit from a spare 16-V 'rat's-tail' power supply I had in the drawer. I have used an SPI-bus 256-step potentiometer - the MCP4101 from Microchip - and connected it to C3 (clock), C5 (data) and B7 (chip select) of the '877. The $10-k\Omega$ 4101 is the bottom part of a potential divider, with a 10-k Ω resistor to +5 V. This produces an output from 0 to 2.5 V in 256 steps. This signal is amplified by a LM324 opamp powered off the 16-V input to produce an output between 0 and (hopefully) 16 V. A simple TIP142 NPN Darlington transistor - effectively

yping Systems

John Dobson

an emitter follower - then provides the power supply output. The emitter of the Darlington is fed to a $0.5-\Omega$ resistor and then to the screw terminal output connector. A differential amplifier will amplify the voltage across the 0.5- Ω resistor, allowing me to make a display of the current output. This will feed into pin A1 of the '877. The output voltage is also divided down by potential divider chain to produce a signal between 0 and 3 V which is directly proportional to Vout. This is connected to pin A0 of the '877. So I can have the software calculate and display both the output voltage and current of the power supply. I plan to produce all of the code for this using Flowcode.

Getting started

My first aim is 'proof of concept' and 'technical risk': I want to know if the idea is likely to work and test the core components: particularly the linear potentiometer which I have never used before. We are going to base our initial prototype on the E-blocks system, as we have a PICmicro programmer, displays, switches, which all connect together very quickly. All we need to do is prototype the parts of the circuit that we don't have: the MCP41010 design, the opamps. I won't bother to prototype the output stage just yet as I am more confident about that part of the design. It makes sense to me to get the 41010 working first as I have never used it and to test the fundamental theory of our design and get the values of the resistors in the op-amps right. The MCP41010 and the LM324 can be seen in close-up on Figure 2, and you can see the initial prototyping E-blocks system in Figure 3.

In Figure 3 you can see we have an E-blocks PICmicro Multiprogrammer with an LCD display on port B, some switches on port D, and port A and C feeding onto the prototype board containing our 41010 and LM324 circuit. Once the circuit diagram was established this only took around 15 minutes to construct.

Here is a hint: in Figure 2 you can see that we are using a pack of small multi-strand leads with rugged gold end terminals to make the connections

 


Figure 2. The MCP4101 and the LM324 happy together on a prototype board.

on the prototype board. You can use single core wire for this quite adequately, but if you are going to do this frequently then the proper leads are worth investing in: the single core wires have a tendency to snap off inside your Protoblock, and they are slightly too large for inserting into

turned-pin sockets which are almost universally used for prototyping. Note also that on the prototype board shown there are

- · two E-blocks D-type connectors;
- two terminal screw connectors for power and ground;
- · two single inline 9-way turned pin

 


Figure 3. The E-blocks prototyping system.

 


Figure 4. The final design on a patch board.

sockets for both E-blocks ports;

 a patch area to the right of the Protoblock for connecting the more awkward components that won't fit onto your Protoblock, these include potentiometers and surface mounted components (SMDs).

Patch boarding

The problem with the Protoboard approach is that is it only temporary —

once your design is proven then you need to find a more permanent way of developing your project. You have a number of choices here:

- develop a custom printed circuit board (the best method, but time consuming and expensive);
- use stripboard a.k.a. veroboard or perfboard (yeuch!);
- · use what we call a patch board.

Patch boards simply consist of a bare

circuit board with a large number of plated through holes onto which you solder your final circuit. Once you are confident of your design, you can simply go ahead and solder the components on and wire them up - if you do make a mistake then it is easy enough to remove the components. Note that some people use patch boards for the first prototype, but it does take longer to correct mistakes. The great advantage of the patch board system is that, as all the components are soldered onto the board, it is more rugged and essentially makes a more permanent E-block component.

In Figure 4 you can see the final design on an E-blocks patch board. This has an E-blocks connector on the top and all the components mounted onto the board and soldered in place. When it comes to wiring, you also have some choices: you can use coloured single-core wire, which provides a strong and easily traceable circuit, but can get messy when you have lots of connections (note on this design there are around 50 wires). I prefer another approach which is much, much faster: if you look at Figure 5 you can see that I have used what is called 'wiring pencil wire'. This thin wire has a layer of polyurethane insulating coating that burns away with a soldering iron to reveal the copper wire beneath. To use it you just apply the soldering iron for a second or so and then solder it to the appropriate component pin. I don't

 


Figure 5. Close up of the bottom of the patch board showing wiring and SMD components.

Earlier in this series

Electronic Building Blocks, November 2005.

E-blocks and Flowcode, December 2005.

E-blocks in Cyberspace, January 2006.

E-blocks - now you CAN, February 2006.

E-blocks Making Waves, March 2006.

E-blocks Making Waves at C, April 2006.

Articles may be downloaded individually from our website.

For a complete overview of available E-blocks visit the relevant SHOP pages at

www.elektor-electronics.co.uk

Call for Papers Here are a few suggestions for E-blocks projects we would like to see:

DMX • RFID • Zigbee • Joystick • Camera • SRD RF transceiver • Compass • Real-time clock • FPAA interface • Colour sensor • 8051 • Z80 • PC E-block.

Readers are invited to submit outlines and detailed propositions for any of the above projects.

know of a faster way of making a circuit and the results are surprisingly rugged. In Figure 5 you can see that I have also used some surface-mounted components on the bottom side of the patch board.

Design summary

The design itself seems to work fairly well. The collector-emitter drop on the Darlington was more than I expected and I ended up with an output range of around 0 to 12 V rather than the desired 0 to 16 V. I tested the design with a resistive load (ah the aroma of burning resistors) and drew around 350 mA. I did not get round to develop-

ing the current monitor circuit and software, and my voltage algorithm in Flowcode only gave an integer read out. Room for improvement in the programming department!

I was impressed by the ease of use of the Microchip MCP4101 device and will certainly use it again. If you are going to use it make sure you have the most recent SPI components for Flowcode installed. An article on SPI was published in last month's Elektor Electronics.

Conclusion

From this brief article you have hopefully seen the steps you need to take to make your own E-blocks board, and also how you can take a project from the initial prototyping through to a finished item.

We are always looking for new project ideas for E-blocks and we have a large number of new boards coming in the next few months (including Bluetooth, Bluetooth CODEC, SD/MMC card reader, motors, LIN, PS2/VGA, optoisolator, USB/RS232, MP3, GPS, and relay). However, there are a several other functions that we would like to see in E-blocks format listed above. If you are interested in developing a project for these – including the code for a PICmicro based in C – then please contact the Editor.

CONSTRUCTION GUIDELINES

Elektor Electronics (Publishing) does not provide parts and components other than PCBs, and preprogrammed ICs (not necessarily for all projects). Components are usually available from a number of retailers – see the adverts in the magazine. Selected projects are supplied as kits.

Large and small values of components are indicated by means of one of the following prefixes:

$E(exa) = 10^{12}$	$a (atto) = 10^{-18}$
$P(peta) = 10^{15}$	$f(femto) = 10^{-15}$
$T (tera) = 10^{12}$	$p (pico) = 10^{-12}$
$G (giga) = 10^9$	$n (nano) = 10^{-9}$
$M \text{ (mega)} = 10^{6}$	μ (micro) = 10-5
$k \text{ (kilo)} = 10^3$	$m \text{ (milli)} = 10^{-3}$
$h (hecto) = 10^2$	c (centi) = 10^{-2}
da (deca) = 100	d (deci) = 10-1

In some circuit diagrams, to avoid confusion, the value of components is given by substituting the relevant prefix for the decimal point.

For example,

$$3k9 = 3.9 \text{ k}\Omega$$
 $4\mu\text{F7} = 4.7 \mu\text{F}$

Unless otherwise indicated, the tolerance of resistors is $\pm 5\%$ and their rating is $\frac{1}{2}$ - $\frac{1}{2}$ watt. The working voltage of capacitors is ≥ 50 V.

In populating a PCB, always start with the smallest passive components, that is, wire bridges, resistors and small capacitors; and then IC sockets, relays, electrolytic and other large capacitors, and connectors. Vulnerable semiconductors and ICS should be done last.

Soldering. Use a 15-30 W soldering iron with a fine tip and good quality solder tin. Insert the terminals of components in the board, bend them slightly, cut them short, and solder; wait 1-2 seconds for the tin to flow smoothly and remove the iron. Do not overheat, particularly when soldering ics and semiconductors. Unsoldering is best done with a suction iron or special unsoldering braid.


Faultfinding. If the circuit does not work, carefully compare the populated board with the published component layout and parts list. Are all the com-

ponents in the correct position? Has correct polarity been observed? Have the powerlines been reversed? Are all solder joints sound? Have any wire bridges been forgotten?

If voltage levels have been given on the circuit diagram, do those measured on the board match them – note that deviations up to $\pm 10\%$ from the specified values are acceptable.

Possible corrections to published projects are published from time to time in this magazine. Also, our online Forum often contains useful comments/additions to the published projects.

 The value of a resistor is indicated by a colour code as follows.



Examples: brown-red-brown-gold = 120Ω , 5% yellow-violet-orange-gold = $47 k\Omega$, 5%

UV LED Light More efficient PCB exposure

Reinhardt Weber

Commercial PCB exposure light boxes usually employ gas discharge tubes as an ultraviolet (UV) light source, these devices are however bulky, fragile and costly. Incandescent lamps are not a good alternative; they produce a lot of heat and relatively little UV. An interesting development boasting high efficiency and excellent reliability is the recently introduced UV LED.


This design will be welcomed by anyone considering homebrew PCB production, it uses the L-7113UVC type UV LED from the 'Super Bright LED Lamps' range by Kingbright to build a UV light box. The emission wavelength of this LED is precisely 400 nm, ideal for transferring a mask pattern to the photo-resist layer of coated PCBs. The maximum LED forward current is quoted as 30 mA, producing a voltage drop of 4.2 V.

The entire light source is made up of 24 diodes arranged in a grid pattern to ensure even illumination across the Eurocard sized PCB. The beam angle for this LED is given as 20 degrees. Beam edges are defined as points in the radiation pattern where the luminous intensity has fallen 50 % compared to its peak at the centre of the beam. The LED grid spacing is chosen to ensure that the overlapping light cones produce an even distribution of light over the complete area of exposed PCB.

Figure 1 gives the exposure time as a

Figure 1.

 Correlation of LED spacing, distance to the glass platen and exposure time.





Eurocard illumination

material.

Placing the LEDs closer together allows a shorter distance between the LEDs and the glass platen. This would increase the UV intensity and reduce the PCB exposure time but at the expense of more LEDs, as ever we run into the speed verses cost trade off. The LEDs in this design are arranged in a grid on a Eurocard sized PCB with a spacing of approximately 31 mm. The total number of UV LEDs required for this 100 mm x 160 mm card is 24 (Figure 2). At a distance of about 80 mm between the LEDs and the glass platen the light exposure time for a PCB was found to be around six minutes.


and to some extent the age of the

The optimal distance between the LEDs and glass platen to give an even light distribution can be determined empirically; put on a pair of UV protection glasses and place a sheet of white paper over the glass platen, move it away from the LEDs until the individual pools of light overlap to form a uniform area of illumination on the sheet. The distance can be increased to cover a greater area but the PCB mask exposure time will need to be increased correspondingly.

Circuits don't get much simpler

The electrical assembly work for this design involves little more than soldering the LEDs to suitable series resistors. The LEDs are wired as 12 pairs, each with a single 120 Ω series resistor connected to the 12 V input (Figure 3). Each pair draws about 25 mA so the 12 V mains adapter must be capable of supplying a total of around 300 mA. The reverse breakdown volt-

Figure 2. LED layout on the Eurocard sized PCB.

 

has also produced a Eurocard sized PCB for the circuit (Figure 2 and Figure 3) and also a half size board containing 12 LEDs. Both of the layouts can be downloaded from www.elektorelectronics.co.uk free of charge, the file number is 060029-1.zip (see articles listed for this month May 2006).

Construction

Before any components are mounted on the board it is necessary to apply some form of reflective layer to the board surface. This can be self adhesive white plastic film or a few layers of white spray paint, a particularly good finish can be achieved with a layer of metallic silver followed by a layer of clear lacquer. The light-scattering property of this finish helps to produce good, even illumination across the board.

The PCB carrying the LEDs can now be fitted (glue or screw) into the base. of a suitably sized container or enclosure. Leads carrying power to the cir-



Figure 4. This warning symbol can be used on the unit. UV protection glasses must be worn; eyes can be damaged by the high intensity UV.

It is especially important not to look directly into the UV beam!

cuit are fed from the back of the PCB through a hole in the casing or via a suitable connector to a 12 V mains adapter. The unit is now complete and only requires the glass platen to be fitted or glued to the container. Finally don't be tempted to cut corners with the PCB material, in the long run it always pays to use the best quality material you can afford.

(650629-1)

Links

www.kingbright.com www.rs-components.co.uk www.reichelt.de

 



Figure 3. The circuit uses 24 LEDs. A free PCB layout can be downloaded from www.elektor-electronics.co.uk.

Materials and suggested sources:

12 pcs. 120-Ω resistor 1 pc. diode 1N4001 24 pcs. UV-LED, Kingbright L-7113UVC (RS Components Stock No 507-4034). I pc. connection cable for mains adapter

I pc. components storage cabinet with drawers, approx. size 140 x 220 x120 mm (W x L x H)

 1 pc. glass platen, cut to size, or glass cover of frameless picture holder. White or metallic silver self-adhesive foil (or clear lacquer, see text)











The world beating PCB design software



Easy-PC version 9 just gets better


Winning accolades the world over, Easy-PC for Windows V9 is another major milestone in the evolution of this extremely popular software tool. Try a demonstration copy of Easy-PC and prepare to be amazed at the power, versatility and remarkable value for money.

> Fully integrated Schematics & PCB layout in a single application complete with forward and back annotation. Design and rules checks at all stages ensure integrity at. all times. Professional manufacturing outputs allow you

Version 9 fetaures

- 3D Board View
- New Win XP User Interface
- Reverse Engineer SCM from PCB
- Track Fattening
- Interactive Schematic Routing
- New Sliding Toolbars
- Component Clearance Checks
- Alphanumeric Pin Names

Plus many more exciting features.....

 

Stop press... Stop press... Stop press...

Easy-PC imports Eagle files as well as Tsien Boardmaker 2 files


call for a brochure, prices & CD on +44 (0)1684 773662 or e-mail sales@numberone.com you can also download a demo from





www.numberone.com

 Number One Systems - Oak Lane - Bredon - Tewkesbury - Glos - United Kingdom - GL20 7LR UK



Are you bothered by stray cats and dogs prowling and digging in your garden? Or does your own pet require strong persuasion to stay within a restricted area? This electric fence generator may well be the answer to your problems. A simple generator built around a 555 timer and an old ignition coil are sufficient to build a suitable circuit at a small outlay.

ric Fence Energizer

Those of you who have been with us since the mid-1970s may recall the 'disposable' circuits we used to print on the address label used to get the mag to subscribers. One of the more illustrious designs from that dim past was an electrified wire circuit. Now, more than 35 years on, we present its successor — an old idea but using a fresh approach.

Of course, electric fence units can be purchased commercially and these will typically include a water-resistant enclosure. However, honouring 'home construction is more fun' we thought it would be nice to build such a unit ourselves.

A small circuit

As shown by the schematic in Figure 1, the circuit proposed here does not require much in the way of components. The one part that may strike you as less usual is the ignition coil. If you find a new coil rather expensive, visit the local car breakers for one salvaged from a vehicle and you'll notice the price difference. The remainder of the components are fairly standard. The circuit diagram requires very little

comment. The circuit is built around

the timer IC type 555 (IC1), which is configured here as an oscillator with adjustable pulse/pause ratio.

Since in this case we wish to combine a very short 'on' time with a long 'off' time, two diodes, D2 and D3, are included in the frequency determining network. Using slide switch S1 you can select between three pulse ratios, this is effectively achieved by connecting to different taps in potential divider R1-R5.

The output of the 555 drives a power MOSFET (T1), which in turn connects the ignition coil primary to ground during the pulse 'on' time. This causes a strong voltage surge induced into the secondary, which is connected to the fence wire.

Components D6, C7 and C8 ensure that the timer IC can operate 'on its own' for a short time. This has to do with the fact that an (almost) drained battery may result in the IC being reset, which in turn upsets the pause between the discharge pulses. These would then follow at a too fast rate. To prevent an unwieldy value for C7, we used a CMOS TLC555 instead of the plain vanilla, bipolar NE555.

Finally, a voltage indicator has been added with D1, R7 and D5.

Quick specs

- Discharge energy selectable between 250 mJ, 400 mJ and 450 mJ.
- Low current consumption: 25 mA,
 70 mA or 150 mA depending on discharge energy selection.
- Long lasting: 50, 20 or 8 days depending on discharge energy (using a 45 Ah battery and 2/3 discharge).
- 1.5 seconds between pulses (easily adaptable with R5).
- Pulse duration selectable between 16.5 ms, 24 ms and 31 ms.
- Current consumption of control board: max. 1.6 mA.

I Further reading
I www.foothill.net/~ringram/
I energzer.htm

Building it

Figure 2 shows the copper track layout and component mounting plan of the PCB designed fore this little circuit. Construction will be mostly plain sailing, although we should mention that


 


Figure 1. Here a 555 is configured as an astable multivibrator.

 

 


Figure 2. The PCB has remained nicely compact. The coil is much larger!

 


Figure 3. For clarity's sake we have pictured the construction of a vehicle ignition coil. The primary and the secondary share a common ground terminal.

the wire link next to D2 must not be forgotten.

A few remarks should also be given about some of the other components: For the frequency determining capacitor C4 we used a Siemens MKT type because of its low leakage and longer life expectancy compared with an electrolytic cap. The value of R7 may be changed depending on how brightly you want to see the LED light.

If C5 turns out to 'play hard to get' (locally) then consider using an alternative dimensioning. R1 then becomes 8k2; R2 and R3 4k7 and C5 470 nF / 630 VDC.

A possible alternative to the MOSFET is, for example, the 20N60. Incidentally, the MOSFET is not mounted directly onto the PCB, but at a few mm above the PCB surface using a bolt and two nuts. This mounting method helps the device stay reasonably cool.

If the time between pulses is too long, R5 may be replaced by a wire link.

The ignition coil (Figure 3) should preferably be one from an electronic ignition system for 12-V cars. The type we happened to use had a primary resistance of about 0.7 Ω and a selfinductance of 5 mH. To protect the coil against faults in the circuit we strongly recommend using an in-line fuse. After all, if the 555 fails or goes haywire from some reason or other, the ignition coil primary forms a virtual short-circuit on the battery and a very high current will start to flow, eventually causing the coil to be destroyed or, worse, causing a fire. To increase the reliability of the circuit, it is best to solder the IC directly onto the circuit board, yes that's without a socket. IC socket pins are subject to oxidation in the typical environment the circuit will be used in (outside, in a garden or meadow). For the same reasons of reliability, we're using two paralleled switch contacts instead of just one, reducing the risks of a bad contact disturbing your night rest. If it is desired to operate the switch with the circuit in an enclosure, you may find it useful to mount it at the solder side just look at the height of C5 and the Fast-on (spade) connectors.

(050248-11

COMPONENTS LIST

Resistors

 $R1 = 15k\Omega$

 $R2,R3 = 6k\Omega8$

 $R4 = 1M\Omega$

 $R5 = 390k\Omega$

 $R6 = 470\Omega$

 $R7 = 560\Omega$

Capacitors

C1,C2 = 100µF 63V radial

C3 = 10nF

C4 = 1µF5 MKT, lead pitch 5mm or 7.5mm

C5 = 220nF 630V MKT, lead pitch 22.5

or 27.5mm, size 11x30 mm C6,C8 = 100nF

 $C7 = 47\mu F 25V radial$

Semiconductors

D1 = zener diode 10V 0.5W

D2;D3 = 1N4148

D4 = 1N4007

D5 = LED, low-current

D6 = 1N4002

T1 = IRFP460PBF (500 V/20 A)

TO247AC), e.g., Digi-Key IRFP460PBF-ND

IC1 = TLC555CP (do not use NE555!)

Miscellaneous

K1-K4 = Fast-on (spade) connector,vertical, 2-way PCB mount

S1 = slide switch, PCB mount, 3 x changeover (2 poles, 3 positons), e.g., Conrad Electronics 708097-62

In-line fuse 4A T (slow) with holder

12-V ignition cail (w. length of spark plug cable)

1 wire link (next to D2)

PCB, ref. 050248-1 from The PCBShop

DON'T LOSE YOUR TEMPER

Before phoning us - if you are looking for a hard-to-find part. We have over 20,000 items in stock - including obsolete and up-to-date parts.

WHY NOT VISIT OUR WEBSITE www.cricklewoodelectronics.com

2N 2SA 2SB 2SC 2SD 2P 2SJ 2SK 3N 3SK 4N 6N 17 40 AD ADC AN AM AY BA BC BD BDT BDV BDW BDX BF BFR BFS BFT BFX BFY BLY BLX BS BR BRX BRY BS BSS BSV BSW BSX BT BTA BTB BRW BU BUK BUT BUV BUW BUX BUY BUZ CA CD CX CXA DAC DG DM DS DTA DTC GL GM HA HCF HD HEF ICL ICM IRF J KA KIAL LALB LC LD LF LM M M5M MA MAB MAX MB MC MDAJ MJE MJF MM MN MPS MPSA MPSH MPSU MRF NJM NE OM OP PA PAL PIC PN RC S SAA SAB SAD SAJ SAS SDA SG SI SL SN SO STA STK STR STRD STRM STRS SVI T TA TAA TAG TBA TC TCA TDA TDB TEA TIC TIP TIPL TEA TL TLC TMP TMS TPU U UA UAA UC UDN ULN UM UPA UPC UPD VN X XR Z ZN ZTX + many others

> We accept Mail, telephone & email orders. Callers welcome. Opening hours Mon-Sat 9:30 - 6:00











Cricklewood Electronics Ltd


40-42 Cricklewood Broadway London NW2 3ET Tel: 020 8452 0161 Fax: 020 8208 1441 sales@cricklewoodelectronics.com



CD-ROM Robotics

A large collection of datasheets, software tools, tips, tricks and Internet links to assorted robot constructions and general technical information. All aspects of modern robotics are covered, from sensors to motors, mechanical parts to microcontrollers, not forgetting matching programming tools and libraries for signal processing. Robots built from LEGO®

bricks also get a fair amount

 

ISBN 90-5381-179-6 £12.05 / US\$ 21.25

Order now using the Order Form in the Readers Services section in this issue.

Elektor Electronics (Publishing) Regus Brentford 1000 Great West Fload Brentford TW8 9HH United Kingdom Tel. +44 (0) 208 261 4509

See also www.elektor-electronics.co.uk

Electronic Web: www.lichfieldelectronics.co.uk el: (U1543) 256684

The Corn Exchange **Conduit Street** Lichfield, Staffs. W513 6JU



Telephone board £28,99 Make your own telephone and learn how they work.

Chasing Arrow £9.99 A 21 LED kit to build an animated arrow, 9-12V-DC



Electronic Sandglass £14.99 A 22 LED digital sandglass With adjustable speed.

Fire Siren

£4.99

Using transistors and passive parts build a fire siren with button.



Electronic Dice 7 LED kit to make an electronic dice: Uses 4017 and transistors

2 Way V.U. Meter A 20 LED audio meter. MANA MAGO No batteries required habble for terms



2 Digit Digital Counter £9.99 How does a metal detector work? Find out with this great kit.

Electronic Shock Machine £5.99 This great kit turns low voltage mas E DC in to high voltage AC.



Easy FM Radio £14.99 A simple IC based FM Radio Reciever, 88-108Mhz

Video Amplifier £12.99 to 4 channel video amplifier with adjustable gain 1-4 db.





4 Way Traffic Light £6.99 Build this 12 LED traffic light, A kit everyone should do once.

Electronic Code Switch £14.99 The circuit is a 10 key 4 digit code lock with relay for solenoid.



Magnetic Alarm £16.99 Make a magnetic switch burglar alarm using this simple kit.

Telephone Interceptor £8.99 A small amplifier circuit which lets you hear phone conversations



Clap on/off switch £9.99 Make a sound activated on/off switch with relay and mic.

15W Stereo Amp £24.99 Build your own high quality stereo amplifier.



0-30V 3A PSU £15.99 Build your own variable voltage 3 amp Power supply.

Raining Alarm £6.99 A simple circuit with remote rain sensor and alarm



Walky Talky kit £34.99 1 Pair of 27Mhz Walky Talkies in kit form.

Telephone In-Use £2.99. A nice simple kit with two. LED's. No batteries req.



of attention.

Aovue 850 Rework Station £54.99 This great hot air rework station is ideal for hobbyists working with ever smaller chips, The 850 includes 3 nozzles and has a temperature range of 100-500C and adjustable air flow. Ideal for SOIC-QFP

Aoyue 936 Soldering Iron £24.99 A high quality temperature controlled 35W soldering iron with long lastingceramic heater element, metal iron stand with solder holder/feeder. Spare element included free! Temp range: 200-480C



Aoyue 909 iron, g	un an	d PSU Also Av	ailable £99	99
Other available	kits:	Babani Bo	oks & Mo	ore
V.U. Meter 6 LED	£3.99	Electronic Projects for if	te (jipica:	£4.95
3 Level Water Level Indicar	or£3.99	45 Simple Terminal Blo	-10	-£4.93
6 LED Triangle Flasher.		Test Equipment Constru		£3.99
Atomic Chasing Light 7 LE		How to Design and Mak		
3 LED Chasing Light	£4,49	Getting the Most From 1		£3.99
LED Flasher 10 LED Circle		An Introduction to Amar Power Supply Projects	tera: kresno	E4.99 124.99
AC Flasher ICH 220V 700		The Art of Soldering		£3,99
0-30V IA Variable PSU	07.00	A Beginners Guide to T	II Digital les	€4.95
		A Beginners Guide to Cl	MOS Digital les	£4.93
Visitor Chime kit	£7.99	Practical Electronic Mus	Made .	£4,95
Cockroach Banisher Circuit	- "	Electronic Projects for V		£4:93
10 LED Running light straig		Note de Voits US Electro	mies Magazine	14.99
Two way chasing light	£8.99	Post and	Packing	
12V Xenon Tube Flasher	£8,99	TA COLUMN	THEKING	
Touch Switch (On Off)	£8.99	Order Value	P&P Cost	
Rotation chasing light	£10,99	£4.99-£12.99	£1.50	
Wireless V.U. Meter 15	£12:99	£13.00-£22.99	£2.50	
Robot voice changer	£12.99.			
8W Stereo Amplifier kit	£13.99	£23.00-£49.99	£6.00	
Stereo Simulator	£14.99	£50.00-£150.00	£12.00	
23ft IR Remote control rela-	v £18.99	UK Only, phone f	or P&P to Irel	and.
Dancing Light 3CH-2400W	€19.99	Pay by cheque, car	rd er postal or	der!
			1	

PIR Infrared sensor switch £27.99 Visit website for weight based P&P 124 new kits, 21 new enclosures and a new online shop since last month. Or visit our shop in Lichfield

Reforming old electrolytic capacitors


Luc Lemmens

Electrolytic capacitors that have spent a long time in storage are being sold as 'new old stock' (NOS) by the surplus trade, or come from old equipment, are not or no longer of a suitable quality that allows them to be used just like that.

After manufacturing, there is a very thin layer of oxide on the positive electrode that acts as a dielectric between the plates. In normal use, when there is a voltage across the capacitor, this layer is maintained by the leakage current in this component. But if the capacitor is not used for a long time, this thin layer slowly disappears, so that the capacitor starts to look more like a short circuit. If a voltage is then suddenly applied, the current can rise so high that the capacitor overheats and the dielectric evaporates. This can result in the explosion of the capacitor.

 At low values of capacitance it is not worth the trouble to take the risk because these components are not that expensive. Unless you want to restore, for example, an old radio, and want to keep it as original as possible. Also, axial capacitors are becoming increasingly rare





and are almost not available new. Large power supply reservoir capacitors have always been expensive and certainly in this category it is definitely worth the effort to try to breathe new life into them. And of course, it is this category that generates the most speciacular 'explosions' when something goes wrong...

This can be avoided by waking op the capacitor slowly (that is: reform the oxide layer slowly). Use a large value resistor (1 MΩ, for example) and connect it in series with the capacitor to a lab power supply. Start with a power supply voltage of about a quarter of the rated capacitor voltage and measure the voltage across the capacitor. It can take some time, even a number of hours before this voltage is equal to the power supply voltage (i.e., the capacitor is charged). It takes some patience to allow the oxide layer to be reformed. After that you can increase the voltage in a few steps to the rated value (each time wait until both voltages are equal again before proceeding). There is a reasonably good chance that this procedure will be successful of you follow this method with care and patience!


(0.600324-1)

Current surge limiter for toroidal transformers

K. Viernickel

Lots of circuit variations exist on this theme. We would like to add one more, however, that's not easily beaten for simplicity and reliability.

It seems that toroidal mains transformers can only be switched on by a helty initial current. The current surge is especially high when initially the residual magnetism stored in the closed core has to be built up because of the instantaneous phase angle. The current surge occurs when the sinusoidal current in the primary winding and the remaining magnetism in the iron core cause the latter to go into saturation. An example

 

may help here. The residual magnetism has a positive value. When power is applied to the primary, a positive half cycle that

happens to arrive raises the positive magnetism value to a value sufficient to cause massive saturation of the iron core. In this condition, the only current limiter is the resistance of the primary winding copper wire, and that for sure is a very low value in the case of heavy toroidal transformers. Only after a few full cycles of the mains voltage will the magnetisation get synchronised with the alternating current, keeping the iron core free from saturation up to the nominal load limit. During the critical period, some kind of current limiting device should be used to prevent a big 'thump' at poweron. Here, a thermistor is used for that purpose.

In parallel with the NTC we find a normally-open relay contact. The contact will bypass the NTC after a short time, supplying the transformer with the full mains voltage and of course allowing the NTC to cool down for the next power-on sequence.

The relay will pull in as soon as the transformer is ready to accept the full mains voltage. The NTC is protected by a resettable thermal switch and a 10-A slow-blow fuse.

The circuit has proved to be utterly reliable in practice. Besides a low component count, it is also marked by low current consump-

tion. Of course, it will cause a short power-on delay.

The value of resistor R2 and zener diode D2 may have to be adapted to suit the coil voltage of RE1.

(150291-3)

Warning.

This circuit is connected directly the mains voltage. All relevant precautions apply in respect of electrical safety.


PCB pin insertion tool

Luc Lemmens (Elektor labs)

The humble PCB pin is used not only to connect wires to PCB tracks, but also for test and measurements points on circuit boards. Despite their mechanical simplicity, PCB pins are surprisingly difficult to mount and solder. Frequently encountered problems (admit it!) are burnt fingers while soldering the pin, and pins dropping from the board when the board is turned, or, worse, when they're being soldered. Try to keep it in place with your finger - too hot to touch — look for pliers — pin dislocated — and so on.

It's a good idea to drill the holes for the PCB pins a fraction smaller than the pin diameter — that way, the pin remains in place

 when you're ready to solder it. However, that also requires a bit more force to push the pin into position and a tool is then useful to prevent injuring your fingers. Pliers may be less suitable, especially if considerable force is required on the pin. To the best of knowledge, commercial tool exists for the No purpose. problem, let's make a PCB pin insertion tool ourselves.



A discarded round file or screwdriver is great. Cut or grind the shaft as straight as you can and drill a hole in the end so the ridge on the PCB pin is secure against the surface of the tool. The PCB pin is inserted into the tool and held in place with a nail or fingertip. The tool handle provides a secure grip and allows considerable insertion force to be applied. If an old file is used, it is recommended to cover the remaining section of the steel surface with heat shrink tubing. This will prevent injury to your hand.


(1962-1)

Accurate timebase

Thomas Pototschnig

This circuit demonstrates how easily a timebase can be designed using a minimum number of components. This circuit consists of no more than an IC and an oscillator to which a few connections and decoupling parts are added. Use is made of a single IC from the 4000 series, the type 4521 oscillator / counter with 24 steps. Here we only use the counter section of the IC.

 The IC is supplied with a clock signal by an oscillator module. The clock signal is divided down by the 4521 to obtain certain values. Discrete frequencies obtained in this way are available on the counter output pins of the 4521. For example, pin 10 (Q18) supplies the clock frequency (applied to pin 6) by a factor of 218 or 262, 144. Like-



wise, pin 1 (Q24) divides the input signal by 2^{24} or 16,777,216. By using a clock frequency of

2.097152 MHz the following timebase frequencies are obtained at the output of the 4521:

- Pin 10 (Q18); 8 Hz;
- Pin 11 (Q19): 4 Hz;
- Pin 12 (Q20): 2 Hz;
- Pin 13 (Q21): 1 Hz;
- Pin 14 (Q22): 0.5 Hz;
- Pin 15 (Q23): 0.25 Hz;
 Pin 1 (Q24): 0.125 Hz.

In case other frequencies are required, a different crystal oscillator module should be selected. For flexibility, an IC socket is recommended so modules can be exchanged quickly. Alternatively, modules may be connected to the 4521 by means of a selector switch.

To keep the circuit as versatile as possible, the outputs of the 4521 counter may be made available for connection to the outside world by way of a pinheader. For the sake of convenience, the pinheader also supplies ÷5 V and GND.

(05004515)



Quasar Electronics Limited

PO Box 6935, Bishops Stortford CM23 4WP, United Kingdom

Tel: 0870 246 1826 Fax: 0870 460 1045

E-mail: sales@quasarelectronics.com Web: www.QuasarElectronics.com

Postage & Packing Options (Up to 2Kg gross weight): UK Standard 3-7 Day Delivery - £3.95; UK Mainland Next Day Delivery - £8.95; Europe (EU) - £6 95 Rest of World - £9 95 (up to 0.5kg) !Order online for reduced price UK Postage!

We accept all major credit/debit cards. Make cheques/PO's payable to Quasar Electronics. Prices include 17.5% VAT.

Call now for our FREE CATALOGUE with details of over 300 kits. projects, modules and publications. Discounts for bulk quantities.



VISA





electronics



CREDIT CARD SALES

7177168



Get Plugged Ini

Motor Drivers/Controllers

Here are just a few of our controller and driver modules for AC, DC, unipolar/bipolar stepper motors and servo motors. See website for full details:

NEW! Bidirectional DC Motor Controller



Controls the speed of most common DC. motors (rated up to 32Vdc/5A) in both the forward and reverse direction. The range

of control is from fully OFF to fully ON in both directions. The direction and speed are controlled using a single potentiometer. Screw terminal block for connections. Kit Order Code: 3166KT - £15.95

Assembled Order Code: AS3166 - £25.95

DC Motor Speed Controller (5A/100V)



Control the speed of almost any common DC motor rated up to 100V/5A. Pulse width modulation output for maximum motor torque

at all speeds. Supply: 5-15Vdc. Box supplied. Dimensions (mm): 60Wx100Lx60H. Kit Order Code: 3067KT - £12.95 Assembled Order Code: AS3067 - £20.95

NEW! PC / Standalone Unipolar

Stepper Motor Driver Drives any 5, 6 or 8-lead

unipolar stepper motor rated up to 6 Amps max. Provides speed and direc-




tion control. Operates in stand-alone or PCcontrolled mode. Up to six 3179 driver boards can be connected to a single parallel port. Supply: 9Vdc. PCB: 80x50mm. Kit Order Code: 3179KT - £11.95

Assembled Order Code: AS3179 - £19.95

NEW! Bi-Polar Stepper Motor Driver

 Drive any bi-polar stepper motor using externally supplied 5V levels for stepping and direction control. These usually come from software running on a computer.



Supply: 8-30Vdc. PCB: 75x85mm. Kit Order Code: 3158KT - £14,95 Assembled Order Code: AS3158 - £29.95

Most items are available in kit form (KT suffix) or assembled and ready for use (AS prefix).

Controllers & Loggers

Here are just a few of the controller and data acquisition and control units we have. See website for full details. Suitable PSU. for all units: Order Code PSU345 £9.95

Rolling Code 4-Channel UHF Remote

State-of-the-Art. High security. 4 channels. Momentary or latching relay output. Range up to 40m. Up to 15 Tx's can be learnt by one Rx (kit includes one Tx but more avail-

able separately). 4 indicator LED 's, Rx: PCB 77x85mm, 12Vdc/6mA (standby). Two and Ten channel versions also available. Kit Order Code: 3180KT - £39,95 Assembled Order Code: AS3180 - £47.95

Computer Temperature Data Logger



4-channel temperature logger for serial port. °C or *F. Continuously logs up to 4 separate sensors located 200m+ from board. Wide range of free software appli-

cations for storing/using data. PCB just 38x38mm. Powered by PC. Includes one DS1820 sensor and four header cables. Kit Order Code: 3145KT - £17.95 Assembled Order Code: AS3145 - £23.95 Additional DS1820 Sensors - £3.95 each


NEW! DTMF Telephone Relay Switcher

Call your phone number using a DTMF phone from anywhere in the world and remotely turn on/off any of the 4 relays as desired.



User settable Security Password, Anti-Tamper, Rings to Answer, Auto Hang-up and Lockout, Includes plastic case. Not BT approved, 130x110x30mm, Power, 12Vdc. Kit Order Code: 3140KT - £44.95 Assembled Order Code: AS3140 - £64.95

Serial Isolated I/O Module

 

Computer controlled 8channel relay board. 5A mains rated relay outputs. 4 isolated digital inputs. Useful in a variety of control and

sensing applications. Controlled via serial port for programming (using our new Windows interface, terminal emulator or batch files). Includes plastic case 130x100x30mm. Power Supply: 12Vdc/500mA.

Kit Order Code: 3108KT - £54.95 Assembled Order Code: AS3108 - £64.95 Infrared RC Relay Board Individually control 12 onboard relays with included infrared remote control unit.

range. 112x122mm. Supply: 12Vdc/0.5A Kit Order Code: 3142KT - £42,95

Toggle or momentary, 15m+ Assembled Order Code: AS3142 - £52.95

PIC & ATMEL Programmers

We have a wide range of low cost PIC and ATMEL Programmers. Complete range and documentation available from our web site.

Programmer Accessories:

40-pin Wide ZIF socket (ZIF40W) £15.00 18Vdc Power supply (PSU010) £19.95 Leads: Parallel (LDC136) £4.95 / Serial (LDC441) £4.95 / USB (LDC644) £2.95

NEW! USB 'All-Flash' PIC Programmer

USB PIC programmer for all 'Flash' devices. No external power supply making it truly portable. Supplied with box and Windows Software, ZIF Socket and USB Plug A-B lead not incl. Assembled Order Code: AS3128 - £39.95

"PICALL" PIC Programmer



"PICALL" will program virtually all 8 to 40 pin serialmode* AND parallel-mode (PIC16C5x family) programmed PIC micro control-

lers. Free fully functional software. Blank chip auto detect for super fast bulk programming. Parallel port connection. Supply: 16-18Vdc. Assembled Order Code: AS3117 - £24.95

ATMEL 89xxxx Programmer

Uses serial port and any standard terminal comms program. 4 LED's display the status. ZIF sockets not included. Supply: 16-18Vdc. Kit Order Code: 3123KT - £24.95

NEW! USB & Serial Port PIC Programmer



USB/Serial connection. Header cable for ICSP. Free Windows software. Wide range of supported PICs - see website for complete listing. ZIF Socket/USB

Plug A-B lead not incl. Supply: 16-18Vdc. Kit Order Code: 3149EKT - £37.95 Assembled Order Code: AS3149E - £52.95



www.quasarelectronics.com

Secure Online Ordering Facilities • Full Product Listing, Descriptions & Photos • Kit Documentation & Software Downloads


1-to-3 Phase Converter (1994/1995)

Jan Buiting

Our resident designer Karel Walraven has been known for almost three decades to have a serious infatuation with electric motors and it was no wonder he was assigned, back in 1994, to a project received from one B. Yahya for a 1-to-3 phase converter. Unlike his colleagues (and myself) safe in the world of milli-amps and everything sub 20 volts or so, Karel likes kVAs, big a.c. motors and 'electrical engineering' ÎĐ general (although he will also happily whip up a piece of 8051 assembly code for you). From the very beginning, the phase converter project raised high hopes as back in 1994 such units were rarer than hens' teeth and only found in the professional domains, i.e., well out of the reach of the DIY enthusiast. So what's the point in converting your 230-V 1-phase mains voltage to three phases? The answer is: none, unless you have a really fine 3-phase motor lying about you'd like to apply speed control on. Three phase motors are relatively powerful per watt of energy absorbed and therefore the items of choice in lots of professional equipment. The principle underlying the abil-


ity to control a 3-phase motor for speed is illustrated by the block schematic. It is based on the fact that the speed of a 3-phase motor depends on the frequency of the applied voltage rather than the voltage level. In our design, a hefty control circuit through some power MOSFETs applies almost sinusoidal voltages across the motor windings connected in 'star' arrangement. The sinusoidal voltage was created using pulse-width modulation.

 Without delving into the operation of the design, two things must have struck our readers as quite novel at the time: firstly, the use of an 80C535 microcontroller (not easily associated with 750-watt a.c. motors) and sec-





 ondly, the sudden appearance of a GAL of the 20-legged variety. The GAL, in the end, caused the most concern as it was a relaof course, we supplied it readyprogrammed, but lots of readers started asking for the jedec file to



burn their own 16V8. I remember some readers accusing us of black-box engineering on account of the GAL being a key component they could not easily produce at home. Some even claimed it 'did nothing except filling Elektor's pockets', but when shown the equivalent in logic gates the critics soon shut up.


The converter was so complex, and there was so much to say about it, the article had to be split in two parts. The unit graced the magazine cover in December 1994 and its construction was described in January 1995. A good deal of attention was given to electrical safety aspects of the project.

When I pulled the unit from cabinet #12 in our laboratory it struck me that a motor or two would be nice to photograph with the converter. Karel opened a drawer and handed me three mint looking motors which, he said, had been in use by the Dutch State Mines (DSM) in the late 1960s (I thought they couldn't have been older than a few years). I was in for another surprise: the motors were the ones originally pictured on the December 1994 magazine cover.


Having been told about this months' subject for Retronics my colleague Guy Raedersdorf in the French editorial department suddenly remembered having received a letter from an irate reader from a North-African country. Not mincing his French, the correspondent condemned Elektor & staff for All Eternity on account of having printed the name of an author he was at loggerheads with regarding some religious interpretation. The wretched author, it turned out, was Harun Yahya — not even a distant relative of the designer of the Elektor project. Twelve years on I can safely say that the converter was a very popular project and we are no longer-waiting for whatever curse of to fall upon us: Or maybe it was that virus in last week's email?

(055034-1)

 Retronics is a monthly column covering vintage electronics including legendary Elektor designs. Contributions, suggestions and requests are welcomed; please send an email to editor@elektor-electronics.co.uk, subject: Retronics EE.



E-blocks: whatever you want to make

 

Take one of our upstream programmer boards + add a number of downstream peripheral boards + combine with our range of software utilities and = develop a wide range of highly functional electronic systems

E-blocks are small circuit boards each of which contains a block of electronics that you would typically find in an electronic system. The E-blocks range consists of around 150 separate items which can be combined to make an enormous variety of electronic systems offering a wide range of learning opportunities. Learn more about E-blocks?





Hexadoku

Puzzle with an electronic touch

Here is our Hexadoku puzzle for the month of May. Switch off the PC and sharpen your pencil for another brain teaser that'll turn out to be a real challenge to solve.

Send us your solution and win one of the fantastic prizes!

The instructions for the puzzle are straightforward. In the diagram composed of 16x16 boxes, enter numbers in such a way that **all** hexadecimal numbers 0 through F (that's 0-9 and A-F) occur once in every row, once in every column, and in every one of the 4x4 boxes (marked by the thicker black lines). A number of clues are given in the puz-

zle and these determine the start situation.

Your solution may win a prize and requires only the numbers in the grey boxes to be sent to us (see below). The puzzle is also available as a **free download** from our website (Magazine → 2006 → May).

(0:25042-1)

Entering the competition

Please send the numbers in the grey boxes by email, fax or post to

Elektor Electronics Hexadoku
Regus Brentford
1000 Great West Road
Brentford TW8 9HH
United Kingdom.
Fax (+44) (0)208 2614447
Email:
editor@elektor-electronics.co.uk
Subject: hexadoku 05-2006.

The closing date is 24 May 2006.

Competition not open to employees of Segment b.v., its business partners and/or associated publishing houses.

Prize winners

The solution of the February 2006 Hexadoku is: 3B479. The **E-blocks Starter Kit Professional** goes to: Steve Barber (Stotfold, UK).

An Elektor SHOP Voucher worth £35.00 goes to:

Jari Koskinen (Koulova, FIN), R. Wilton (Helston, UK) and Jim Gray (Jefferson, USA).

0			3	5			Α	8	E	2	4		D	C	
D	4			i											0
В	5	1	6			2		F		9		8			
					7		8	6	0		D	2	9		В
E	0			Α	9	3	7		6						
	1		С		F			0			5	E			
4	F			C	2		1	Α					6	D	
	6		2			0	D	7				Α	В	5	4
		6		1		8	0	С	9				ē		F
	С		7	6	Α		Е				8	3	2		D
8	В	4	9	7				E	F				0	6	
3				9	4		F	2				7	1		
		Е		D		Α					1	6		0	C
	9		4				C		2		0		8	3	
		В				# ".		D		Α	Е			F	1
Α			1	F				3	7	6		В	5	E	

Solve Hexadoku and win!

Correct solutions qualify for an

E-blocks Starter Kit Professional



worth £248.55 and three

Elektor Electronics
Shop Vouchers
worth £35 each.

We believe these prizes should encourage all our readers to participate!

ELEKTORSHOWGASE

To book your showcase space contact Huson International Media Tel. 0044 (0) 1932 564999 Fax 0044 (0) 1932 564998

ATC SEMITEC LTD

www.atcsemitec.co.uk

Thermal and current-sensitive components for temperature control and circuit protection;

- NTC Thermistors
- Current Diodes
- Thermostats
- Re-settable Fuses
- Thermal Fuses
- · Temperature Sensors

Call today for free samples and pricing

Tel: 0870 901 0777 Fax: 0870 901 0888

BETA LAYOUT

www.pcb-pool.com

Beta layout Ltd Awardwinning site in both English and German offers prototype



PCBs at a fraction of the cost of the usual manufacturer's prices.

DESIGN GATEWAY

DESIGN == www.design-gateway.com

PalmLogic II US\$ 399.00.

- Compact Logic Analyzer (L116mm x W73.3mm x T3mm)
- High sampling rate (400 MHz/ 8ch, 200 MHz/16ch, 100 MHz/32ch)
- . USB 2.0 high speed mode
- · 8MB memory storage
- · Bus Analyzer function
- · Multiple waveform windows
- · Waveform save/restore

DESIGN GATEWAY

www.design-gateway.com True PCI Starter Kit US\$135.00

- PCI Development Kit
- Based on 200,000 gates FPGA
- Extension connectors for 72 pin I/O TRUE PO
- Configuration support for JTAG and slave serial
- · Free PCI Core for Target Mode

DESIGN GATEWAY

www.design-gateway.com Ethernet IO US\$115.00



DESIGN ==

- 8 bits embedded network microcontroller
- · 6 channels available for 10 bits ADC
- Ethernet lo . Ethernet 10 BASE T 10 Mb
- UART port RS232/RS485, Max Speed at115200bps
- 35 bits general purpose I/O
- . 500 bytes user area flash memory


DESIGN == **DESIGN GATEWAY** www.design-gateway.com

VariClock ... US\$163.00

- · Adjustable clock signal synthesizer
- · 3 rotary switches for frequency setting
- · Standard DIP pin arrangement
- Support both 3V/5V by on-board regulator


VC250M14P Frequency range : 25-400 MHz

 Frequency setting: 1MHz step. VC100M14P Frequency range : 25-100 MHz







 

AVIT RESEARCH

www.avitresearch.co.uk

USB has never been so simple...

with our USB to Microcontroller Interface cable. Appears just like a serial port to both PC and Microcontroller, for really easy USB connection to your projects, or replacement of existing RS232

interfaces.

See our webpage for more details. Only £29.99 inc vat.

COMPUCUT

http://www.compucutters.com

Computer Numerical Control from your home PC. Great for tricky jobs, and accurate repetitive work. We supply: - Software - Interface - Manual

- Support

Price £250 plus postage.

COMPULOGIC LTD

www.compulogic.co.uk

Internet Remote Control Starter Kit £139.99 Create a simple web based remote control interface for many applications

- · Miniature Web Server Module
- · Analogue/Digital Module
- PSU
- Manuals, software, example HTML code

CONFORD ELECTRONICS

http://www.confordelec.co.uk

Lightweight portable battery/mains audio units offering the highest technical performance. Microphone, Phantom Power and Headphone Amplifiers, Balanced/unbalanced signal lines with extensive RFI protection.

DANBURY ELECTRONICS

http://www.DanburyElectronics.co.uk

Transformer manufacturers since 1983. Visit our new site! Also link directly to Mike Holme's Valve/-Tube DIY amplifier site, featuring our standard Audio Transformers (Mains, Output, Chokes, PP, SE, etc).

EAGLEPICS

http://www.eaglepics.co.uk

Embedded Internet Solutions

- · Stand alone TCP/IP module
- Platform independent
- . Simple "AT-like" command set
- GPRS or modern connection
- · E-Mail, FTP, HTTP, UDP
- · Development board available
- · Free development utilities
- · Free UDP-only stack

EASYSYNC

http://www.easysync.co.uk

EasySync Ltd sells a wide range of single and multiport USB to RS232/RS422

and RS485 converters at competitive prices.



ELNEC

www.elnec.com

- · device programmer manufacturer
- · selling through contracted distributors all over the world
- · universal and dedicated device programmers
- · excellent support and after sale support
- · free SW updates
- · reliable HW
- · once a months new SW release
- · three years warranty for most programmers

FUTURE TECHNOLOGY DEVICES

http://www.ftdichip.com

FTDI designs and sells USB-UART and USB-FIFO interface i.c.'s.

Complete with PC drivers,

these devices simplify the task of designing or upgrading peripherals to USB

FUTURLEC

http://www.futurlec.com

Save up to 60% on

- · Electronic Components
- · Microcontrollers, PIC, Atmel
- · Development Boards, Programmers

Huge range of products available on-line for immediate delivery, at very competitive prices.

HEROS TECHNOLOGY LTD

www.herostechnology.co.uk

Introducing Modular Concept for microcontrollers.

Suitable for Developers, Pre-production, Educational and Hobby applications.

- WinPlC2006 USB full speed programmer.
- · CPU microcontroller modules.
- · Peripheral modules for all microcontrollers.

IPEVA LIMITED

http://www.ipeva.com

IPEVA sell low cost USB FPGA development boards. IPEVA provide Design Consultancy for Embedded Systems.

OpenCores-IP, FPGA, ASIC, HDL translation and

migration. Tel. 0870 080 2340.





apeva

products and services directory

JLB ELECTRONICS

www.jlbelectronics.com

Suppliers of electrical / electronic parts and consumables. Including:

- · Cable ties / bases
- Tools / hardware
- · Bootlace ferrules
- Connectors
- · Solvent sprays & cleaners
- PVC Tape
- · Heat Sink compound

KMK TECHNOLOGIES Ltd.

http://www.kmk.com.hk

Low Cost DIY Robotic Kits and Computer Controller Boards.



LONDON ELECTRONICS COLLEGE

http://www.lec.org.uk

Vocational training and education for national qualifications in Electronics Engineering and Information Technology (BTEC First National, Higher National NVQs, GCSEs and Advanced Qualifications). Also Technical Management and Languages.

MQP ELECTRONICS

http://www.mapelectronics.co.uk

Leaders in Device Programming Solutions.

- · Online shop
- . Low Cost Adapters for all Programmers
- Single Site and Gang Programmers
- · Support for virtually any Programmable Device

NEW WAVE CONCEPTS

www.new-wave-concepts.com

Software for hobbyists:

- · Livewire circuit simulation software, only £34.99
- · PCB Wizard circuit design software, only £34.99



Available from all Maplin Electronics stores and www.maplin.co.uk.

OLD COLONY SOUND LAB

www.audioXpress.com

New catalog features:

Premier source for DIY audio for 35 years!

- · Books
- CDs
- Test & Measurement
- Kits

Full range of products and magazines for the DIY audio enthusiast!

PCB WORLD

http://www.pcbworld.org.uk

World-class site: Your magazine project or prototype PCB from the artwork of your choice for less. Call Lee on 07946 846159 for details. Prompt service.

ULTRALEDS

Ultraleds.co.uk

http://www.ultraleds.co.uk

tel: 0871 7110413

Large range of low cost Ultra bright leds and Led related lighting products. Major credit cards taken online with same day depatch.

Email: sales@QuasarElectronics.com ROBOT ELECTRONICS Old Colony e

http://www.robot-electronics.co.uk

QUASAR ELECTRONICS

www.QuasarElectronics.com

Over 300 electronic kits.

projects and ready built

including PIC/ATMEL

units for hobby, education

and industrial applications

Tel: +44 (0) 870 246 1826

Fax: +44 (0) 870 460 1045

Advanced Sensors and Electronics for Robotics

programming solutions. Online ordering facilities:

- . Ultrasonic Range Finders
- · Compass modules
- · Infra-Red Thermal sensors
- Motor Controllers
- Vision Systems
- · Wireless Telemetry Links.
- · Embedded Controllers



SK PANG ELECTRONICS

http://www.skpang.co.uk

- · ELM OBDILIC
- VAG-COM Interface
- OBDII connector and cable.
- Modtronix Micro X board
- · Embedded Ethernet Controlle.
- · PIC Microcontroller, CAN Bus driver Major credit cards taken online.

SYTRONIC TECHNOLOGY LTD

www.m2mtelemetry.com

Supplier of wireless modules and accessories for remote

monitoring M2M applications.

- GSM/GPRS TCP/IP modules
- · Embedded GSM/GPRS modem.
- · Development Kits
- · GPS modules
- GSM/GPS antennas
- Adapter cables

Online ordering facilities. Tel (01394) 210911



USB INSTRUMENTS

http://www.usb-instruments.com

USB Instruments specialises in PC based instrumentation products and software such as Oscilloscopes, Data Loggers, Logic Analaysers

which interface to your PC via USB.



VIRTINS TECHNOLOGY

www.virtins.com

PC and Pocket PC based virtual instrument for electronics enthusiasts. students, professionals and scientists, including sound card real time oscilloscope,



spectrum analyzer, and signal generator. Free to download and try.



SHOWCASE YOUR COMPANY HERE

Elektor Electronics has a feature to help customers promote their business, Showcase - a permanent feature of the magazine where you will be able to showcase your products and services.

- For just £220 + VAT (£20 per issue for eleven issues) Elektor will publish your company name, website adress and a 30-word description
- For £330 + VAT for the year (£30 per issue for eleven issues) we will publish the above plus run a 3cm deep full colour image - e.g. a product shot, a screen shot from your site, a company logo - your choice


Places are limited and spaces will go on a strictly first come, first served basis. So please fax back your order today!

I wish to promote my company, please book my space: Text insertion only for £220 + VAT
 Text and photo for £330 + VAT NAME: ORGANISATION: JOB TITLE: ADDRESS: PLEASE COMPLETE COUPON BELOW AND FAX BACK TO 00-44-(0)1932 564998 COMPANY NAME WEB ADDRESS..... 30-WORD DESCRIPTION

Straight from the heart of electronics each month

This Issue: STAND-ALONE EOBD ANALYSER

the fast link to a microcontroller!

 

Next Issue: SCOPEMETERS COMPARED

10 mobile oscilloscopes compared for performance

Want to know everything each month? Select your own annual subscription and receive a free 1W Luxeon LED Torchlight*



Available options:

- Elektor Electronics annual subscription (standard)
 You receive 11 issues, including the July/August double issue.
- Elektor Electronics annual subscription-PLUS
 You receive 11 issues, including the July/August double issue,
 plus a copy of the Elektor Electronics Volume 2006 CD-ROM
 (normal price £16.25). Your saving: approx. £10.00!

Please fill out the Order Form with this issue. Subscription rates and conditions may be found at the back of this issue.



 Offer available to Subscribers who have not held a subscription to Elektor Electronics during the last 12 months. Offer subject to availability.



Order now using the Order Form in the Readers Services section in this issue.

CD-ROM

Elektor Electronics (Publishing) Regus Brentford 1000 Great West Road Brentford TW8 9HH United Kingdom

Telephone +44 (0) 208 261 4509 +44 (0) 208 261 4447 Fax Email: sales@elektor-electronics.co.uk

More information on www.elektor-electronics.co.uk

BESTSELLERS

Elektor 2005

This CD-ROM contains all editorial articles, with the exception of New Products items, published in Elektor Electronics magazine Volume 2005. Using the supplied Acrobat Reader program, articles are presented in the same lay-



out as originally found in the magazine. The Disk-Mirror utility on this CD-ROM allows your earlier Elektor year volume CD-ROMs (1997-2004) to be added to a large archive on hard disk for fast access and easy reference. A built-in search function allows you to find references in any article from the archive on hard disk, or from individual year volume CD-ROMs you have available.

£16.25 (USS 28.75)

Home Automation

This CD-ROM provides an overview of what manufacturers offer today in the field of Home Networking, both wired and wireless. The CD-ROM contains specifications, standards and protocols of commercially available bus and network systems. For develo-



pers, there are datasheets of specific components and various items with application data. End-users and hobbyists will find ready-made applications that can be used immediately.

£12.95 (US\$ 22.90)

ECD Edition 3


Elektor's Components Database gives you easy access to design data for over 5,000 ICs, more than 35,000 transistors, FETs, thyristors and triacs, just under 25,000 diodes and 1,800 optocouplers. All data-



bank applications are fully interactive. allowing the user to add, edit and complete component data. £14.95 (USS 26.50)

Modern High-end Valve Amplifiers


Valve amplifiers are regarded by many to be the ne plus ultra when it comes to processing audio signals. The combination of classical technology and modern components has resulted in a revival of the valve amplifier. The use of toroidal-core output transformers, developed by the author over the past 15 years, has contributed to this revival. This book explains the whys and wherefores of toroidal output transformers at various technical levels and offers innovative solutions for achieving perfect audio quality.

 

ISBN 0 905705 63 7 264 Pages £25.95 (USS52.00)

Build your own Audio Valve Amplifiers

To many people, the thermionic valve or electron tube is history. However, whether it is nostalgia, interest in the technical parameters, the appeal of a gleaming amplifier chassis with softly glowing valves or perhaps the firm conviction that the sound of a valve cannot be bettered, it is a fact that the valve is making a come-back. This book contains, apart from construction projects for preamplifiers, power amplifiers, and amplifiers for musical instruments, information on the operation of electron tubes, while the first chapter gives a short history of the valve.

 

ISBN 0 905705 39 4 253 Pages £15.55 (US\$31.00)

MICROCONTROLLER

BASICS

BESTSELLING BOOKS

Top-5


Microcontroller Basics



ISBN 0-905705-67-X £18.70 (USS 33.70)

Modern High-end Valve Amplifiers

ISBN 0-905705-63-7 £25.95 (USS 52.00)

 



308 Circuits ISBN 0-905705-66-1 £18.20 (USS 37.00)

More information on www.elektor-electronics.co.uk



Order o www.elektor-e

Order now using the Order Form in the Readers Services section in this issue.

GPS Receiver on USB

(June 2005)

Complete kit (not including IC3) with Lassen iQ-receiver and extra long cable, CD with software and waterproof antenna case.

040264-71



Electrosmog Tester

(June 2005)

Ready-built PCB (excl. enclosure)

£ 50.00 / \$ 94.25

Matching enclosure

050008-71

050008-91

£ 10.25 / \$ 19.30



OBD-2 Analyser

(July/August 2005)

Kit of parts including PCB, programmed controller, components (including IC7; IC3 = PCA82C250, 12 V), enclosure and RS232 cable.

OBD cable not included.

050092-71

£ 52.50 / \$ 96.95

OBD cable


050092-72

£ 27.55 / \$ 51.95



(September 2005)

 Kit of parts including PCB, default LCD module, 2x16 characters and programmed controllers.



READY-BUILT PROJECTS	12	S
ClariTy 300-W Class-T Amplifier		
030217-91 Amplifier board with SMDs pre-fitted; cores for L1 & L2	34.50	55.70
Electrosmog Tester		
050008-91 PCB, ready built and tested	50-00	94.25
050008-71 Matching enclosure	10-25	19.30
Flash Microcontroller Starter Kit	the two	
010208-91 ready-assembled PCB incl. software, cable, adapter & related articles	69.00	112.50
Gameboy Digital Sampling Oscilloscope (GBDSO)		
990082-91 ready-assembled board, incl. the PC software and related articles	103-00	183.00
LPC210x ARMee Development System		
040444-91 Processor board, ready-made and tested	25-56	48.05
Micro Webserver with MSC1210 Board		
030060-91 Microprocessor Board, ready-assembled	75-90	(
044026-91 Network Extension Board, ready-assembled	44-50	
	117.50	220 95
NO. 354 MAY 2006		
Onboard OBD-2 Analyser		
050176-73 LCO, 4x20 characters with backlight		
050176-72 Kit of pasts, incl. 050176-1, 050176-2, 050176-42, all components.	exel, LC	ġ.
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components; 050176-74 Case, Boola Unimas 160 with Perspex cover and mounting plate	****	
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega16, programmed	10-30	19.45
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components, 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega16, programmed 050092-71 Kit of parts without cable	10-30 52-50	19.45 96.95
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components, 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega16, programmed 050092-71 Kit of parts without cable 050092-72 DB9 to OBD adapter cable	10-30	19.45 96.95
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components, 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega16, programmed 050092-71 Kit of parts without cable 050092-72 DB9 to OBD adapter cable Mini ATMega Board	10-30 52-50 27-55	19.45 96.95 51.95
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components, 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega16, programmed 050092-71 Kit of parts without cable 050092-72 DB9 to OBD adapter cable Mini ATMega Board 050176-1 PCB, includes adapter PCB 050176-2	10-30 52-50 27-55	19.45 96.95 51.95
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components, 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega16, programmed 050092-71 Kit of parts without cable 050092-72 DB9 to OBD adapter cable Mini ATMega Board 050176-1 PCB includes adapter PCB 050176-2 NO. 353 APRIL 2006	10-30 52-50 27-55	19.45 96.95 51.95
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components. 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega16, programmed 050092-71 Kit of parts without cable 050092-72 DB9 to 0BD adapter cable Mini ATMega Board 050176-1 PCB, includes adapter PCB 050176-2 INO, 353 APRIL 2006 Simple recharable A Cell Analyser	10-30 52-50 27-55 8-95	19.46 96.95 51.96
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components, 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega 16, programmed 050092-71 Kit of parts without cable 050092-72 DB9 to OBD adapter cable Mini ATMega Board 050176-1 PCB includes adapter PCB 050176-2 NO. 353 APAIL 2006 Simple recharable A Cell Analyser 050394-1 PCB, bare	10-30 52-50 27-55 8-95	19.45 96.95 51.95 16.85
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components. 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega 16, programmed 050092-71 Kit of parts without cable 050092-72 DB9 to 0BD adapter cable Mini ATMega Board 050176-1 PCB, includes adapter PCB 050176-2 NO. 353 APAIL 2006 Simple recharable A Cell Analyser 050394-1 PCB, bare 050394-11 Disk, PC Software	10-30 52-50 27-55 8-95	19.45 96.95 51.95 16.85
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components; 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42. ATmega16, programmed 050092-71 Kit of parts without cable 050092-72. DB9 to OBD adapter cable. Mini ATMega Board 050176-1 PC6, Includes adapter PCB 050176-2. NO. 353 APRIL 2006 Simple recharable A Cell Analyser 050394-1 PCB, bare 050394-11. Disk, PC Software. Universal SPI Box	10-30 52-50 27-55 8-95 4-60 5-18	19.46 96.95 51.95 16.85 9.75
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components: 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega16, programmed 050092-71 Kit of parts without cable 050092-72 D69 to O60 adapter cable 050092-72 D69 to O60 adapter cable 050176-1 PC6, includes adapter PC6 050176-2 NO. 353 APRIL 2006 Simple recharable A Cell Analyser 050394-1 PC6, bare 050394-11 Disk, PC Software Universal SPI Box 050198-41 AT89C2051-24PC, Programmed	10-30 52-50 27-55 8-95	19.46 96.95 51.95 16.85 9.75
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components; 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42. ATmega16, programmed 050092-71 Kit of parts without cable 050092-72. DB9 to OBD adapter cable. Mini ATMega Board 050176-1 PC6, Includes adapter PCB 050176-2. NO. 353 APRIL 2006 Simple recharable A Cell Analyser 050394-1 PCB, bare 050394-11. Disk, PC Software. Universal SPI Box	10-30 52-50 27-55 8-95 4-60 5-18	19.46 96.95 51.95 16.85
050176-72 Kit of parts, incl. 050176-1, 050176-2, 050176-42, all components: 050176-74 Case, Bopla Unimas 160 with Perspex cover and mounting plate 050176-42 ATmega16, programmed 050092-71 Kit of parts without cable 050092-72 D69 to O60 adapter cable 050092-72 D69 to O60 adapter cable 050176-1 PC6, includes adapter PC6 050176-2 NO. 353 APRIL 2006 Simple recharable A Cell Analyser 050394-1 PC6, bare 050394-11 Disk, PC Software Universal SPI Box 050198-41 AT89C2051-24PC, Programmed	10-30 52-50 27-55 8-95 4-60 5-18	19.45 96.95 51.95 16.85 9.04 9.75

050179-1 PC8	13-77	25:94
030451-72 LCD with backlight	7-25	13.65
030451-73 Poly-LED display	25-50	48.05
FPGA-Prototyping board		
050370-91 Ready assembled board		
For subscribers	171-80	323.50
For non-subscribers	206-30	388.50
Telephone Eavesdropper	·	
030379-1 PCB	9.05	17.05
Versatile FPGA Module		
040477-91 Ready assembled plug-on module		
For subscribers	171-60	323.50
For non-subscribers	206-30	388.50
NO. 351 FEBRUARY 2006		
Brushless Motor Controller		
050157-41 ST7MC1, programmed	3-20	7.15
A 16-bit Tom Thumb		
A 10-Dit 10III HIGHID,		
050179-91 R&C Starter Kit	8:30	15.60
	8:30	15.60
050179-91 R8C Starter Kit	8:30	15.60
050179-91 RSC Starter Kit NO. 350 JANUARY 2006	8:30 4:80	15.60 9.05
050179-91 R8C Starter Kit NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB		
050179-91 R8C Starter Kit NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB	4.80	
050179-91 R8C Starter Kit NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller	4-80 5-20	9.05 9.75
050179-91 R8C Starter Kit NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller 050139-11 Disk PIC source & fiex code 050139-41 PIC16F84A-201/P, programmed 030451-72 LCD Modue 2x16 characters	4-80 5-20	9.05 9.75
050179-91 R8C Starter Kit NO. 350 JANUARY 2005 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller 050139-11 Disk PIC source & hex code 050139-41 PIC16F84A-201/P, programmed	4-80 5-20 13-10	9.05 9.75 24.65
050179-91 R8C Starter Kit NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller 050139-11 Disk, PIC source & hex code 050139-41 PIC16F84A-20t/P, programmed 030451-72 LCD Module 2x16 characters 030451-73 PLED Module 2x16 characters	4-80 5-20 13-10 7-25	9,05 9,75 24,65 13,65
050179-91 R8C Starter Kit NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller 050139-11 Disk, PIC source & hex code 050139-41 PIC16F84A-20I/P, programmed 030451-72 LCD Module 2x16 characters 030451-73 PLED Module 2x16 characters	4-80 5-20 13-10 7-25 25-50	9,05 9,75 24,65 13,65
050179-91 R&C Starter Kit NO. 350 JANUARY 2005 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller 050139-11 Disk PIC source & frex code 050139-41 PIC16F84A-201/P, programmed 030451-72 LCD Module 2x16 characters 030451-73 PLED Module 2x16 characters SMD Reflow Soldering Oven	4-80 5-20 13-10 7-25 25-50 5-20	9.05 9.75 24.65 13.65 48.05
NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029:1 PCB Automatic Attic Window Controller 050139:11 Disk PIC source & hex code 050139:41 PIC16F84A-201/P, programmed 030451:72 LCD Module 2x16 characters 030451:73 PLED Module 2x16 characters SMD Reflow Soldering Oven 050319:11 Disk source and hex code 050319:41 AT89C52/24JI, programmed 030451:72 LCD Module 2x16 characters	4-80 5-20 13-10 7-25 25-50 5-20 7-60 7-25	9.05 9.75 24.65 13.65 48.05 9.75 14.25 13.65
NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller 050139-11 Disk PIC source & hex code 050139-41 PIC16F84A-20I/P, programmed 030451-72 LCD Module 2x16 characters 030451-73 PLED Module 2x16 characters SMD Reflow Soldering Oven 050319-11 Disk source and hex code 050319-41 AT89C52/24JI, programmed	4-80 5-20 13-10 7-25 25-50 5-20 7-60	9.05 9.75 24.65 13.65 48.05 9.75 14.25 13.65
NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller 050139-11 Disk PIC source & hex code 050139-41 PIC16F84A-201/P, programmed 030451-72 LCD Module 2x16 characters 030451-73 PLED Module 2x16 characters SMD Reflow Soldering Oven 050319-11 Disk source and hex code 050319-41 AT89C52/24JI, programmed 030451-72 LCD Module 2x16 characters	4-80 5-20 13-10 7-25 25-50 5-20 7-60 7-25	9.05 9.75 24.65 13.65 48.05 9.75 14.25 13.65
NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller 050139-11 Disk PIC source & hex code 050139-41 PIC16F84A-20VP, programmed 030451-72 LCD Module 2x16 characters 030451-73 PLED Module 2x16 characters SMD Reflow Soldering Oven 050319-11 Disk source and hex code 050319-41 AT89C52/24JI, programmed 030451-72 LCD Module 2x16 characters 030451-73 PLED Module 2x16 characters Timer Switch for Washing Machine 050058-1 PC8	4-80 5-20 13-10 7-25 25-50 5-20 7-60 7-25	9.05 9.75 24.65 13.65 48.05 9.75 14.25 13.65
NO. 350 JANUARY 2006 95-watt Laptop PSU Adaptor 050029-1 PCB Automatic Attic Window Controller 050139-11 Disk PIC source & hex code 050139-41 PIC16F84A-201/P, programmed 030451-72 LCD Module 2x16 characters 030451-73 PLED Module 2x16 characters SMD Reflow Soldering Oven 050319-11 Disk source and hex code 050319-41 AT89C52/24JI, programmed 030451-72 LCD Module 2x16 characters 030451-73 PLED Module 2x16 characters Timer Switch for Washing Machine	4-80 13-10 7-25 25-50 5-20 7-80 7-25 25-50	9.75 24.65 13.65 48.05 9.75 14.25 13.65 48.05


nline at lectronics.co.uk

Due to practical constraints, final illustrations and specifications may differ from published designs. Prices subject to change. See www.elektor.electronics.co.uk for up to date information.

FPGA Project Bundle (FPGA Module & FPGA Prototyping Board) (March 2006)

Ready-assembled Versatile FPGA Module:

 - Altera Cyclone FPGA (12,060 LE's!)
- 4 Mbit configuration RAM
- 8 Mbit user RAM (20nS!)
- 1 Mbit user FLASH memory
- 80 user I/O lines
- 1 dedicated fast clock input
- 4 dedicated PLL outputs
- integrated power supply unit
- 50MHz oscillator



Kits & Modules

Including programming interface, programming cables, connectors and ready-assembled FPGA Prototyping Board.


Special Offer for subscribers: £ 275.00 Non-subscribers: £ 324.00

The Versatile FPGA Module (no. 040477-91) and the FPGA Prototyping Board (no. 050370-91) are also available individually. See www.elektor-electronics.co.uk for more details.

A 16-bit Tom Thumb

(February 2006)

 R8C Starter Kit comprising CD-ROM and R8C/13 microcontroller board with SIL pinheaders supplied separately.



050179-91 £ 8.30 / \$ 15.60

040015-41 ATmega8-16PC, programmed

Application Board for R8C/13

(March 2006)

Extends R8C/13 micro module with 2 x serial I/O. USB, LCD, LEDs, analogue I/P, PSU and, reset and MODE control.

Elektor Electronics (Publishing)

Email: sales@elektor-electronics.co.uk

Regus Brentford

United Kingdom

1000 Great West Road

Tel.: +44 (0) 208 261 4509

Fax: +44 (0) 208 261 4447

Brentford TW8 9HH



050179-92

15-50 29.25

£ 48.27 / \$ 90.94

LCD with backlight

£ 7.25 / \$ 13.65

Poly-LED display 030451-73 £ 25.50 / \$ 48.05



040015-11	Disk, project software	5.20	9.75
Precision	Barometer/Altimeter		
040313-11	Disk, project softwere	5.20	9.75
	PIC16F876, programmed	16-55	
040313-1			14.25
Racetraci	Timer		
The second secon	AT89C2951-24P1	8-85	12.95
040395-81	COROM, project software	5 15	9.75
NO. 345	JULY/AUGUST 2005		
1 MHz Fre	equency Counter		
030045-11	Disk, project software	5-20	9:75
030045-41	AT90S2313-10PI, programmed	5.50	10.35
	k with One Button		
	Disk, source & hex files	5-20	9/75
040481-41	PIC16F84, programmed	6-85	
Digital VU	Meter	- 14	
050118-11	Disk, Affiny software	5-20	9.75
050118-41	Attiny 15L, programmed	3-40	6,45
DIL/SOIC/	TSSOP Adapter Boards		:
040289-1	PCB, for 20-way DIL IC	6.75	12.70
040289-2	PCB, for 20-way SOIC IC	6.75	12.70
040289-3	PCB, for 29-way TSSOP IC	6-75	12.70
MP3 Adap	otor for TV		
054035-1		3-95	7.50
	Disk, project software	5.20	9.75
	EPM7064SLC44-10, programmed	27-55	51.95
DBD-2 Ar	alyser		
	PCS, bare	8-95	16.85
050092-41	T89C51CC02UA, programmed	26-20	49.40
	Kit of peris without cable	52.50	95.95
050092-72	DS9 to OSD adapter cable	27-55	51,95

Products for older projects (if available) may be found on our website www.elektor-electronics.co.uk

home construction = fun and added value



Scopemeters Compared

Everyone serious about electronics as a profession but also as a pastime will need to use an oscilloscope from time to time. The conventional oscilloscope is usually powered from the mains and designed to stay on the test bench for most of its useful lifetime. By contrast, a new generation of instruments called scopemeters is designed for portability and use 'in the field'. In the next issue we will provide a market overview of available instruments.

Electronic Passports

If your passport runs out in the next few months the chances are you could be issued with one of the new electronic passports that are being introduced throughout the EU this year. ePassports have an embedded RFID tag containing your personal information which Immigration officials can read remotely; hopefully nobody else will be eavesdropping on this electronic conversation...

Theme Plan for 2006

January Recycling / Reverse Engineering February Motors / Propulsion

March Development / Microcontrollers April Power Supplies / Safety May Soldering / Etching

JuneTest & Measurement

July/August ... Summer Circuits RFID / Medical Electronics September

OctoberE-Simulation NovemberChipcards / Security

.Electromechanical / Enclasures December ...

Also ...

Lambda Probes: PCB Short Circuit Locator; FM Stereo Test Transmitter; FPGA Course (3); E-blocks for X10 Networks; Hexadoku Puzzle.

Network Cable Tester

Computer networks are not just found in offices but also in private homes, albeit at a smaller scale in most cases. Everything's just fine as long as the network does what it's supposed to do, but when problems start to occur, a good tester is in order to pinpoint the cable or connection that needs to be replaced. In our design for such a tester, a PIC 16F874 checks the four wire pairs for proper connectivity, showing the result on four LEDs. A separate switch allows (Gigabit) cross-over cables to be tested as well.

RESERVE YOUR COPY NOW!

The June 2006 issue goes on sale on Thursday 11 May 2006 (UK distribution only).

UK subscribers will receive the magazine a few days before this date.

Article titles and magazine contents subject to change.

NEWSAGENTS ORDER FORM

SHOP SAVE / HOME DELIVERY

Please save / deliver one copy of Elektor Electronics magazine for me each month

Name: Address: Post code: Telephone:

Date: Signature: lektor

Please cut out or photocopy this form, complete details and hand to your newsagent. Elektor Electronics is published on the third Friday of each month, except in July. Distribution S.O.R. by Seymour (NS).

www.elektor-electronics.co.uk www.elektor-electronics.co.uk www.elektor-electronic

Elektor Electronics on the web

All magazine articles back to volume 2000 are available online in pdf format. The article summary and parts list (if applicable) can be instantly viewed to help you positively identify an article. Article related items are also shown, including software downloads, cir-

cuit boards, programmed ICs and corrections and updates if applicable. Complete magazine issues may also be downloaded.

In the Elektor Electronics Shop you'll find all other products sold by the publishers, like CD-ROMs, kits and books. A powerful search function allows you to search for items and references across the entire website.

Also on the Elektor Electronics website:

- Electronics news and Elektor announcements
- Readers Forum,
- PCB, software and e-magazine downloads
- Surveys and polls
- FAQ, Author Guidelines and Contact



elektor electronics - 5/2006 84

Please supply the following. For PCBs: front panel foils, EPROMs, PALs, GALs, microcontrollers and diskettes, state the part number and description; for books, state the full title; for photocopies of articles, state full name of article and month and year of publication. PLEASE USE BLOCK CAPITALS.

Description		Price each	Qty.	Total	Order Code	METHOD OF PAYMENT			
	C-C-LAI					(see reverse before ticking as appropriate)			
CD-ROM Elektor 2005	NEW	£ 16.25	41			Bank transfer			
CD-ROM Home Automation	NEW	2 12.95	-			Cheque			
Visual Basic for Electronics	NEW					(UK-resident customers ONLY)			
Engineering Applications		£ 27.50		<u> </u>		Giro transfer			
Microcontroller Basics		٤ 18.70				VISA Masterian			
E-blocks Starter Kit basic		€ 96.00							
E-blocks Starter Kit professiona		£ 166.00							
						Expiry date:			
						Verification code:			
						SWITCH ONLY:			
						Start date:			
						Issue number:			
Prices and item descriptions subject to change.		Sub-total P&P				Please send this order form to "			
The publishers reserve the right to change prices without prior notification. Prices and item descriptions						(see reverse for conditions)			
shown here supersede those in previous issues. E. & O.E.		Total paid				Elektor Electronics (Publishing)			
					1	Regus Brentford			
						1000 Great West Road			
Name						Brentford TW8 9HH			
T TELL PRO						United Kingdom			
Address + Post code						Tel.: (+44) (0) 208 261 4509 Fax: (+44) (0) 208 261 4447 Internat: www.elektor-electronics.co.uk sales@elaktor-electronics.co.uk			
						*USA and Canada residents may (but are not obliged to)			
Tel.		Email				use 5 prices, and send the order form to: Did Colony Sound Lab			
Date — —	2006 8	Rignature				P.O. Box 876, Peterbordugh NH 03458-0576, Tet. (603) 924-6371, 924-6526			
EL05						Fax: (503) 924-9467 Email: custserv@audisXpress.com			
Yes, I am taking out an to elektor electronics a 1 W Luxeon LED Torchi	nd rece			on		METHOD OF PAYMENT (see reverse before ticking as appropriate) Bank transfer Cheque (UK-resident customers ONLY) Giro transfer			
Standard Subscription (11	(squas)					UISA S			
	issuesi					Master and			
Subscription-Plus (11 issues plus the Elektor	Volume 2	006 CD-RO	M)						
* Offer available to Subscribers who have to Elektor Electronics during the last 12 See reverse for rates and conditions.			iilability			Verification code:			

1 W Luxeon LED Torchlight.
I would like:
Standard Subscription (11 issues)
Subscription-Plus
(11 issues plus the Elektor Volume 2006 CD-ROM)
Offer available to Subscribers who have not held a subscription to Elektor Electronics during the last 12 months. Offer subject to availability. See reverse for rates and conditions.
Name
Address + Post code
<u> </u>
Tel. Email
Date – – 2006 Signature
* cross out what is not applicable
ELO5

Cheque (UK-resident customers ONLY)
Giro transfer
VISA Mastertand
Expiry date:
Verification code:
SWITCH ONLY: Start date:
Issue number:

Please send this order form to

Elektor Electronics (Publishing)

Regus Brentford 1000 Great West Road Brentford TW8 9HH United Kingdom

Tel.: (+44) (0) 208 261 4509 Fax: (±44) (0) 208 261 4447 Internet; www.elektor-electronics.co.uk subscriptions@elektor-electronics.co.uk

ORDERING INSTRUCTIONS, P&P CHARGES

Except in the USA and Canada, all orders, except for subscriptions (for which see below), must be sent BY POST or FAX to our Brentford address using the Order Form overleaf. On-line ordering: http://www.elektor-electronics.co.uk

Readers in the USA and Canada may (but are not obliged to) send orders, except for subscriptions (for which see below), to the USA address given on the order form. Please apply to Old Colony Sound for applicable P&P charges. Please allow 4-6 weeks for delivery. Orders placed on our Brentford office must include P&P charges (Priority or Standard) as follows:

UK: £4.00 Europe: £5.00 (Standard) or £7.00 (Priority) Outside Europe: £8.00 (Standard) or £12.00 (Priority)

HOW TO PAY

All orders must be accompanied by the full payment, including postage and packing charges as stated above or advised by Customer Services staff.

Bank transfer into account no. 40209520 held by Elektor Electronics (Publishing) / Segment b.v. with ABN-AMRO Bank, London, IBAN: GB35 ABNA 4050 3040 2095 20, BIC: ABNAGB2L, Currency: sterling (UKP). Please ensure your full name and address gets communicated to us.

Cheque sent by post, made payable to Elektor Electronics (Publishing) / Segment b.v.. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics (Publishing) / Segment b.v. Please do not send giro transfer/deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA, Access, MasterCard, JCBCard and Switch cards can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

COMPONENTS

Components for projects appearing in Elektor Electronics are usually available from certain advertisers in this magazine. If difficulties in the supply of components are envisaged, a source will normally be advised in the article. Note, however, that the source(s) given is (are) not exclusive.

TERMS OF BUSINESS

Delivery Although every effort will be made to dispatch your order within 2-3 weeks from receipt of your instructions, we can not guarantee this time scale for all orders. Returns Faulty goods or goods sent in error may be returned for replacement or refund, but not before obtaining our consent. All goods returned should be packed securely in a padded bag or box, enclosing a covering letter stating the dispatch note number. If the goods are returned because of a mistake on our part, we will refund the return postage. Damaged goods Claims for damaged goods must be received at our Brentford office within 10-days (UK); 14-days (Europe) or 21-days (all other countries). Cancelled orders All cancelled orders will be subject to a 10% handling charge with a minimum charge of £5:00. Patents Patent protection may exist in respect of circuits, devices, components, and so on, described in our books and magazines. Elektor Electronics (Publishing) does not accept responsibility or liability for failing to identify such patent or other protection. Copyright All drawings, photographs, articles, printed circuit boards, programmed integrated circuits, diskettes and software carriers published in our books and magazines (other than in third-party advertisements) are copyright and may not be reproduced or transmitted in any form or by any means, including photocopying and recording, in whole or in part, without the prior permission of Elektor Electronics (Publishing) in writing. Such written permission must also be obtained before any part of these publications is stored in a retrieval system of any nature. Notwithstanding the above, printed-circuit boards may be produced for private and personal use without prior permission. Limitation of liability Elektor Electronics (Publishing) shall not be liable in contract, tort, or otherwise, for any loss or damage suffered by the purchaser whatsoever or howsoever arising out of, or in connexion with, the supply of goods or services by Elektor Electronics (Publishing) other than to supply goods as described or, at the option of Elektor Electronics (Publishing), to refund the purchaser any money paid in respect of the goods. Law Any question relating to the supply of goods and services by Elektor Electronics (Publishing) shall be determined in all respects by the laws of England. January 2006

SUBSCRIPTION RATES FOR ANNUAL SUBSCRIPTION

United Kingdom	Standard £41.90	Plus £48.80
Surface Mail		_
Rest of the World	£54.50	£61:40
USA & Canada	US\$ 95.50	US\$106.50
Alrmail		
Rest of the World	268.90	£75.80
USA & Canada	USS120.00	US\$131.00

HOW TO PAY

Bank transfer into account no. 40209520 held by Elektor Electronics (Publishing) / Segment b.v. with ABN-AMRO Bank, London, IBAN: GB35 ABNA 4050 3040 2095 20. BIC: ABNAGB2L, Currency: sterling (UKP). Please ensure your full name and address gets communicated to us:

Cheque sent by post, made payable to Elektor Electronics (Publishing) / Segment b.v.. We can only accept sterling cheques and bank drafts from UK-resident customers or subscribers. We regret that no cheques can be accepted from customers or subscribers in any other country.

Giro transfer into account no. 34-152-3801, held by Elektor Electronics (Publishing) / Segment b.v. Please do not send giro transfer/ deposit forms directly to us, but instead use the National Giro postage paid envelope and send it to your National Giro Centre.

Credit card VISA, Access, MasterCard, JCBCard and Switch cards can be processed by mail, email, web, fax and telephone. Online ordering through our website is SSL-protected for your security.

SUBSCRIPTION CONDITIONS

The standard subscription order period is twelve months. If a permanent change of address during the subscription period means that copies have to be despatched by a more expensive service, no extra charge will be made. Conversely, no refund will be made, nor expiry date extended, if a change of address allows the use of a cheaper service.

Student applications, which qualify for a 20% (twenty per cent) reduction in current rates, must be supported by evidence of studentship signed by the head of the college, school or university faculty. A standard Student Subscription costs £33.50, a Student Subscription-Plus costs £40.40 (UK only).

Please note that new subscriptions take about four weeks from receipt of order to become effective.

Cancelled subscriptions will be subject to a charge of 25% (twentyfive per cent) of the full subscription price or £7.50, whichever is the higher, plus the cost of any issues already dispatched. Subsciptions cannot be cancelled after they have run for six months or more.

January 2006




ISBN 0-905705-68-8 496 pages £27.50 / US\$ 51.50

Visual Basic for Electronics Engineering Applications

This book is targeted towards those people that want to control existing or home made hardware from their computer. After familiarizing yourself with Visual Basic, its development environment and the toolset it offers are discussed in detail. Each topic is accompanied by clear, ready to run code, and where necessary, schematics are provided that will get your projects up to speed in no time.

This book discusses tools like Debug to find hardware addresses, setting up remote communication using TCP/IP and UDP sockets, writing your own internet servers and even connecting your own block of hardware over USB or Ethernet and controlling it from Visual Basic.

 All examples are ready to compile using Visual Basic 5.0, 6.0, NET or 2005. Extensive coverage is given on the differences between what could be called Visual Basic Classic and Visual basic .NET / 2005.



Order now using the Order Form in the Readers Services section in this issue.

Elektor Electronics (Publishing) Regus Brentford 1000 Great West Road Brentford TW8 9HH **United Kingdom** Tel. +44 (0) 208 261 4509

See also www.elektor-electronics.co.uk

INDEX OF ADVERTISERS

ATC Semited Ltd. Showcase:	. www.atcsemites.co.uk	78
Audioxpress, Showcase	. www.ai/dioxpress.com	79
Avit Research, Showcase	www.avitrosearch.co.ek	78
Beta Layout, Showcase	. www.pcb-pcal.com	.57, 78
Bitscape Designs	. www.bitscope.com	7
Steadsoeding Systems		29
Compuser Showease	. www.compaculters.com	78
Computogic, Showcase	. www.compulogic.co.uk	78
Contete Electronics, Showcase	_ www.confordelec.co.uk	78
Crickleivood	_ www.crickiewoodelectronics.com	71
Danbury, Showcase		78
Design Gateway, Showcase	www.design-galeway.com	78
Eaglepics, Showcase	. www.eaglepics.co.uk	78
Easysync, Showcase	. www.easysync.co.uk	.23, 78
Enec, Snowcase	. www.elnes.com	78
Eurocircuits	. www.thepcbshop.com	5
Future Technology Devices, Showcase .	. www.ftdichip.com	78
Futuries, Showcase	. www.futudec.com	78
Heros Technology, Showcase	. www.herostechnology.co.uk	78
Ipeva Limited. Showcase	: www.ipeva.com	
Jaycar Electronics		2
JLB Electronics, Showcase	. www.jibelectronics.com	79
KMK Technologies Ltd, Showcase	. www.kink.com.hk	79
Laboanter	. www.labcenter.co.uk	89
Lichfield Electronics		71
London Electronics College, Showcase	. www.lec.org.uk	75

Microchip	www.microchip.com	
MQP Electronics, Showcase		79
New Wave Concepts, Showcase	www.new-wave-concepts.com	79
Newbury Electronics	www.newburyelectronics.co.uk	
Number Öne Systems:		67
Nurve Networks	www.xgamestation.com	ā
PCB World, Showcase	www.pebworld.org.uk	***
Peak Electronic Design	www.peakelest.co.uk	67
Pico	www.picotech.com	
Quissar Electronics, Showcase	www.quasarelactronics.com	74, 79
ÄD Research	www.spice-software.com	45
Robot Electronics, Showcase	www.ronat-electronics.co.uk	
Showcase		78, 79
SK Pang Electronics, Snowcase	www.skpang.co.uk	
Sytronic Technology, Showcase	,www.m2mtelemetry.com	
Ultraleds, Showcase	www.uitraleds.co.uk	
USS Instruments, Showcase	www.usb-instruments.com	
Writing Technology Showings	inský vártice recier	70

Advertising space for the issue of 13 June 2006 may be reserved not later than 16 May 2006

with Huson International Media - Cambridge House - Gogmore Lane -Chartsey, Surrey KT16 9AP - England - Telephone 01932 564 999 -Fax 01932 564998 - e-mail: gerryb@husonmedia.com to whom all correspondence, copy instructions and artwork should be addressed.

87 5/2006 - elektor electronics

PROTEILS ELECTRONIC DESIGN

FROM CONCEPT



SCHEMATIC CAPTURE PROSPICE EMBEDDED SIMULATION PCB DESIGN

1515 SCHEMATIC CAPTURE

A powerful capture package tailored for todays engineer and designed to allow rapid entry of complex schematics for simulation and PCB Layout.

PROSPICE MIXED MODE SIMULATOR

A customised implementation of the industry standard Berkeley SPICE 3F5 engine with extensive optimisations and enhancements for true mixed mode simulation and circuit animation.

VSM VIRTUAL SYSTEM MODELLING

The worlds first and best schematic based microcontroller co-simulation software. Proteus VSM allows you to simulate the interaction between software running on a microcontroller and any analog or digital electronics connected to it. This streamlines the project lifecycle and obviates the need for expensive hardware analysis tools.

ARES PCB DESIGN

A modern and professional layout package which seamlessly integrates with the ISIS capture software. Features such as autoplacement and autorouting, interactive DRC and an intuitive interface all serve to maximise productivity and reduce time to market.

DATE DENTER ELECTRONIES LTD.

A technology pioneer in the EDA industry since 1988.

Technical support direct from the program authors.

Flexible packages and pricing tailored to customer requirements.

abcenter/\/\/\/_{www.labcenter.co.uk}

CONTACT US NOW

to discuss requirements or request a FREE evaluation copy.

Tel: 01756 753440 Fax: 01756 752857 Email: info@labcenter.co.uk

Labcenter Electronics Ltd., 53-55 Main Street, Grassington, North Yorks, 8023 5AA. Registered in England 4692454